

A REVOLUTIONARY NEW RECEIVER!

MAY • JUNE 1964

GRID PEAKS

R/C
DATA
SERVICE

VOLUME 5 • NUMBER 3 • THIRTY-FIVE CENTS

SPECIAL!

For the first time GL prints plans for an airplane, an excellent low wing especially tailored to the demands of a multi-proportional system—

it's Bob Ferris' "R/C Jay."



BOB FERRIS WITH HIS .45-POWERED "R/C JAY." ITS SIMPLE CONSTRUCTION AND EASY-TO-FLY TRAITS MAKE IT POPULAR IN HIS AREA.

8th YEAR OF SERVICE TO THE R/C MODELER

A Radio Control Publication for Beginner & Advanced Modeler

Grid Leaks at Play	1
The Monitor	1
An Interference Resistant Receiver	4
Half Pint	6
The Gemini Single Channel Transmitter Switcher	8
Proportional Control in Perspective	11
R/Cing The Bulldog Tank	12
Improving The Marcy PRM-1 System	14
The R/C Jay	15
R/C Jay Plans	16 & 17
Seen These?	18
Bits and Pieces	20
Notes on Superhet Receivers	22

PAUL RUNGE, Publisher—WILLIAM WINTER, Editor
 WITTICH HOLLOWAY, Art Director—BOBBIE RUNGE, Sec.-Treas.
 Contributing Editors: Gordon Flenniken—Phil Kraft
 Frank Schwartz—Dale Springsted—John Worth—John Phelps

GRID LEAKS is a bi-monthly publication, and is intended for the modeler who is interested in Radio Control. It is published by Ace R/C, Inc., at 203 W. 19th Street, Higginsville, Mo. Copyright 1964 by Ace R/C, Inc. Subscription rate is \$2.00 per 6-issue volume. For subscriptions outside the United States, add \$1.00 for postage. GRID LEAKS is a registered trademark.

FOREIGN SUBSCRIBERS: GRID LEAKS Subscription Agent for ENGLAND and all CONTINENTAL COUNTRIES is THE MODEL AERONAUTICAL PRESS, LTD. 38 Clarendon Road, Watford, Herts, England

Application for second class mailing privileges is pending at the post office in Higginsville, Mo. and at additional mailing offices.

GRID LEAKS AT PLAY

● The last issue of GRID LEAKS contained no ringbinder holes. This was done as an experiment to get reader reaction. As this is being written it is, of course, too early to say whether or not there will be a reaction or, if there is, to predict what that reaction will be. We'd be interested in your comments.

Phil Kraft's article "Proportional Control in Perspective," page 11, we feel is extremely timely, and we have presented it exactly as written by Phil, and recommend you read it attentively.

This article reminded us of a shirt worn by Gordon Gabbert, who is well known in R/C circles, and caused us to dig out a photograph which appeared in a 1960 issue of GRID LEAKS. The shirt says distinctly, "Smile Dammit, It's Just a Hobby." Food for thought?

● Progress is being made on the FCC front. If you have not read it elsewhere, you will be pleased to know that your contributions have made it possible to retain Jeremiah Courtney, a Washington, D.C. communications attorney and that his retention is on a continuing basis.


We'd like to point up one thing here, however, and that is that any actions before the FCC do take time, and we feel patience is of extreme importance. Your AMA-FCC Committee is functioning, and we feel functioning very well. Your interests are in the hands of a capable communications representative.

This is just another one of the many little factors which we feel should demonstrate that the AMA is in there pitching for all your interests. In connection with AMA we'd like to pass on a word of commendation to John Worth, new Executive Director, and the new President, Maynard Hill, for the job that they have begun to do.

● This issue of GRID LEAKS marks an innovation in that we are offering for the first time a full-size plan of a model airplane. (R/C Jay, multi, page 15.) Check our listing elsewhere as to how these plans may be obtained. Lest any of our readers assume that this will mean that there will be a downgrading of the electronic articles for the home builder, this is just not the case. With an expanded number of pages, GRID LEAKS is trying to round out its policy, and still (Continued on page 26)

THE MONITOR

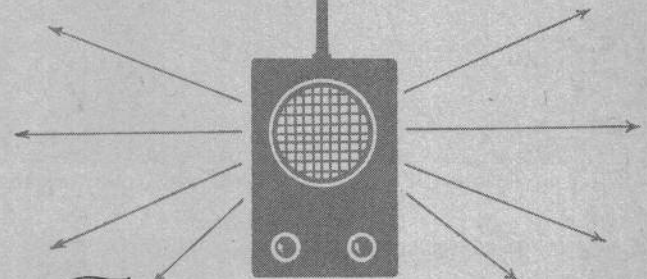Regular round-up of new and overlooked aspects of the growing R/C field • Shop talk and just talk • A discussion corner.



HERE WAS ONCE A SAYING, that what the world needed was a good five-cent cigar. What we need in radio control today is a good \$50 multi-proportional rig. As you will discover from Phil Kraft's timely "Proportional Control in Perspective" on page 11 we may yet see a \$1000 radio. What Vernon Macnabb pointed up in his March-April GL article "What Level of Excellence," Phil now puts into sharper focus and that is, what we demand, costs a lot of money.

At this late date only a few manufacturers are expected to deliver production they are capable of this year. Their lot is not a happy one. Having read both the Macnabb and Kraft articles you will find the reasons obvious. Perhaps it is time to put all radio control into perspective, and not just proportional multi.

Cost always is important. Whether a radio system costs \$75, \$150, \$250, \$500—or a \$1000—the investment is a serious matter to most modelers. The appeal of radio control is something we all understand from firsthand experience and most of us know that, once started, there is a, shall we say, a yearning for something better—more controls and more realism in controls. Those of us who are living it up on top of the pyramid seem little concerned that the overwhelming majority of hobbyists must have a maximum of guaranteed success, regardless of equipment cost.

Is multi—that is 10 and 12 channels and full-proportional—all that matters? Not long ago a magazine published a multi design only when some significant advance had been made—the Smog Hog, Astro Hog, Orion, Sequence for example—but today all publications seem caught in the same bind as the equipment manufacturers who, in the case of proportional, must make a move only because competition forces them to. No one even remembers now all the multis that have been published in recent times, and only a few are built by many people. Contest rules, even in so-called rudder-only, reflect this preoccupation. Flying is not fun unless the equipment, airplanes, are complex and costly.

Stu Babcock tells us that a quarter-million of his compound escapements have been sold. It is conceivable that over a half-million escapements have been manufactured. Where did they go? How many single-channel radios have been produced? How many are in use today? What happened to the others? Judging by the relatively low number of 505's filled out, most of this equipment never got into the air, or into a boat. Why?

It is well, we think, to ask whether proportional. But there are other more important questions we should be asking. The hobby, the industry, is failing the beginner, the typical less-talented, and perhaps untalented, builder who is our most important customer.

A *Science and Mechanics* reader tells us: "I received a Concord for Christmas but have not started building it because I wasn't sure what size engine to use. I am new in R/C flying, having built only a Live Wire trainer and have only one flight on that. All of us here are new to R/C. None can agree on what size engine to use since this plane seems so much smaller than the 'trainer.' What should I use, as a beginner in R/C?"

A *MAN* reader tells us: "I started out by buying a lot of model magazines and reading every word several times over, hoping in this way to learn. Due to (Continued on next page)



At a St. Louis contest, L. to R.: Don Dickerson, John Rawlings, Norm Beeler, Jim Reuter. System is first model of the B & D.

THE MONITOR ...continued

the way most of the articles are written, I have learned very little. You buy a magazine because a certain article strikes your fancy and if you are just getting started, as I am, the whole thing is over your head.

"What on earth is a P.O.D. control? Or a Galloping Ghost? Or an REM servo or for that matter, a compound escapement, to a greenhorn like me?"

That this chap is an MAN reader is of no special significance, he probably reads all the books, and the problem is universal. The public's chief beef is the jargon we all speak. Even the advertisers, who should know better, describe their products in a mysterious language—and it might not help understanding of the gadget and its function even if it was better termed. All editors receive such letters. Suppose we follow the career of this particular tyro. What did he do next?

"I decided to seek out someone that would explain these things to me," he told G.L. "A trip to the local hobby shop was a total zero." (An industry problem is that most retailers don't comprehend the merchandise they handle.) He didn't even have any gas models in stock and absolutely no knowledge of gas-powered aircraft.

"After a few weeks of searching I got wind of a modeler living 50-odd miles away. I drove over to see him but he was away on business. So I wrote him. My questions must have been stupid because I never got an answer. There was only one course left, and that was to write a dealer in New York, order a bunch of stuff and try to figure it out for myself."

Tony, for that is his name, says the model building was not a problem, because basically there isn't a great deal of difference between a rubber job and a gas job, and the glow engine people give a lot of information on the care and feeding of their babies. His problem was figuring out the R/C end of it. By chance he picked a good subject—a deBolt Super Cub.

Tony built from a kit a large tube-type receiver and he stuck a KB 19 in the four-pound airplane. (It seems you can't convince anybody in the business that we over power all beginner airplanes, or, put another way, make them undersize for power specified.) Tony's Cub got to 5,000 feet (he thinks) in 1½ minutes before he thought what to do. When he spiralled

(Continued on page 31)



Tom Shortt, Ireland, made twin-screw Meccano gears. Two MM motors for actuation purposes. Hull length is 46 inches.

THE GL ARTICLE "STYROFOAM — THE MATERIAL OF THE

Future" in the March-April issue — a reprint from the *Montreal Model Bugs* and incidentally, held out of several preceding issues for lack of space — appeared just two weeks before the excellent and most comprehensive feature by Ed Izzo and Ray Olsson was published in MAN. In deference to the then forthcoming MAN coverage, GL confined reporting of the Izzo demonstrations at the Bisons' Conference exhibition to certain facts released by Ed, and included in Joe Niedermayr's GL article one of the Izzo drawings of a multi wing detail. While GL was permitted to trace that drawing it developed afterwards that, while approval for the tracing had been given, the exhibiting personnel had not cleared it with Ed, who thus had no knowledge the drawing was "out" until its "double-exposure." To make things worse for poor Ed, the GL drawing lost its credit line somewhere along the way, with the resulting implication that operator "X-9" was on the scene! Poor Ed and Ray, who had raised these techniques to a truly scientific level, might even have been assumed by innocent readers, to have borrowed Ed's own wing, and construction, from the Canadian control-line people who had already published their earlier but less developed techniques in their club paper. GL is anxious that our friends from Syracuse lose no prestige because of that lost credit line on the drawing which appeared on page 24 in the last issue.



AHC HAS 'EM ALL!

Radio Control

"KYOWA 45" R/C

SPECIAL 995 REG. 19.95

1/2 Price Sale!

AN EXCELLENT GLO PLUG ENGINE FOR RADIO CONTROL - SPECIAL STEEL ALLOY USED FOR CYLINDER & PISTON... LIVES LONGER LIFE... WEIGHT 0.02, MAX. RPM: 12,000, BORE: .8625 STROKE: .7530, DISPL: .4531, COMP. RATIO 9:1

ORDER-BY-MAIL FROM AMERICA'S HOBBY CENTER, 1466L West 22nd. St. N.Y., N.Y. 10011

SPECIAL BONUS OFFERS

Get all these AHC EXTRAS

FREE! OF EXTRA COST WITH EVERY RECEIVER

FREE! OF EXTRA COST WITH EVERY TRANSMITTER

ORDER BOTH RECEIVER & TRANSMITTER AT THE SAME TIME & YOU GET EVERYTHING LISTED ABOVE, PLUS A FREE SOLDERING IRON... SORRY NO BONUS WITH EQUIPMENT ALREADY SAID PRICED... FREQUENCY REMARK WITH EVERY TRANSMITTER

SENSATIONAL VALUE

HERE'S A RED HOT AHC OFFER SAVE **35.05** ON THIS **110.00** R/C DELUXE OUTFIT

SALE \$74.95

WHILE SUPPLY LASTS!

HERE'S WHAT YOU GET:

- R/C AIRCRAFT AIRPLANE \$14.95
- VECO 19 R/C ENGINE... 19.95
- ECK. PACESETTER TRANS... 34.95
- ECK. COURIER RECEIVER... 21.95
- ECK. COMPOUND ESC... 9.95
- ECK. MOTOR CONTROL... 9.95
- ECK. INSTALLATION KIT... 3.70
- R/C TANK & FUEL LINE... 1.20
- 10' WOOD MODEL... 1.20
- ESCAPEMENT RUBBER... 1.15

TOTAL VALUE **\$110.00** HURRY! QUANTITIES ARE LIMITED! ORDER NOW!

COMPLETE R/C DIGITRAN SYSTEM

BCI-19 TRANSMITTER (8 TRANSMITTERS) \$79.95

BCI-18 TRANSMITTER, MOTOR MINDER \$5.95

HYPER COMP. ESC. ANTOR MINDER ESC. WILL GIVE: RIGHT & LEFT RUDDER UP & DOWN, ELEVATOR, & MOTOR SPEED CONTROL... SPECIFY FREQUENCY... 27,100K, 27,225K... \$39.95

F&M ELECTRONICS PIONEER 27% MC RECEIVER

18.95

SINGLE CHANNEL WT. 1 1/8 OZ. SIZE: 7/8" x 1 1/2" x 2 5/8" RESOLVES OPERATION NO VIBRATION OR CONTACT PROBLEM... V. OPERATOR, ACTUATOR USES SAME BATTERIES... ASSEMBLED

F&M ELECTRONICS ECHO 27% MC TONE TRANS.

29.95

SINGLE CHANNEL FULLY TRANSISTORIZED, DUAL OPERATING, LOADED INTERNALLY... WOPA TYPE CIRCUIT... WITH .005 TOLERANCE... ANTENNA INCLUDED, ASSEMBLED.

SPECIAL OFFER! ALL-TRANSISTOR R/C OUTFIT

WHILE -THEY- LAST!

Ready-To-Operate COMPLETE ASSEMBLED Verified **\$55.00** OUTFIT

\$39.95 Less Batteries

CITIZEN BAND THE WORLD'S FINEST TONE EQUIPMENT OPERATES ANY MODEL BOATS, CARS & PLANES - From 1/4 A. to the Very Largest

TRANSMITTER WEIGHS ONLY 12 OUNCES... MEASURES 3 1/4" x 1 1/2" x 7/8" NO REDUCTION OF RF SIGNAL WITH MODULATION... EFFICIENCY EXTERNALLY LOADED ANTENNA... PRINTED CIRCUIT CHASSIS... REQUIRES NO LICENSE.

RECEIVER SUPER REGENERATIVE RELAYLESS, WEIGHS 1 OUNCE & MEASURES 2 1/8" x 1 1/4" x 7/8" TWO PENNELS OPERATE BOTH THE RECEIVER AND ESCAPEMENT... SMALLEST & LIGHTEST WEIGHT R/C SYSTEM AVAILABLE.

RADIO CONTROL RECEIVERS AND TRANSMITTERS

CITIZENSHIP WDL 1 CHANNEL TONE RECEIVER... WT. 1/2 OZ. MEASURES 3/8" x 1 1/8" x 1 1/8" SMALLER THAN A POSTAGE STAMP... \$29.95

CITIZENSHIP SFX 1 CHANNEL TONE TRANSMITTER, WT. 30 OZ. FULLY TRANSISTORIZED, 5 VOLT OPERATION, LOADED ANTENNA... \$39.95

FAM VANGUARD 1 CHANNEL TONE SUPERSET RECEIVER, WT. 2 1/4 OZ. MEASURES: 1 1/2" x 7/8" x 1 1/8" PRINTED CIRCUIT BOARD... \$39.95

F&M ECHO 1 CHANNEL TONE TRANSMITTER... FULLY TRANSISTORIZED, 5 VOLT OPERATION, ANTENNA INCLUDED... \$29.95

VECO 19 R/C ENGINE... \$19.95

VECO 35 R/C ENGINE... \$28.50

VECO 45 R/C ENGINE... \$37.50

VECO 50 R/C ENGINE... \$49.95

VECO 60 R/C ENGINE... \$59.95

VECO 70 R/C ENGINE... \$69.95

VECO 80 R/C ENGINE... \$79.95

VECO 90 R/C ENGINE... \$89.95

VECO 100 R/C ENGINE... \$99.95

VECO 110 R/C ENGINE... \$109.50

VECO 120 R/C ENGINE... \$119.95

VECO 130 R/C ENGINE... \$129.95

VECO 140 R/C ENGINE... \$139.95

VECO 150 R/C ENGINE... \$149.95

VECO 160 R/C ENGINE... \$159.95

VECO 170 R/C ENGINE... \$169.95

VECO 180 R/C ENGINE... \$179.95

VECO 190 R/C ENGINE... \$189.95

VECO 200 R/C ENGINE... \$199.95

VECO 210 R/C ENGINE... \$209.95

VECO 220 R/C ENGINE... \$219.95

VECO 230 R/C ENGINE... \$229.95

VECO 240 R/C ENGINE... \$239.95

VECO 250 R/C ENGINE... \$249.95

VECO 260 R/C ENGINE... \$259.95

VECO 270 R/C ENGINE... \$269.95

VECO 280 R/C ENGINE... \$279.95

VECO 290 R/C ENGINE... \$289.95

VECO 300 R/C ENGINE... \$299.95

ACE KRAFT K3K VOLT RECEIVER KIT

995 WAS \$79.95

SINGLE CHANNEL TONE, WT. 1 OZ. SIZE: 1 1/8" x 1 1/8" x 3/4" PRINTED CIRCUIT BOARD ON EPAY BOARD, COMPLETELY DRILLED HOLE QUALITY COMPONENTS, 400-500CP ADD ON SWITCHER KIT ASK 2.25

VECO .19 R/C

1195

REG. \$16.95

SMOOTH DEPENDABLE FROM IDLE TO TOP RPM'S WITHOUT A FILTER... HAS VECO .35 R/C THROTTLE FITTING FOR ESCAPEMENT OR SERVO OPERATION REG. \$19.95

SAVE \$60.00

CITIZEN BAND MULTI-CHANNEL RELAYLESS SYSTEMS

ZR-10 RECEIVER

TEN CHANNEL SELECTIVE SUPERSET RELAYLESS NEW STIFFER REED BANK RECEIVER... 6 TRANSISTORS... IMPROVED SENSITIVITY... CHANGED FREQUENCY... INEXPENSIVE 9 VOLT BATTERY... OPERATES WITH TMS TRANSMITTER 27,100 MC 27,225 MC... MEASURES: 2 1/8" x 1 1/4" x 1 1/8"

TMS TRANSMITTER

COMPACTIZED HIGH POWER ALL TRANSISTORIZED MULTI-SIMULTANEOUS FOR RECEIVING OPERATION

OUTPUT EQUIVALENT TONE TRANSMITTER... ABSOLUTE TONE STABILITY TO 140PF... USES ONE 9 VOLT BATTERY... COLLAPSIBLE EXTERNALLY LOADED ANTENNA... WEIGHT 1 1/2 OZ. BATTERIES MEASURES: 6 1/4" x 6 7/8" x 3/4"... AVAILABLE FREQUENCIES: 25, 950-27,045-27,090-27,145-27,195-27,255 MC...

an unbeatable R/C TOTAL RETAIL VALUE \$199.95

Combination that Challenges ANY COMPARISON

SPECIAL OFFER! ON SERVO MADE FOR THE ABOVE SET

REG. \$25.95 TRANSISTORIZED SERVO

FOR DIRECT OPERATION ON ANY STANDARD REED BANK... PUSH AND PULL RATIO... 1988 ADJUSTABLE, SAME AS TCA EACH... LESS CAM ACTION.

139 FULLY GUARANTEED

FALCON JR.

395

37" WINGSPAN, FOR .049 ENGINES... DIE CUT PARTS-FORMED LANDING GEAR-SHARPE & NOTCHED LEADING & TRAILING EDGES, GOOD FLYER... FALCON 50 FOR .09, .19, ENGINES

BI HAWK

695

30" WINGSPAN, FOR .020-.049 ENGINES... PRECISION DROP OUT WOOD PARTS, FORMED LANDING GEAR-WHEELS & COVERING, STUNTS LIKE A MULTI!

TRI SQUIRE

1195

31" WINGSPAN, FOR .09-.19 ENGINE... SUPER SHARP DIE CUT PARTS, FORMED WIRE AND DURAL LANDING GEAR, FOR RUDDER AND ELEVATOR.

SCHOOLBOY

350

29" WINGSPAN, FOR .010-.020 ENGINES... REALISTIC ALL Balsa Balsa MODEL... RUBBER-SIMPLE EASY TO BUILD & FLY... FOR R/C OR FREE FLIGHT.

J3 PIPER CUB

995

54" WINGSPAN, FOR .09-.35 ENGINE... DIE CUT WOOD PARTS, SHARPE AND NOTCHED LEADING AND TRAILING EDGES, FORMED METAL COMB. SCALE

CHALLENGER

1995

60" WINGSPAN, FOR .29-.45 ENGINE... ALL WOOD PARTS CUT TO SHAPE... COIL SPRING STEERABLE... MORE GEAR, DESIGNED FOR MULTI R/C.

FALCON JR.

395

BI HAWK

695

TRI SQUIRE

1195

SCHOOLBOY

350

J3 PIPER CUB

995

CHALLENGER

1995

AMERICA'S HOBBY CENTER BEST BUYS

TUBES: 345, 354, XFI, XFY, 6007... REG. SALE

CRYSTALS: EA. 13.627, 16.995, 27.040, 27.089, 27.145, 27.195, 27.255... REG. SALE

FOAM RUBBER: 25¢

SUB MINIATURE: 198

ESCAPEMENT AND SERVO: 249

AMTRON: 249

GIANT MODEL BUILDERS CATALOG: 25¢

FIELD STRENGTH METER: 995

HOBBYIST SETS: \$4.99

FUSEAL: 50¢

R/C TERMINAL BLOCK: 225

NYLON ACCESSORY: 60¢

PENCIL BATTERY BOX: 25¢

R/C SOLDERING IRON: 169

MINI PLUG & JACKS: 15¢

DELUXE RECEIVER INSTALLATION KIT: 98¢

R/C PENNANTS: 25¢

MILLIAMPER METER: 50¢

SINGLEMATIC: \$14.95

BONNER TRANSMITTER SERVO: \$29.95

BONNER RE VARICOMP: \$9.95

DURAMITE SERVO: \$12.95

SUPER MULTI TESTER: 795

HOBBYIST SETS \$4.99

SET OF 1

R/C TERMINAL BLOCK 225

NYLON ACCESSORY 60¢

PENCIL BATTERY BOX 25¢

R/C SOLDERING IRON 169

MINI PLUG & JACKS 15¢

DELUXE RECEIVER INSTALLATION KIT 98¢

R/C PENNANTS 25¢

MILLIAMPER METER 50¢

SINGLEMATIC \$14.95

BONNER TRANSMITTER SERVO \$29.95

BONNER RE VARICOMP \$9.95

DURAMITE SERVO \$12.95

SUPER MULTI TESTER 795

BONNER SN ESCAPEMENT \$5.95

FOR SINGLE CHANNEL SETS-GIVES RIGHT & LEFT RUDDER MOTOR CONTROL...

BONNER RE VARICOMP \$9.95

DURAMITE SERVO \$12.95

SUPER MULTI TESTER 795

BONNER RE VARICOMP \$9.95

COMPOUND ESCAPEMENT FOR RIGHT, LEFT AND UP/ELEVATOR, USE SN ESCAPEMENT OR MOTOR CONTROL...

DURAMITE SERVO \$12.95

SUPER MULTI TESTER 795

DURAMITE SERVO \$12.95

SELF NEUTRALIZING, INCH WADBLE OR PROPORTIONAL CONTROL SYSTEM...

SUPER MULTI TESTER 795

GIANT MODEL BUILDERS CATALOG 25¢

#A63 128 PAGES PICTURES & DESCRIBES MORE THAN 40,000 ITEMS, MODEL AIRPLANE, RADIO CONTROL, DIALS & PLASTIC KITS...

128 PAGES PICTURES & DESCRIBES 2000 MORE THAN 40,000 ITEMS, MODEL AIRPLANE, RADIO CONTROL, DIALS, ACCESSORIES, ETC...

JUST SEND A 5¢ UNUSED STAMP FOR EACH OF THE FOLLOWING

- AV MODEL AIRPLANE PLASTIC & R/C
- RB HO MODEL RAILROAD
- SR MODEL CARS & SLOT RACING
- YB GENERAL HOBBYCRAFT

OVER 5,000,000 MODELERS KNOW IT PAYS TO BUY AT "AHC"

AMERICA'S HOBBY CENTER

1466L West 22nd St., New York, N.Y. 10011

AN INTERFERENCE RESISTANT RECEIVER

RECEIVER

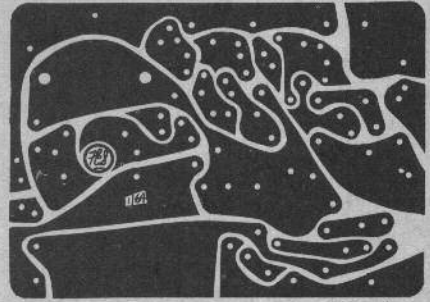
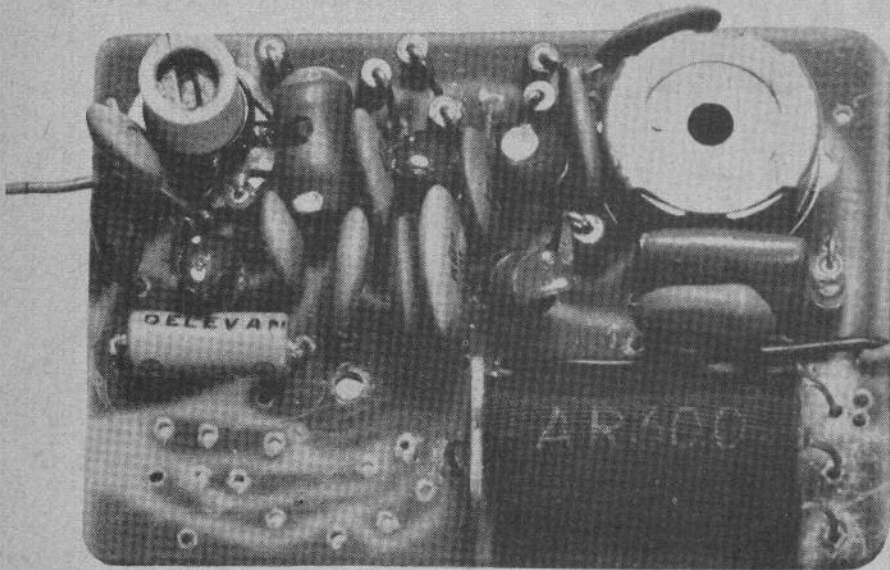


FIG. 4

NINE OUT OF 10 MODELERS IN ALL LOCALITIES WILL HAVE COMPLETE SECURITY FROM CBERS WITH THIS FINE, SUPER-REGEN CIRCUIT.

Editor's Note: This is a truly revolutionary receiver for radio control usage. Repudiating the accepted belief that super-regens cannot be selective enough to minimize interference, it was operated during a two-week test within 1000 feet of two CB base stations. Involving a number of new concepts in design, it is, moreover, easily modified to higher frequency allocations which may open up, if the AMA committee succeeds in its mission.

■ THE RECEIVER DESCRIBED in this article was developed during the period of AMA activity to spur action needed to examine present interference problems and seek new frequency allocations.

In the form described, it represents the author's best attempt to provide a secure (interference resistant) superregenerative receiver capable of holding its own in all but the most unusual interference conditions. For nine out of ten flyers, in all locations, it should provide complete security. Further, it is capable of performing with minor modification in any higher frequency allocation which may open (up to 80 mc). All transistors are rugged, reliable high-temperature silicon units having 200 mc gain-bandwidth products (f_t) and exceptional uniformity.

The detector, a fresh design, contributes in good measure to the overall performance of the unit. About five months ago the first "narrow" detector was developed by the author. By individually adjusting each transistor an operating bandwidth of less than 250 kc at 1000 μ v could be achieved with 500 kc bandwidth, the usual rule. Figure 1 repeats this detector, correcting errors in its first printing. The basic circuit is a common base Colpitts oscillator, biased common collector and quenched by a base leak to form a self-quenched logarithmic mode superregenerator. High operating "Q" is preserved by deliberate collector mis-match (relative to "power-match" optimum). The real benefit of this mis-match, however, results from the lowered collector current conduction angle. Contributing also to this smaller conduction angle is the base bias network which provides high turn-off current to reduce storage time.

In the latest detector, the oscillator is still a common base Colpitts. Common base operation assures the best possible use of the transistor's capability and, in this case, a capability to 100 megacycles with actual operation at one-third this frequency. The direct and quench frequency circuit is common emitter and employs

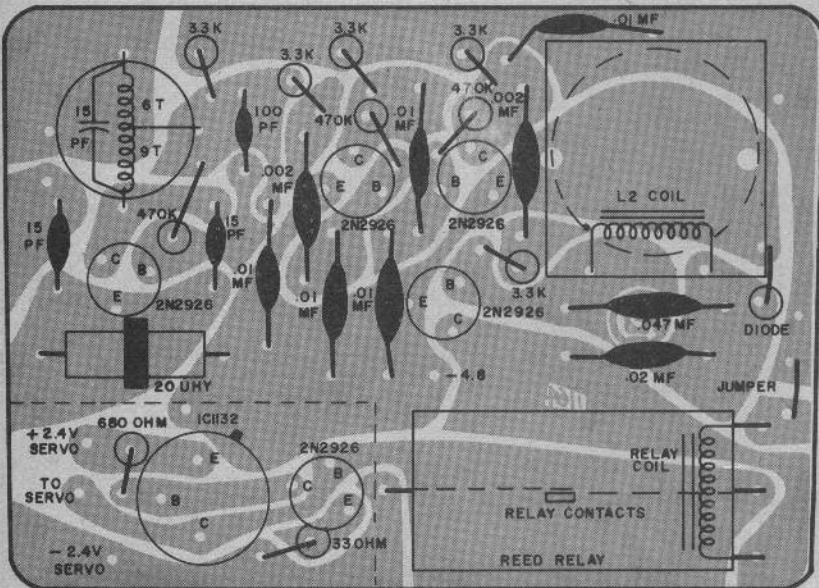


FIG. 5

By J. H. PHELPS


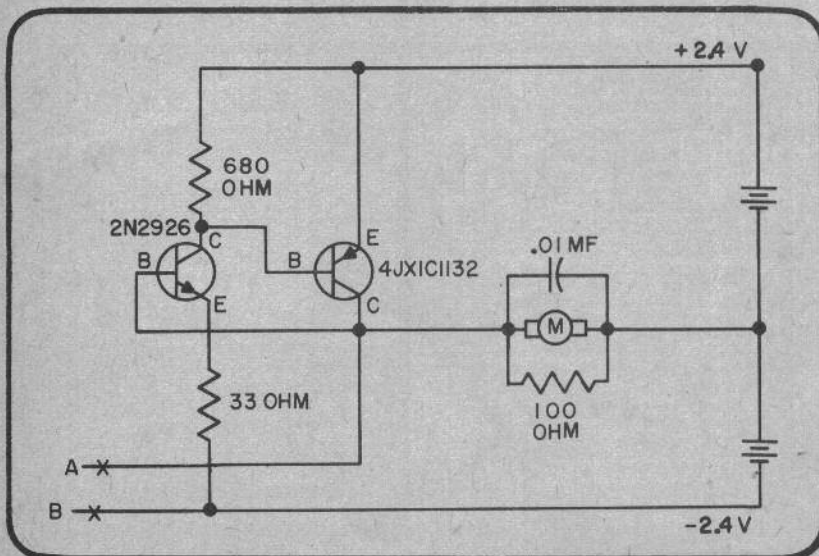


FIG. 3

FIG. 2

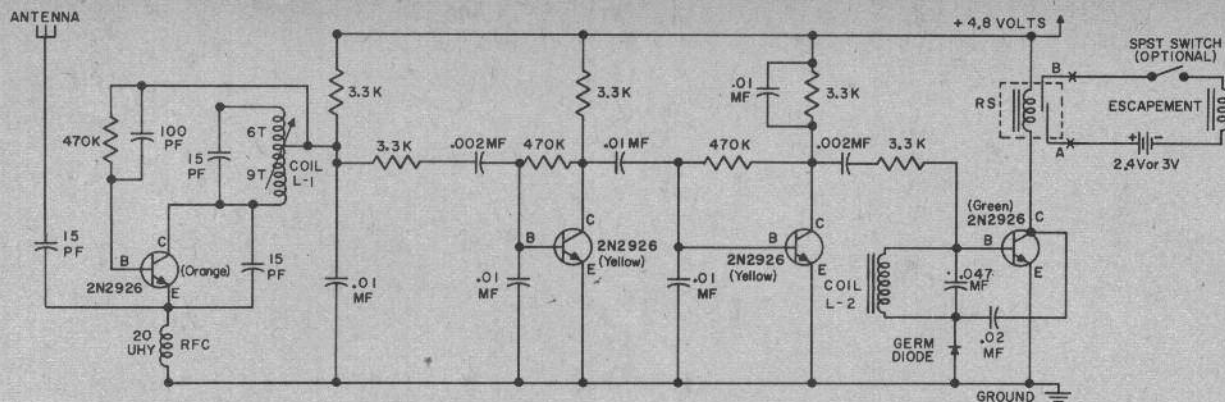


L₁-15 TURNS #30 AWG (SOLDEREASE) TAPPED AT 6T, PROPORTIONED AS SHOWN ON CTC SPC11-4L
 L₂- 50MH FERROXCUBE CUPCORE
 RS-OMEGA SALES HR 300 REED MAGNETIC SWITCH.
 * -.047 MF MYLAR CAPACITOR

negative current feedback to stabilize the operating point against temperature and transistor variations. This mode of operation was chosen because of the instabilities inherent in common collector operation, particularly when attempting to achieve high capture resistance and high recovery efficiency. Further, this mode gives an extra bonus in gain by virtue of its higher current and voltage gain at envelope frequency.

Common to superheterodynes and super-regenerators the phenomenon of capture is an important one and deserves explanation. The simplest way of viewing capture is to see it as an unwanted reduction of receiver sensitivity to the command signal caused by an unwanted signal. Thus an unmodulated Citizens phone station, transmitting no voice, can paralyze a receiver by de-sensitizing it. In the case of a superregenerative receiver it carries the quench PRF to its limit and no command modulation can recapture it. The detector used in this receiver will operate, in the air, at the same time as a standard base unit (1000 μ V meter) at a distance of 4000 feet while receiving command from a fully modulated carrier at 100 μ V meter. Stated another way, you need not worry about stations you cannot see if you fly in a large field with an unobstructed view of one mile in all directions. The remainder of the means to provide this security will be discussed in a bit.

Following the detector is a simple quench filter and two very stable high-gain audio amplifiers. Both stages not only stabilize temperature and transistor variations as they affect operating point but also they affect signal gain. Thus, the summer and winter "ranges" are identical for all practical purposes and no treacherous temperature "cliff" exists which can cause unexplained loss of control.

The last stage is the familiar reflex circuit updated to narrow bandwidth and eliminates resistor selection. Until this stage, all coupling capacitors have been .01mf. Here a .001mf capacitor is used to provide a sharp low frequency droop to help prevent subharmonic frequencies (contained in C.B. voice signals) from causing trouble. Further, the pull in frequency range of only several hundred cycles per second at 3.5 kc rejects noise and even female voice components. During a two week test, a receiver was operated within 1000 feet of two "lady operated" C.B. base stations. The receiver was connected to a "Veeder Root Counter" and only one false

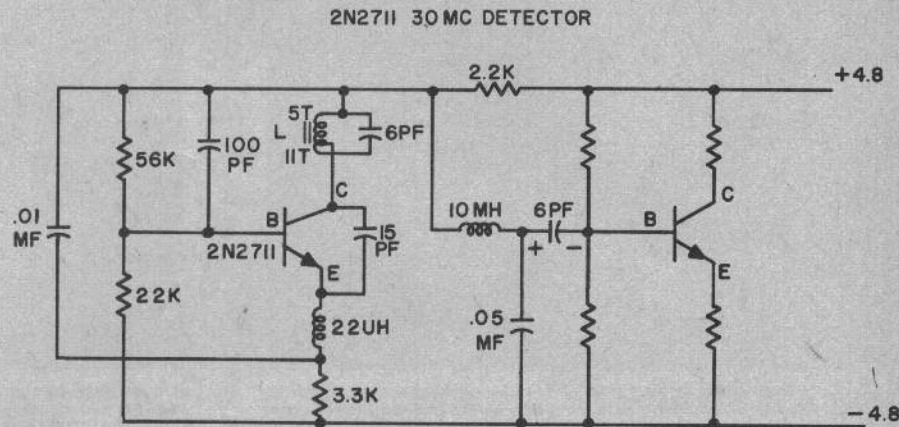

L = LS6 COIL FORM I6T NO. 28 TAPPED AS SHOWN

Fig. 1: This is the first narrow detector developed by the author. The circuit has now been finalized, as shown in fig. 2, which shows the reed switch hooked up to an escapement. The Omega reed will need to pull in at 10 ma or less; Fig. 3 shows the two extra transistors that are

required to make the SPST action of the Omega reed switch into an SPDT action for use by the proportional boys. Fig. 4 is a full sized PC layout base, which may be used for duplicating the receiver. Fig. 5 shows the layout of the component parts for the receiver. The material within the dotted line is the switching material.

count was rung up. This count occurred during the first five minutes of operation and is still unexplained.


Reviewing them, both the first and last stages team together to resist capture and ignore the noises of Citizens band stations. Incidentally, the same selectivity applies to brush and pushrod noise and this receiver has provisions to please the pulse-prop man. Since a reed switch and short coupling and smoothing time constants have been chosen, pulsing to 100 cp is easy. When used with the companion pulser, and feedback servos to be described in another article, superb proportional control results, free of temperature drift and as low in cost as a concerted effort can make it.

The printed circuit board has been laid out to incorporate a simple electronic switching device if more than the single-pole single-throw action of the reed switch is required. By simply adding two additional resistors and two transistors, an SPDT (single-pole double-throw) action will be had for operating devices such as the Mighty Midget and other actuators of this type.


This is one of the most versatile designs that has been presented, and it is hoped at a later date to use portions of this for multi channel and multi proportional receivers. When and if additional frequencies become available, we will present the conversion data.

Tuning this receiver requires a slightly different technique than one you may be used to. But once mastered, it is sure-fire.

Set your VOM meter on the lowest DC voltage scale you have (0-1, 0-3, 0-5). Clip the minus black lead of the VOM to negative, and the positive red lead to the base of the final 2N2926. Apply voltage to the receiver and turn on the carrier of the transmitter. Voltage will read approximately .25 volts with or without carrier. Tune the slug of L1 on the receiver for a dip. This will be about half of the idling current or about .125 volts. Now key any tone and the voltage should increase to .5 volts. Tune slug of L1 for peak. Adjust audio CPS of the transmitter for final peaking. This will increase the voltage reading to .75 volts or so. Adjust the receiver L1 and the transmitter CPS for final peaking at range. ■

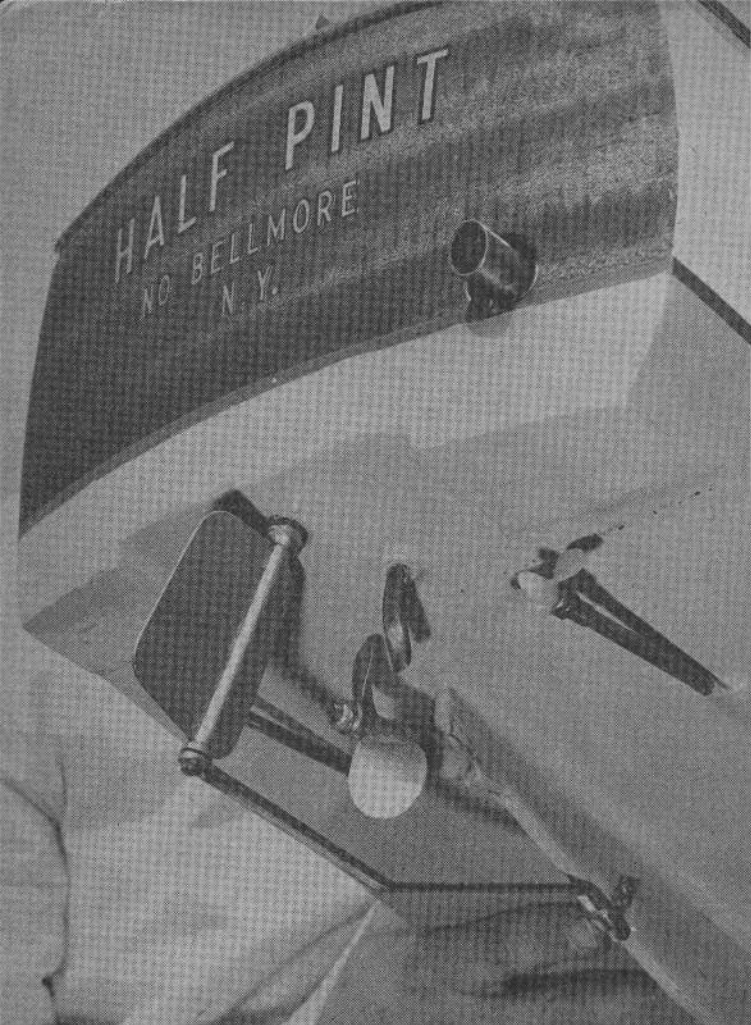

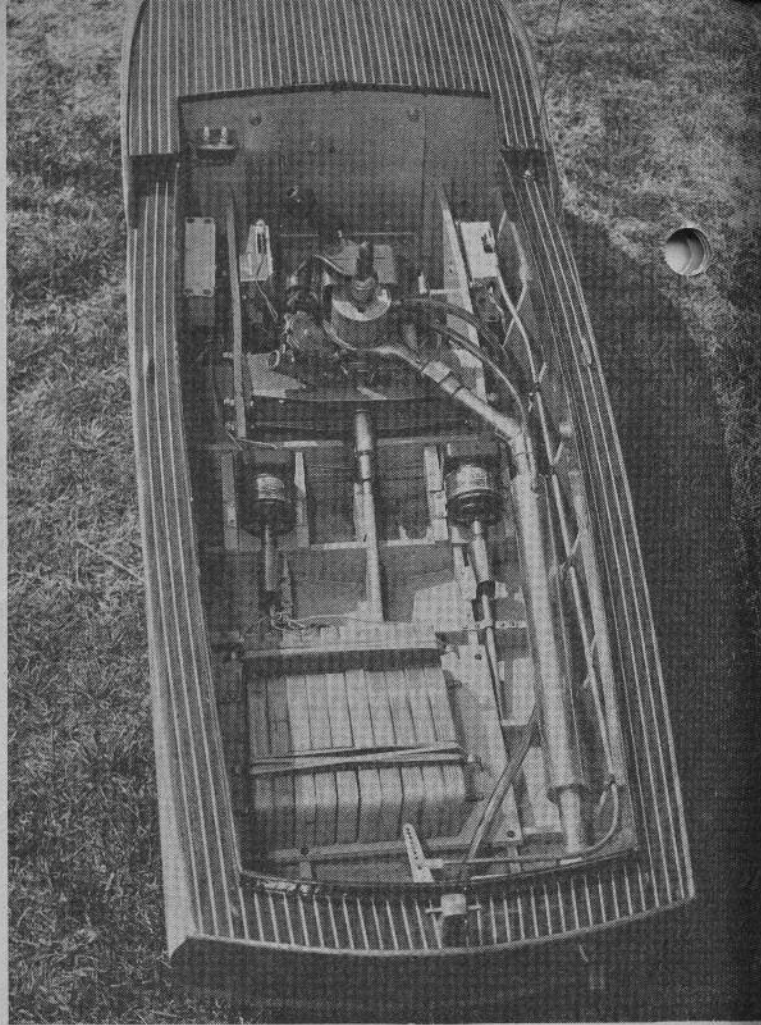
Prop for O & R is $2\frac{1}{2} \times 2\frac{1}{2}$ Octura aluminum, others $1\frac{3}{8}$ nylon by Sterling. Skeg and rudder homemade. Note water pick-up tube. Corner pads on hull were added to trim for more level ride at maximum.



O & R watercooled Compact sits on Octura mounts. Electric motors are Pittman Boatmasters. Three of four servos show, L to R: Electric motor switching, speed (choke was better than throttle), steering.



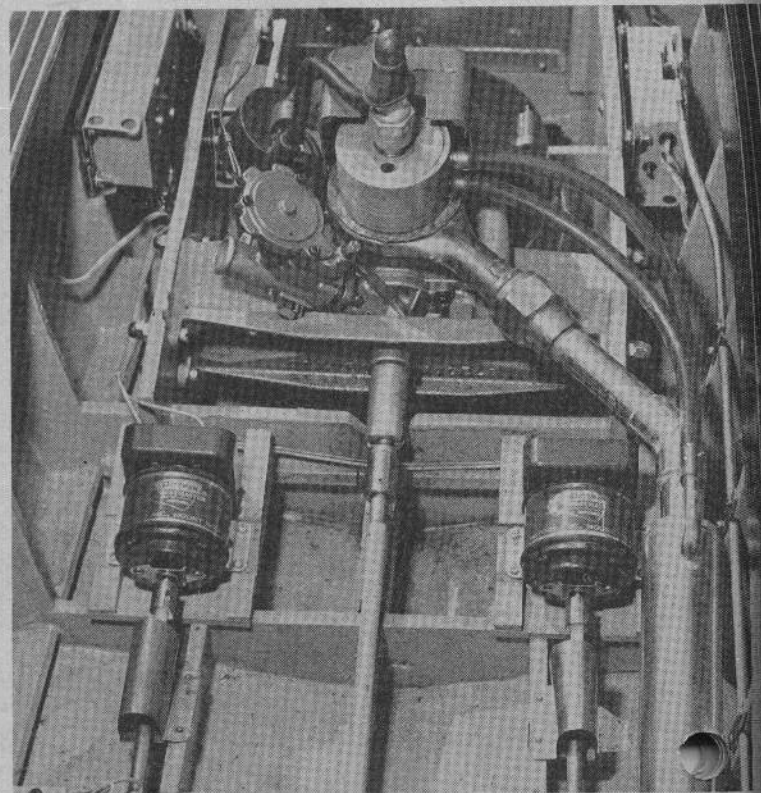Tank made from half-pint can—hence the boat name—clamped to a hatch which closes radio compartment under foredeck. Visual fuel-level gauge and quick-fill caps. Servos placed forward clear of spray.



Muffler is homemade from copper tubing; outside is $1\frac{1}{4}$ in. plumbing waste tube machined to fit. Waste water from jacket empties into muffler to keep cool. No baffles—muffler filled with fiberglass cloth.



This picture of Al with the Half Pint suggests the size and realism of the cabin cruiser. It is based upon a modified Sterling Corvette

hull with substantial fiberglassing for strength. Pull-starting works well with the inboard engine and good muffler keeps interior immaculate.



Half Pint

by AL SEIDENBERG . . . OUTSTANDING PERFORMANCE AND A UNIQUE CONCEPT OF CONTROL WITH 10-CHANNELS IN THIS CABIN

CRUISER MAKE THE PROJECT A SHOWCASE OF FEATURES FOR MARINE HOBBYISTS. AN O & R COMPACT YIELDS AN EXHILARATING TURN OF SPEED. IN EVENT OF ENGINE FAILURE, ELECTRIC DRIVE MOTORS CAN BE SWITCHED ON FOR A RETURN TO "PORT."


Servo (beamwise) just forward of gas engine cuts ignition by shorting. Moving servo arm engages microswitch mounted on top of servo. Deck is carefully planked—dark material rosewood. Note fuel filter.

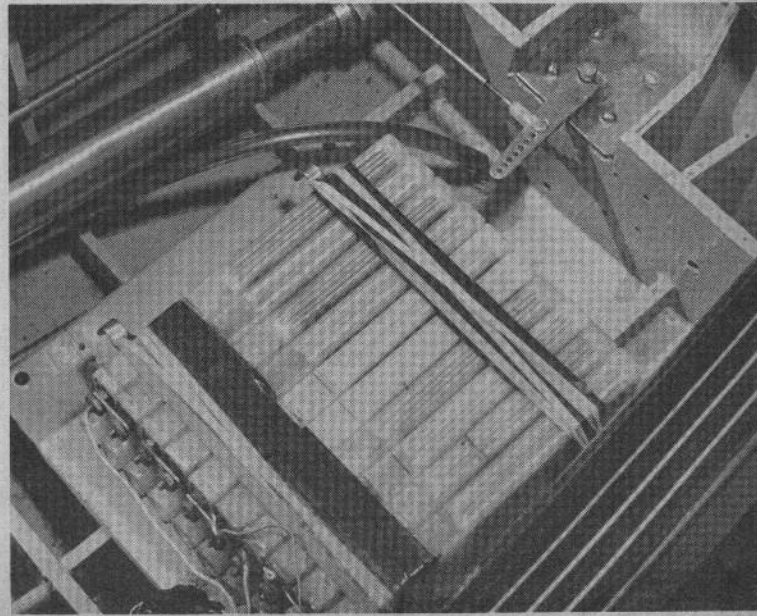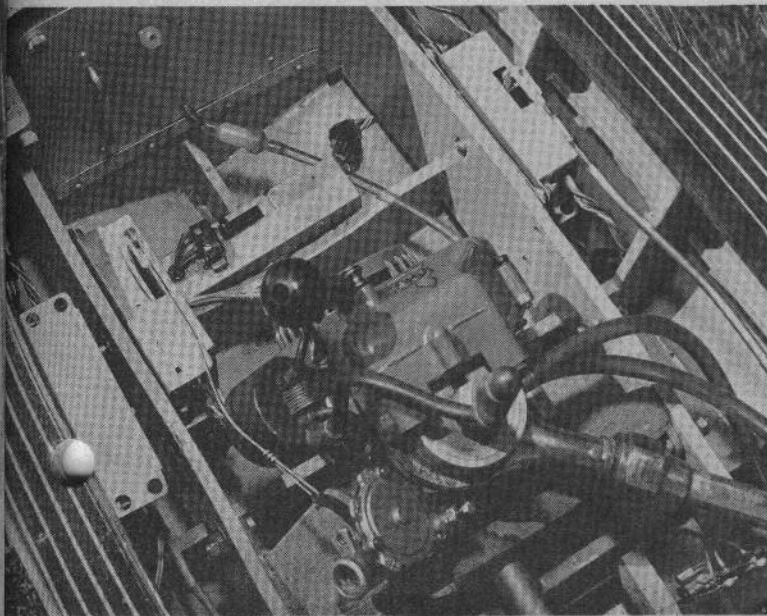Ten nickel-cad 4 amp/hr batteries are tapped so that five will supply 6 volts for receiver and servos, and five 6 volts to motors. A simple tiller is homemade. Steering via flexible cable through conduit tube.





The GEMINI Single-Channel TRANSMITE SWITCHER

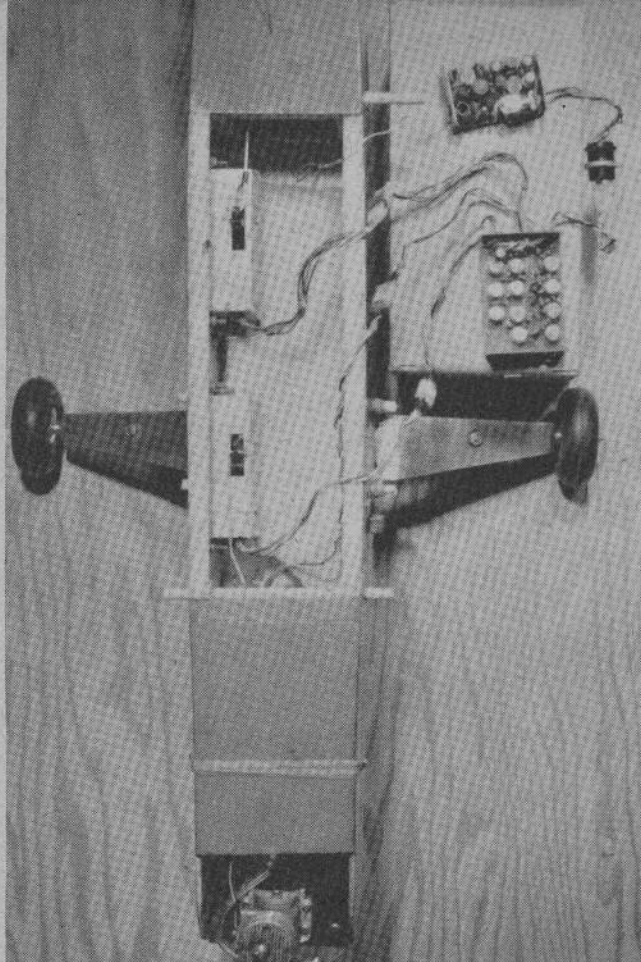Two hundred hours of engineering design and lab testing went into this single-channel system— it provides reed-like operation of the Transmite for rudder and three-position motor control with a second Transmite. Offered to a single-channel flier is extreme reliability and, for some, an economical entre to multi.



Engine and rudder servos mount in tandem on right side of author's craft. Switcher and receiver are shown exposed.

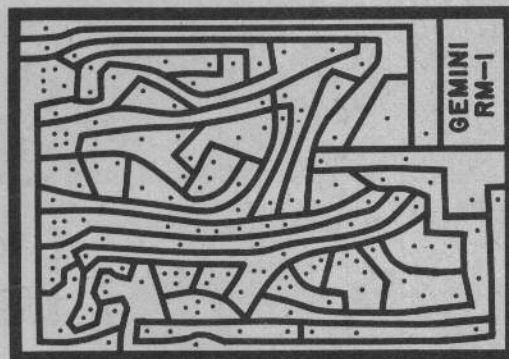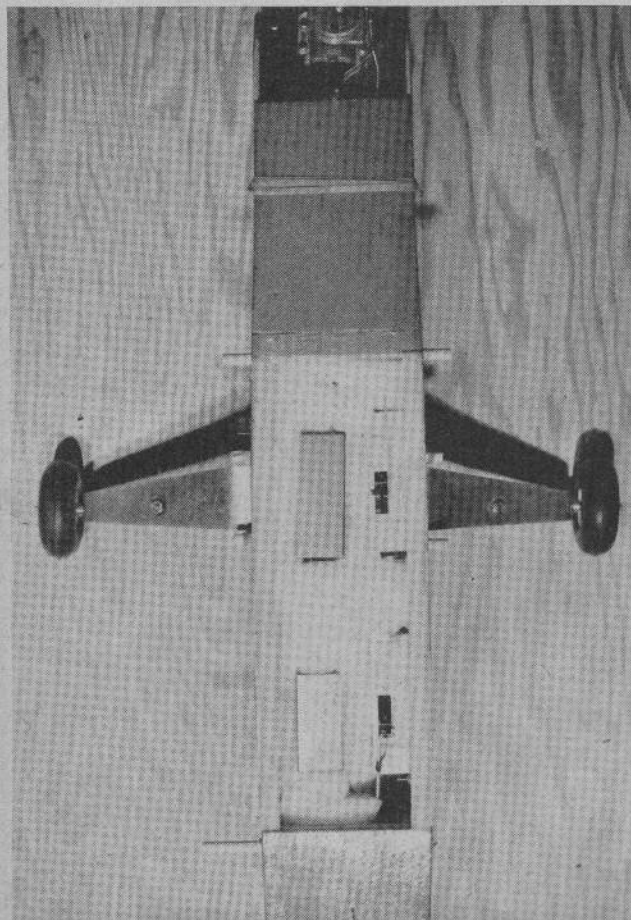Below: In this installation the switcher is placed in the forward position, receiver aft—and surrounded with foam.




AFTER EXPERIENCING NUMEROUS difficulties in obtaining reliable operation from the simpler forms of single-channel actuators, and particularly in finding a suitable engine throttle actuator, I decided to try doing something about the situation. Reliability of the control system and use of existing single-channel transmitters and receivers were the most important considerations.

The highly regarded Bonner Transmite multi servo was selected and its circuitry studied for signals which could be used with digital (on-off) logic circuitry to obtain the controls desired. The Gemini switcher is the result of over 200 hours of engineering design and laboratory testing. Gemini switchers have totaled over 200 successful flights during the past year. A Gemini switcher controlled aircraft placed eighth in Rudder-only Open at the 1962 Chicago Nationals.


Gemini switchers are specifically recommended for the flyer with single-channel equipment who is planning to "go multi" eventually, but needs a reliable single-channel system now. The Bonner Transmites used with the Gemini switcher may be converted at any time for multi operation.

The Gemini RM-1 (rudder-motor) switcher provides fully reliable control of two Bonner Transmite self-neutralizing multi servos for positioning the rudder and the engine throttle of a single-channel radio-controlled miniature aircraft or boat. As with "bang-bang" multi, the rudder servo can be pulsed left or right for smooth turns. Full rudder throw is available when desired and four pounds of thrust is available for operating a steerable nose gear. The rudder travels only a little toward right before going left. The engine servo gives three-speed engine control and can be changed from one speed to any other speed during a single control sequence.

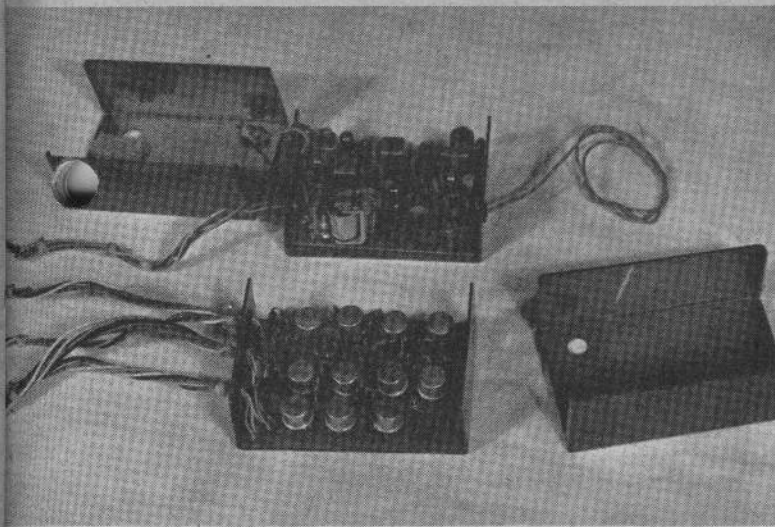
Any single channel transmitter and relay receiver can be used without modification. Simple modifications are required



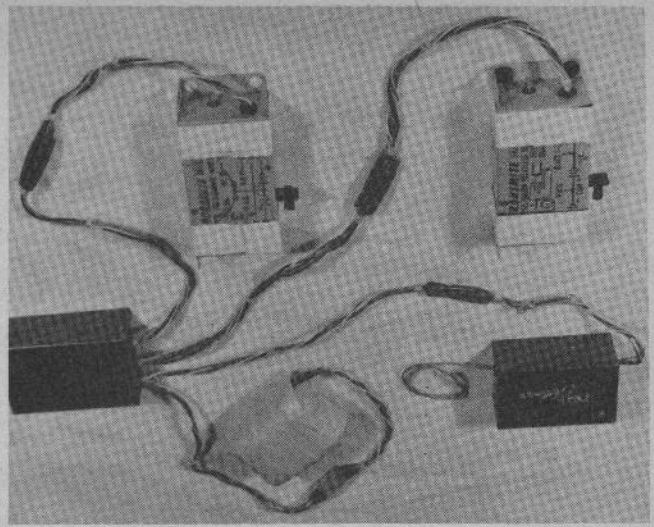Receiver, top, and switcher with covers removed. Any single-channel relay receiver, transmitter may be utilized.



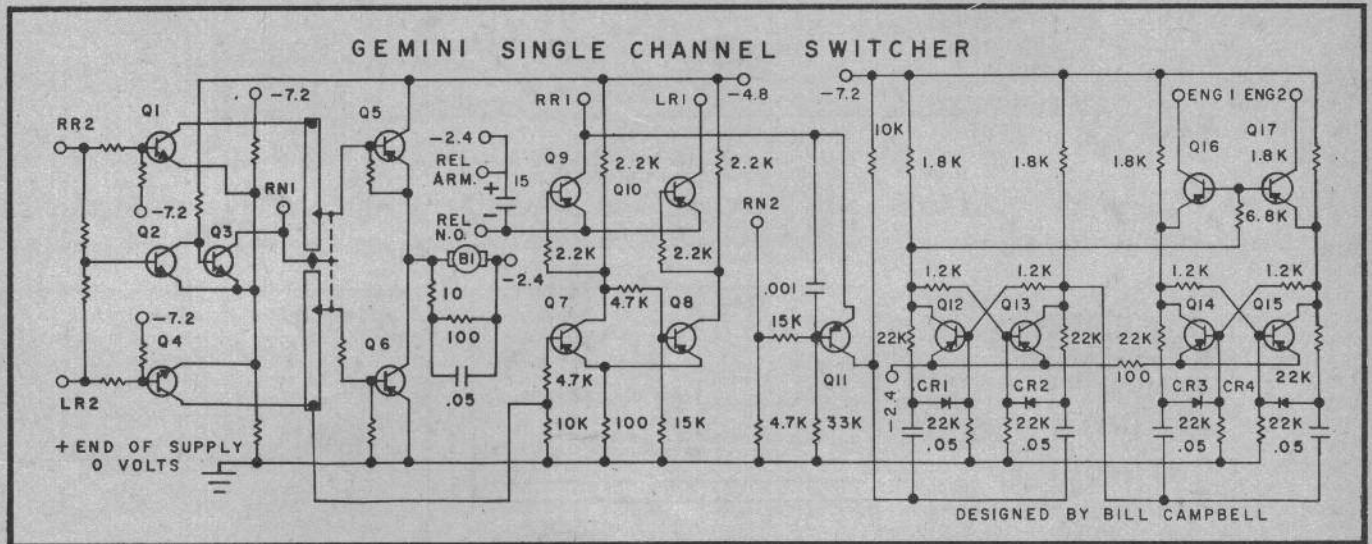Complete system with battery pack is readily removed for checking. Tape wrapping on servos a recommended procedure.



on the Transmite servos. Transmitter keying is similar to that for a compound escapement.

Flying the Gemini Switcher: The Gemini switcher controls a multi servo and must be flown with this in mind. As with multi, smooth turns are accomplished by giving a series of short commands (pulsing) to make the turn. The rudder servo has a longer transit (travel) time than an escapement, so controls must be released a little earlier than with an escapement to prevent overshooting. This is the first thing a multi flyer learns.

Transmitter keying is simple, but as with escapements, careful timing is important.

With "all systems go" depress the transmitter key. The rudder servo will run to right and remain there until the key is released. Release the key and the rudder servo will return to neutral. When pulsing short rights, allow time for the rudder servo to return to neutral between pulses. To key a left, depress the transmitter key and drive the rudder servo far enough toward right to give you time to release the key (which starts the rudder servo back to neutral) and then again depress and hold the key before the rudder servo has returned to neutral. The rudder servo will now drive on through neutral and go to left and remain there as long as the key is held. Release the key and the servo will return to neutral. With a little practice, lefts can be keyed with only a slight right rudder movement. Lefts are most easily insured by driving the rudder servo toward right for twice the time it takes you to release the key and then depress again the second time for the left. Pulsing smooth lefts requires a little more practice than for rights since double keying is required. This can easily be mastered.

The engine-speed sequence is from low to medium to high, to medium to low, etc. For engine speed changes, key the rudder servo to left far enough that you can then release the key (which starts the rudder servo back to *(continued on next page)*)


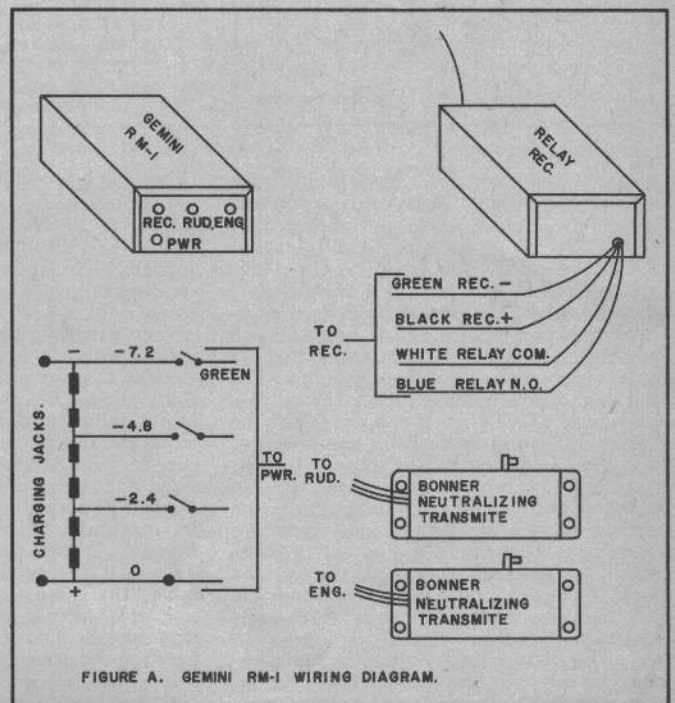


FIGURE A. GEMINI RM-1 WIRING DIAGRAM.

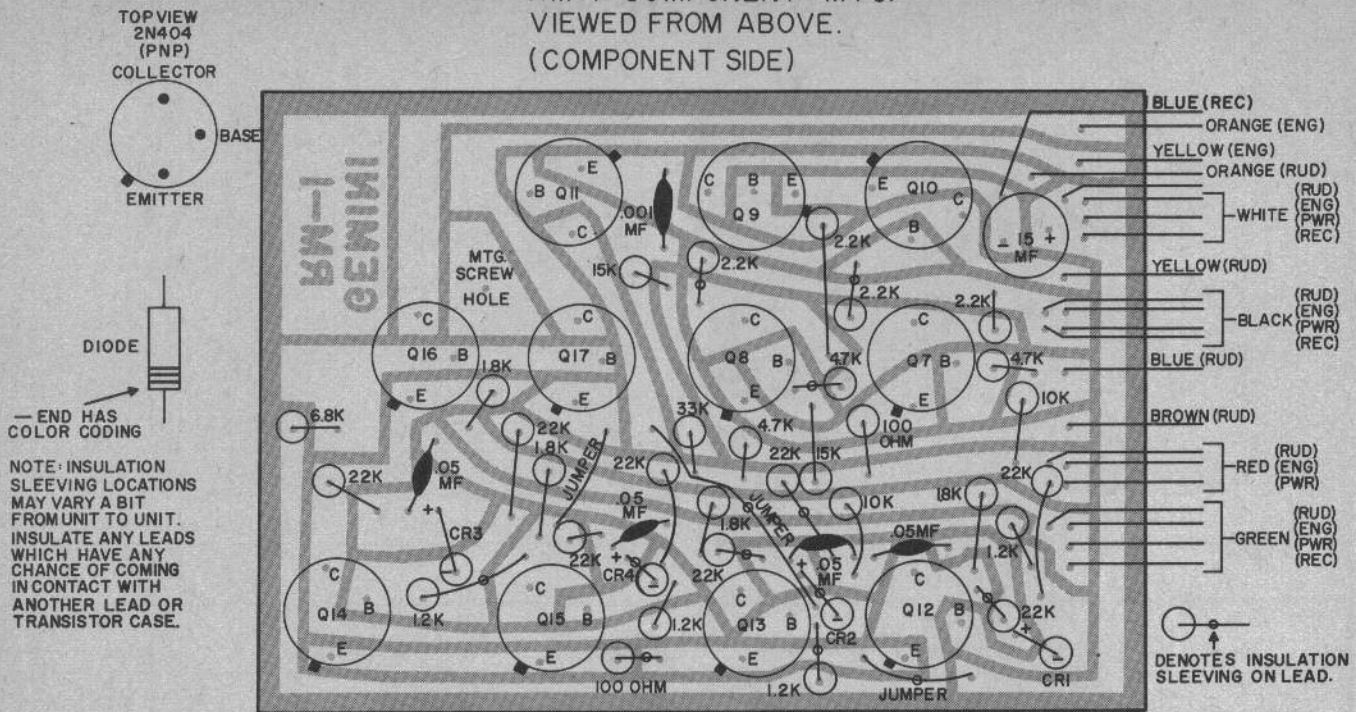RM-1 COMPONENT MTG.
VIEWED FROM ABOVE.
(COMPONENT SIDE)



RECOMMENDED ASSY. SEQ.

- 1- ALL TRANSISTORS: TRY TO LOCATE TO CLEAR OTHER NEARBY COMPONENTS AS MUCH AS POSSIBLE.
- 2- THE THREE JUMPER WIRES
- 3- CERAMIC CAPACITORS
- 4- RESISTORS, DIODES, AND ELECTROLYTIC
- 5- HOOKUP WIRES

FIGURE G.

THE GEMINI
SINGLE-CHANNEL
TRANSMITE
SWITCHER
CONTINUED

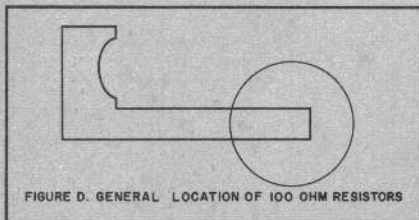


FIGURE D. GENERAL LOCATION OF 100 OHM RESISTORS

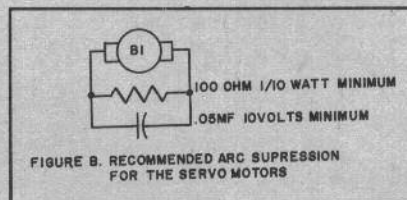


FIGURE B. RECOMMENDED ARC SUPPRESSION FOR THE SERVO MOTORS

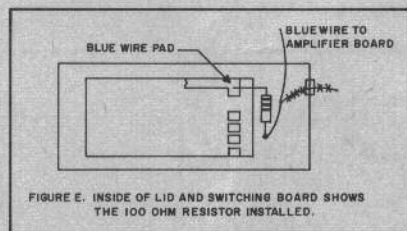


FIGURE E. INSIDE OF LID AND SWITCHING BOARD SHOWS THE 100 OHM RESISTOR INSTALLED.

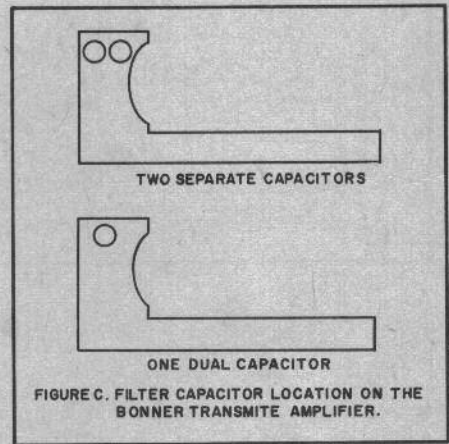


FIGURE C. FILTER CAPACITOR LOCATION ON THE BONNER TRANSMITE AMPLIFIER.

neutral) and then pulse it once for each in-sequence engine speed change desired before the rudder servo has returned to neutral from left. Each pulse will advance the engine speed one position. One, two, or three pulses may be keyed as desired.

Installing the Gemini Switcher: Four separate color-coded wire cables exit through grommets from the switcher RM-1 case.

1. The power cable contains four wires and runs through the switcher to the battery pack. Three of the wires must be switched. See Fig. A for color coding.

2. The receiver cable supplies 2.4 volts, if required, for a 3-volt receiver. It also contains two wires which connect to the receiver relay normally open and armature (common) contacts. See Fig. A. If other than a 3-volt receiver is used, simply tape back the green and black wires and use only the blue and white wires which connect to the receiver relay.

3. The rudder and engine cables color code directly to the rudder and engine servo cables. The yellow and orange wires

in the rudder servo cable cannot be reversed to change the direction of rudder throw. If necessary, the rudder pushrod should be moved to the other side of the rudder. The Gemini switcher puts a signal on the yellow wire to the rudder servo when right rudder is keyed. The direction of servo travel when a signal is on the yellow wire is marked on the cover of the Bonner Transmite servo case.

Batteries: Six series-connected 450- or 500-MAH minimum capacity nickel cadmium batteries must be used for the power supply. Fig. A shows the battery connections and wire color coding to match the Gemini power cable. Solder all connections for maximum reliability.

Bonner Transmite Servo Modifications: Two self-neutralizing Bonner Transmite multi servos must be modified as follows:

1. Both servos must have arc suppression installed to prevent any interaction between the servo motors and the receiver. Recommended arc suppression is shown in Fig. B. Goo (a rubber cement) or epoxy

the components to the motor case to prevent their breaking loose from vibration. Solder the leads directly across the motor-brush covers being careful not to over-heat the nylon motor case. The arc suppression need not be removed if the servos are ever used in a multi system. No further modification is required to the engine servo.

The rudder servo is further modified as follows:

If no engine servo is to be used with the Gemini switcher, step 2 may be omitted. Step 2 is absolutely essential, however, when an engine servo is used with the RM-1.

2. Remove the amplifier board from the servo case. (See R/C Modeler, November 1963, "Probing the Transmite Servo.") Unsolder and remove the filter capacitors located approximately as shown in Fig. C. On the newer Transmites both filter capacitors are located inside one container and have three leads to be unsoldered. Keep the filter (continued on page 28)

PROPORTIONAL CONTROL

By PHIL KRAFT

IN PERSPECTIVE

Caught between consumer demand for proportional multi and the high cost of making what he considers good equipment, the manufacturer shows a growing concern.

TODAY'S MAIN TOPIC of conversation among enthusiasts is, of course, proportional control. A whole new vocabulary of exotic words is becoming part of the vernacular; i.e., feedback, logic, digital, phase-shift, glitch, subcarrier, spike, etc. It would seem that the long awaited era of proportional control is finally here, or is it? Is this emphasis on expensive, sophisticated control systems good for a hobby? I believe it is time to re-evaluate this "new era" to try to gain a reasonable perspective.

There are no "experts" on proportional control. The field is too complicated and too new to make positive statements regarding methods and systems. However, I believe the experience of those in our organization is such that perhaps we can draw definite conclusions pertaining to certain aspects of the overall picture.

For the past two years we have had the pleasure of working with Jerry Pullen towards the development of a commercial proportional system. Pullen was the first to fly a true feedback proportional control system some six years ago. His early systems were largely responsible for creating West Coast interest in proportional control. Recently, Don Mathes became part of our company. His proportional control experience dates back to preliminary work on the early Space Control System. In the past three years he has worked on the prototype development and final production of the Digicon System. Mathes with Doug Spreng originated the digital concept of proportional control. It is now being initiated by other manufacturers. Based on the experience of these men and two years of concentrated effort on our part, I believe we have reached some valid conclusions. However, before continuing this discussion of proportional control as applied to our hobby, consider the history of other hobbies and sports.

Before the war and immediately after, hot-rodding was, if somewhat ill-famed, a great sport. The average enthusiast with skill and a few hundred dollars could compete at the "Lakes" or drag strips. Today, only those professionals with commercial sponsors stand a chance in competition. There was a time when one could climb into an MG-TD with his girl friend and drive to the sports car races to compete. Perhaps he might bring home a trophy. Today, sports car racing is confined to factory teams, millionaire department store heirs, or Texas oilmen. Go-carting started with lawn mower engines on crude frames. Soon, twin engines of special design and several thousand dollars were mandatory. This sport died as quickly as it grew.

Is there a parallel between this sport and radio control? I feel there is. Fortunately, however, I believe that 99 out of 100 radio control enthusiasts are primarily interested in flying for fun, not for competition. Therefore, let's stop deceiving our-


selves about proportional control, and realistically evaluate our sport in terms of control systems best suited to the average enthusiast. In this light, proportional control is not at this stage of development for the average model builder, simply because of cost. Also, our experience indicates that this picture is not likely to change in the near future. Our multi-channel reed systems have developed to an exceptional standard of reliability. Yet many so-called "experts" are proclaiming reeds to be obsolete. We disagree. With our proportional system finished from the electronic design standpoint, we at Kraft R/C are concentrating on development of our reed system line, because we believe that reeds are still the most practical approach to flying from the standpoint of cost and reliability.

There are many misconceptions regarding proportional control, probably because, in our opinion, there are no true proportional systems in production at this writing. Some say that with proportional control, it is hard to land the aircraft, more difficult to do consecutive maneuvers on heading, etc. This is simply not true. With true proportional controls, flying becomes a matter of the pilot's skill and handling of the aircraft. The degree of precision that can be attained is beautiful to watch. There is no question, assuming equal ability, the reed flyer cannot compete with true proportional flyers. Note, however, the emphasis on true proportional control. A proportional system which does not respond or track well, or is subject to dead spots, neutral drift, etc., is harder to fly with precision than a reed system. It is also true that a good reed flyer will score more contest points than an average proportional flyer no matter how good the proportional system.


Since the proportional control system is obviously superior to reeds for contest use, why can't we produce one at reasonable cost? Actually, the answer should be obvious. The average 10-channel reed system sells for approximately \$400.00, complete and ready-to-install. Our reed transmitter has six transistors, our proportional transmitter has 23 transistors and 11 diodes. The reed transmitter has lever switches for control; the proportional transmitter has a relatively complex control stick operating control potentiometers. The reed receiver has six transistors and a reed bank; our proportional receiver has 28 transistors and 34 diodes. The reed servo has seven transistors and a switch plate. The proportional servo has seven transistors and an extensive feedback potentiometer element. These comparisons, naturally, do not take into account the vast difference in other necessary components.

Our reed system with servos takes approximately seven and one-half manhours, including set up, to complete. The proportional system takes approximately 40 hours. Because of the proportional system's complexity, (Continued on page 27)

R/Cing the Bulldog Tank

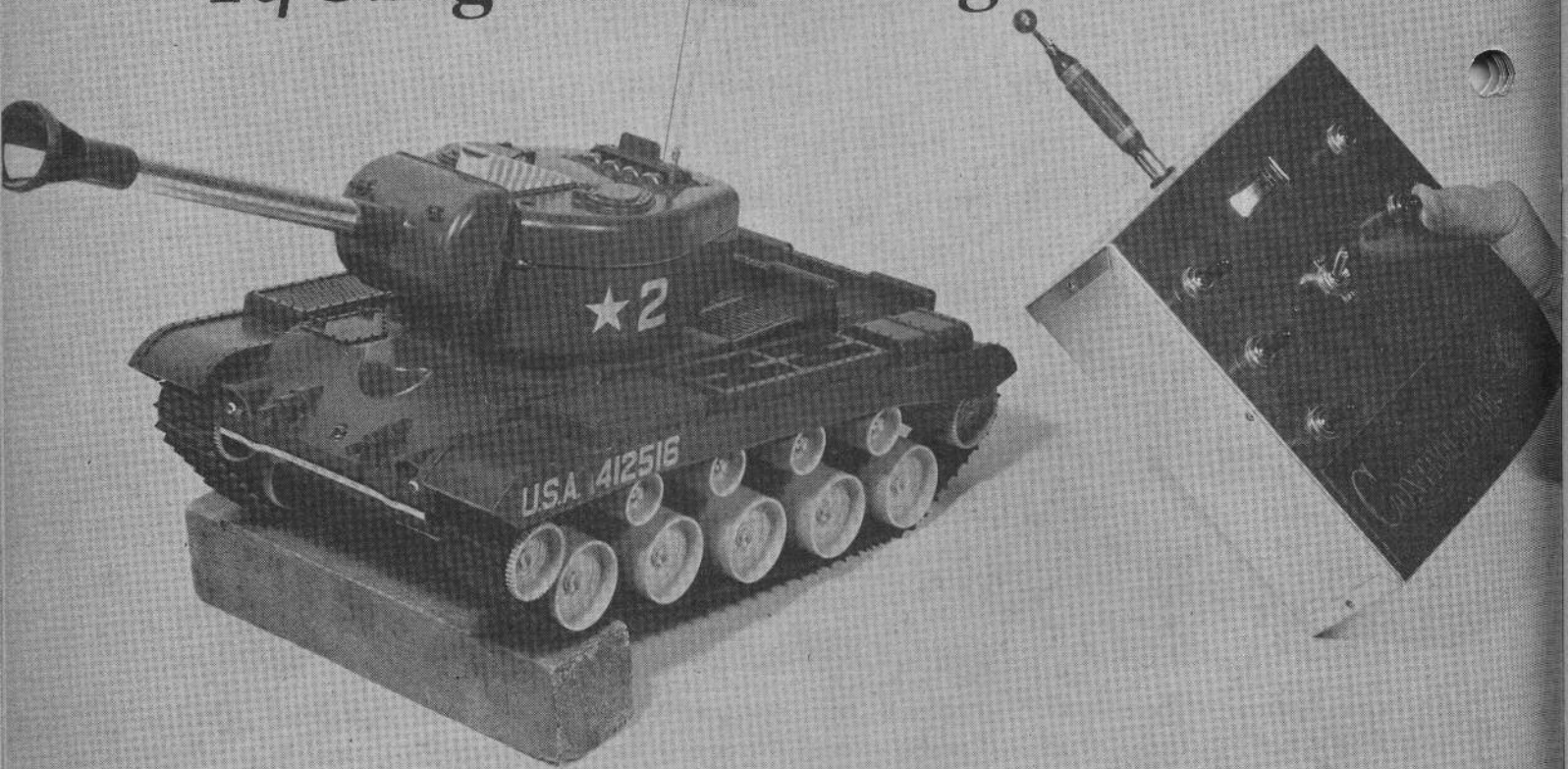

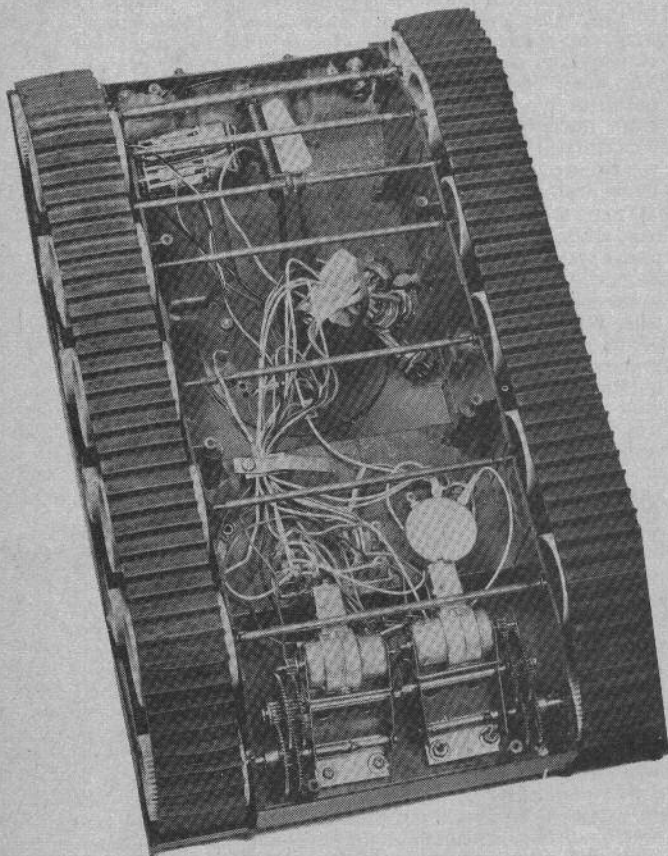
The large size of this realistic tank is evident from a comparison with the 10-channel transmitter. Note the vertical whip.




The cannon-cocking spring, and cocking lever just below it, show at top of picture. Receiver, nickel-cad pack, metal tank bottom not shown. Right: Pot—above right motor—used to adjust the speed of faster motor for straight running.

How Phil Canterra and Kern Bowyer installed radio gear in two toy Army tanks and then fought tank battles with guns which work. It takes six-channel control—and the ideas adapt to all tracked vehicles.

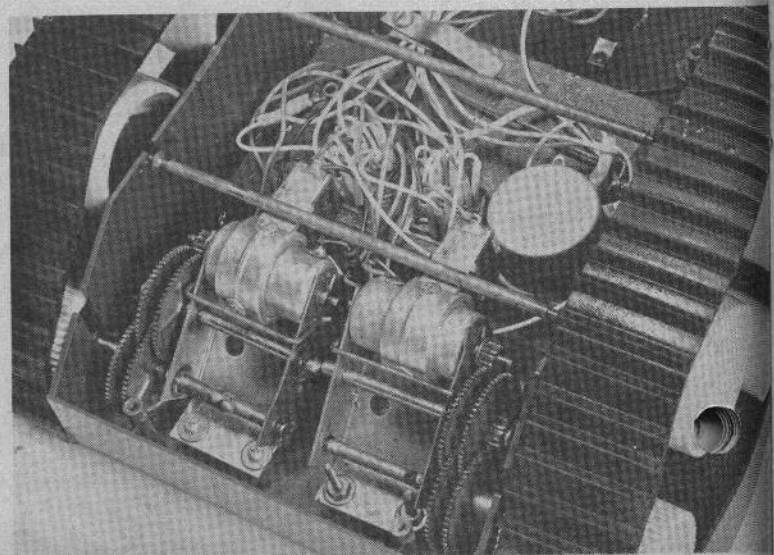■ OFFERING MANY UNEXPLORED and interesting possibilities are the many amazingly realistic motor-driven toys available from supermarkets and toy stores, which can be easily converted to radio control. This Remco U.S. Army Bulldog tank is an outstanding example. Actually, all these non-aircraft projects, including electric-powered boats, pose basically similar challenges.



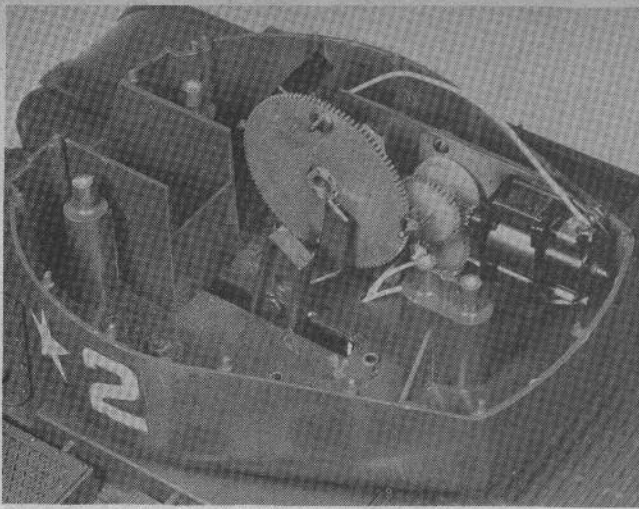

Cocking motor assembly Bonner servo parts except for large gear which moves cocking lever. Gun recocks automatically.

When high-drain drive motors are involved some suitable means must be found to prevent overloads from damaging relay contacts, transistors, etc. in receivers and actuators, usually accomplished, as in this case, by switching relays. Tracked vehicles, such as dozers, tractors and tanks, depending upon separate drive to each track in order to steer, require splitting the drive axle, with each half gear-driven by its own motor.


Canterra and Bowyer first demonstrated their pair of Bulldog tanks at the Bisons, DC/RC and Weak Signals conferences in 1960. Phil and Kern graciously made this information available to GL after digging out one remaining forgotten tank which was rehabilitated for these pictures—the radio, etc. being replaced after some hasty picture making.

"In late 1959, when the weather was closing in on us," Kern recalled, "and flying was stopped, Carl and I looked around for a winter project. After visiting a number of toy stores, we settled upon the larger of two Remco tanks. They appeared large enough to hold all the gear and batteries that would be required and offered the possibility of full forward and reverse, left and right operation, in addition to (Continued on page 26)




This view shows special cocking motor metal mount and micro-switch, to right of big gear, which shuts off motor when gun ready to fire. To rear of turret are four motor-control relays, switches and an antenna pin-jack on rear decking.

CIRCUIT DIAGRAM FOR BULLDOG R/C TANK


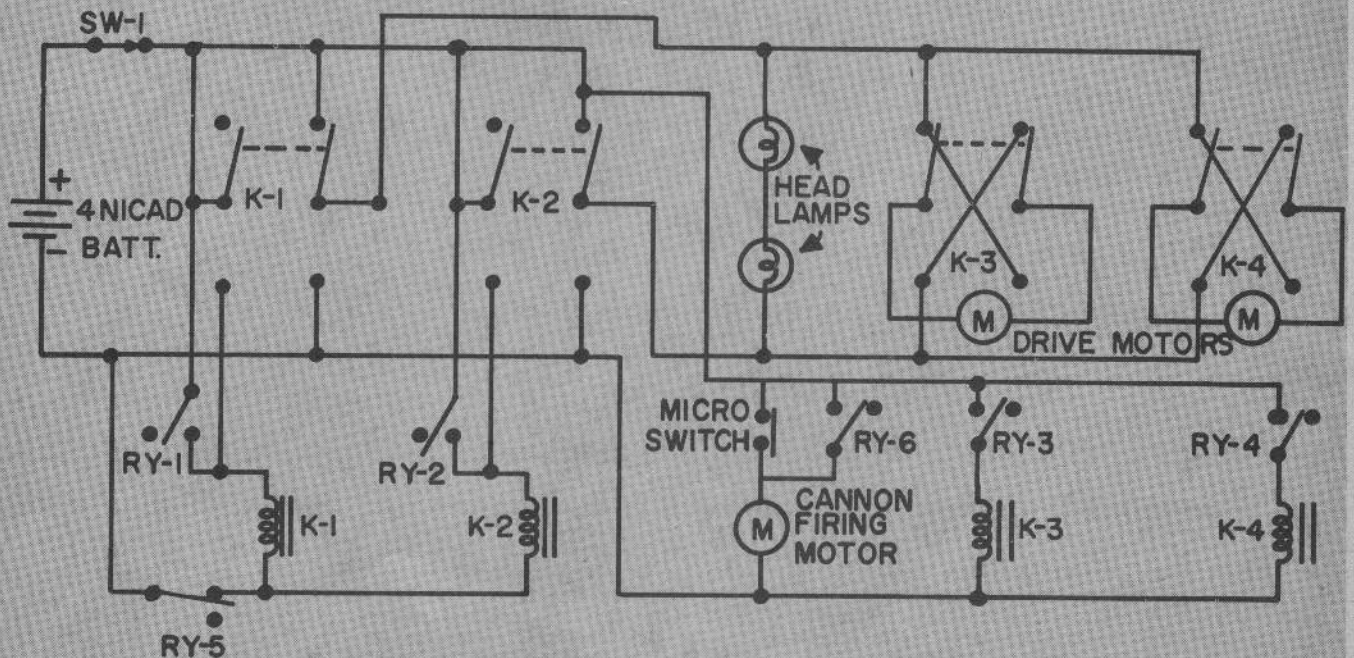


Receiver power wiring not shown; depends on unit. All relays shown in un-energized position. Key: K-1, forward drive relay; K-2, reverse drive relay; K-3, left turn relay; K-4, right turn; Sw-1, main power switch; Ry-1, down elevator rcvr.

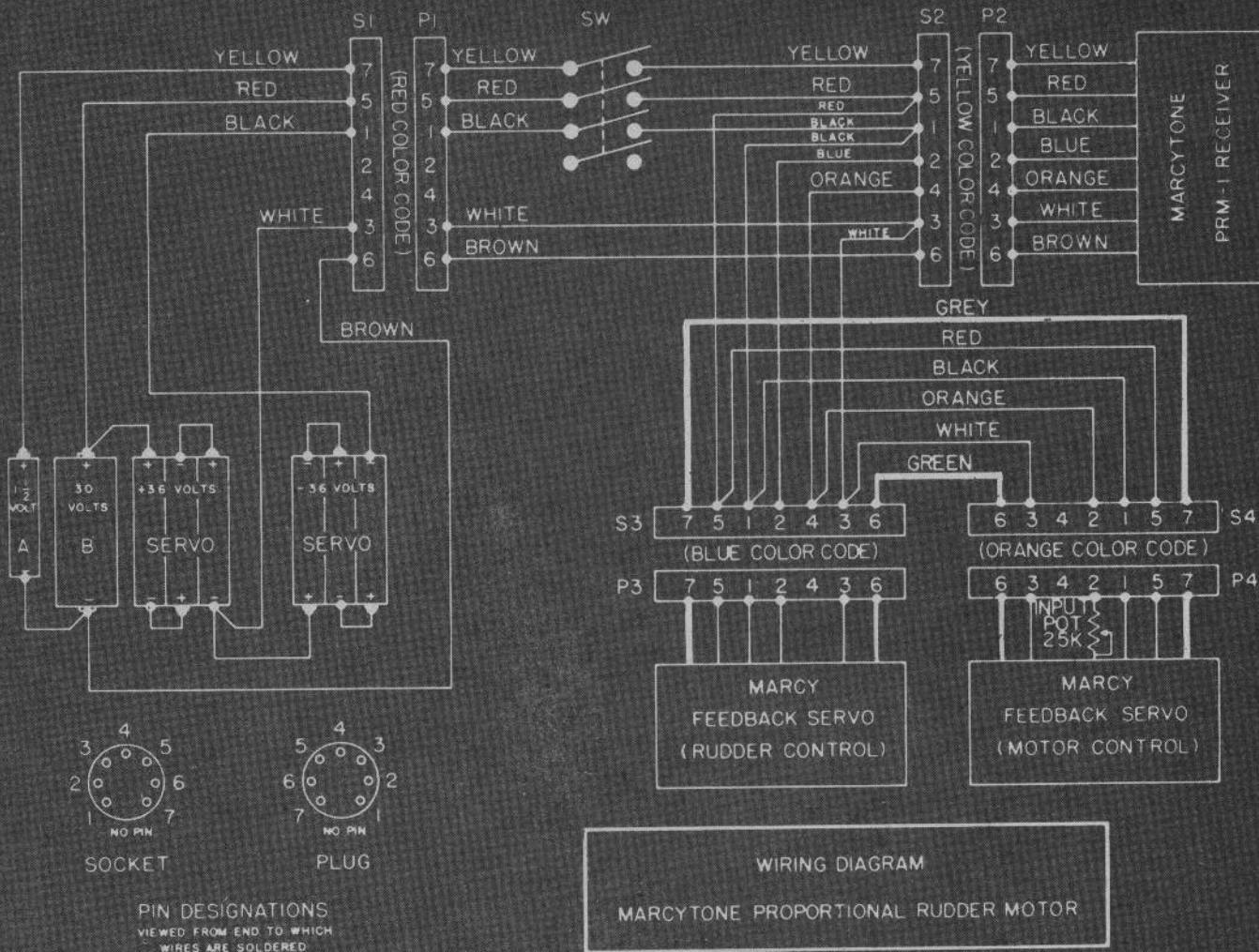relay, starts tank forward; Ry-2, up elevator rcvr. relay, starts tank in reverse; Ry-3, left rudder relay for left; Ry-4, for right; Ry-5, low-motor rcvr. relay stops tank; Ry-6 high motor, fires cannon (by starting cocking motor).



IMPROVING The Marcy PRM-1 System

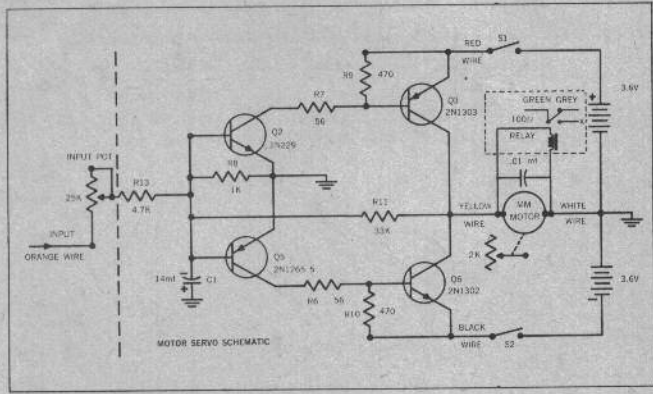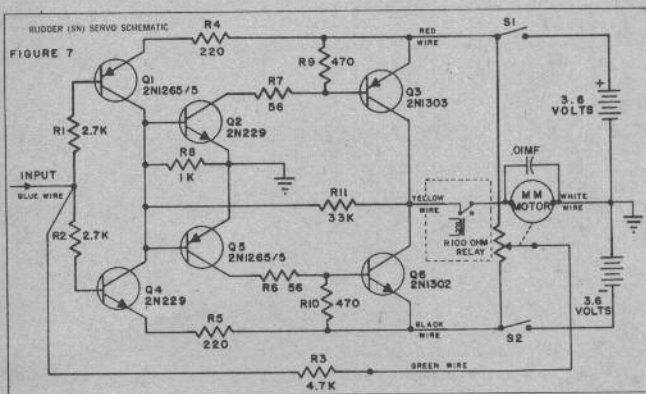

The addition of 100-ohm relay provides for simultaneous control function and eliminates objectionable cycling or partial cycling in rudder when motor is commanded.

BY PUTTING A 100-OHM RELAY of the Deans type across the Marcy Mighty Midget motor used for motor control in the Marcy PRM-1 System, and wiring in its contacts to the Mighty Midget rudder servo, performance of the system can be improved.

With the addition of this relay and its contacts in the servo circuit, the current is immediately taken off of Mighty Midget rudder motor when motor control is commanded.

Even if the rudder is in a turn and motor control is commanded, the rudder will retain the degree of turn at the time of command. This affords simultaneous function and improves

the performance considerably. It also gets rid of the objectionable cycling or partial cycling that has been an inherent quality of the rudder servo on motor command.


There is a slight quick nervous jump of the rudder servo with this relay, but it has no appreciable deflection.

There is room on the motor control-servo PC board to mount the 100-ohm Deans relay, and the heavy wires (see wiring diagram) show how the relay connections may be made on pins 6 and 7 of the two plugs and sockets for both motor and rudder control.—*Marcy Inkman*





...R/C JAY

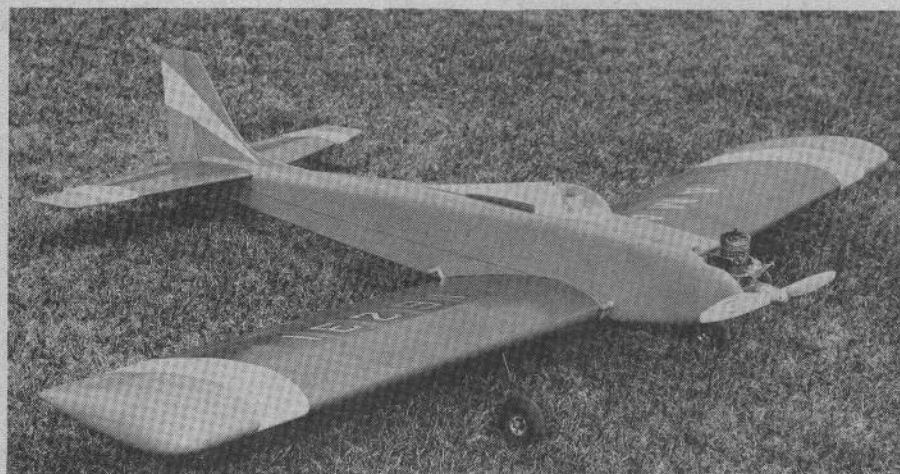When this picture was taken the ship had just completed its 200th flight. Bob specialized in all forms of proportional.



The two-wheel gear, in this instance, presents no takeoff or landing problems.

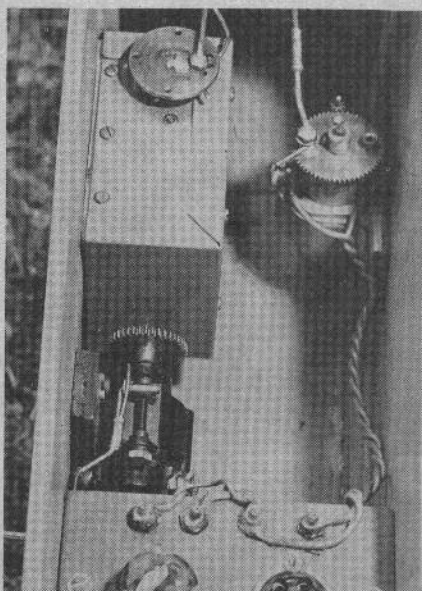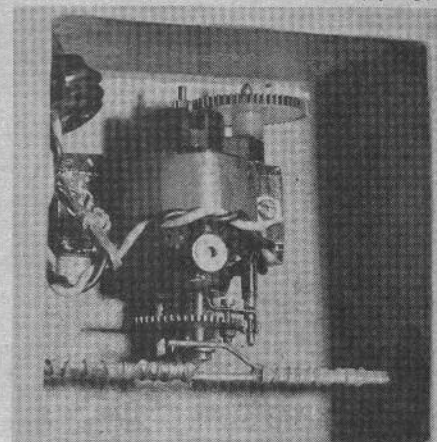Main change in aileron MM is 90-degree rotation of motor on its base (epoxy).



For elevator the DeeBee servo is used. Pulse fans will appreciate the others.

by **BOB FERRIS . . .** *An extremely easy-to-fly advanced multi stunt trainer with especially nice handling traits for proportional. Grid Leaks is happy to present this basic plan of an honest plane for your favorite gear.*

GRID LEAKS is rather proud of the fact that neither the magazine nor the designer of this airplane claim it to be still another multi capable of gunning down all before it. However, it is a fine airplane or it would not be here.

Bob Ferris, TWA jet pilot, is a long-time modeler who went into radio control via rudder-only pulse, Galloping Ghost, dual proportional; and for the past two seasons, full-house via Don Brown's DeeBee equipment. He flies for fun and he goes to contests. He knows how an airplane should fly—and on proportional.

Now, really good airplanes get built by other people without benefit of magazine articles. After GL spotted an R/C Jay in the hands of another TWA pilot, a veteran multi man, then a third and a

fourth with folks who learned to fly multi with them on DeeBee, the design was studied and evaluated over a 12-month period. It flies right, handles well, is safe, and the construction adheres to general practice in all major components.


GL does not compete with the popular magazines so an airplane plan—even if basic and without specific building instructions—is a landmark, and it is our policy to publish only occasional plans for airplanes—and perhaps other "things"—provided there is a real need for the project. Anyway, we hope you like this plan and use it to get some fun out of your dual-prop or full-house gear. Or stick that reed set in it!

The original plane has 3-ply 1/16th sheet fuselage (Continued on page 25)

PLANS FOR R/C JAY ON NEXT TWO PAGES


FULL-SIZE PLANS OF THE R/C JAY ARE AVAILABLE!

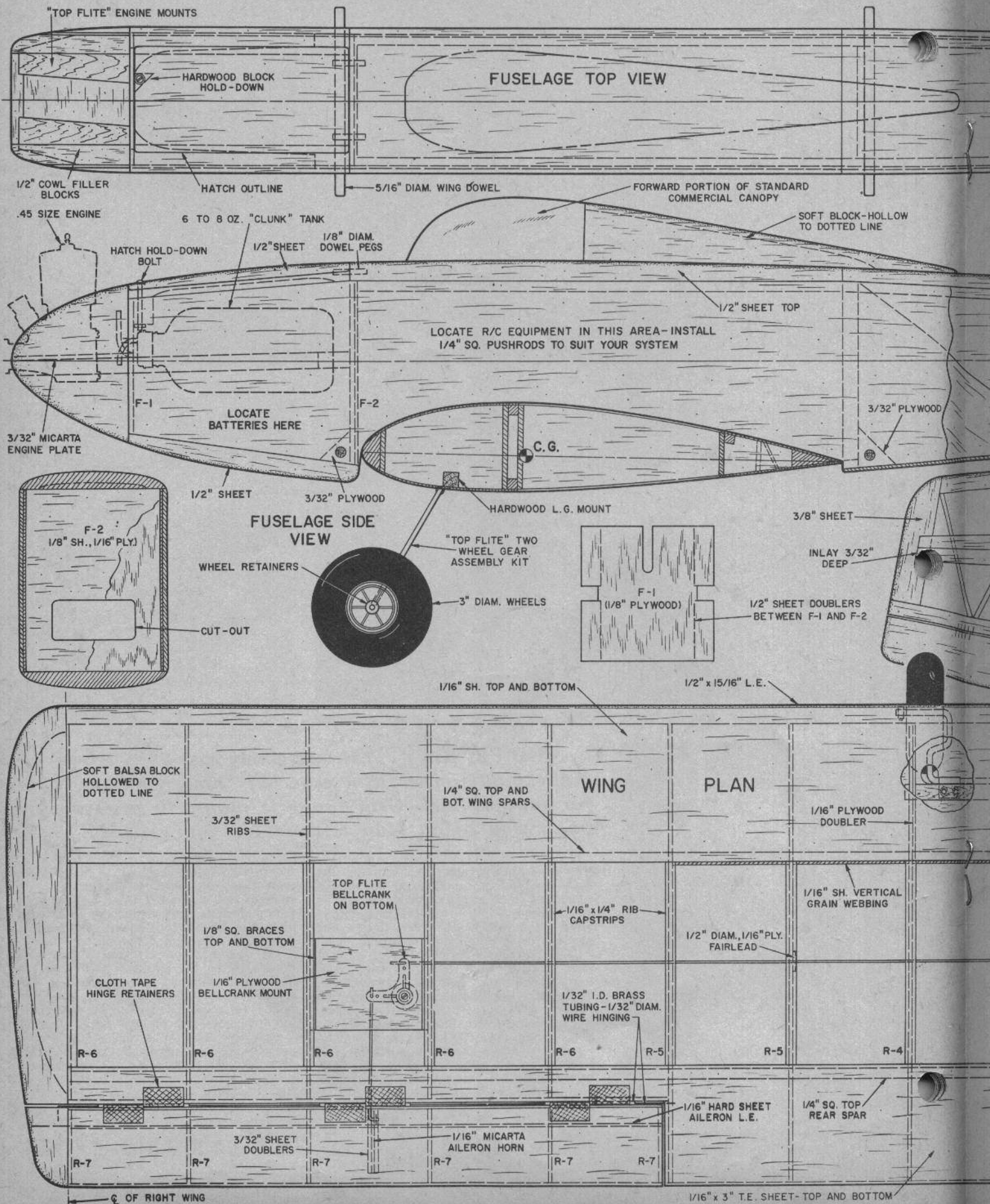These plans are individual prints—they are not folded—shipped to you in a mailing tube. Send \$2.00 to GRID LEAKS, Box 301, Higginsville, Missouri. Outside of the United States add 50 cents extra.




R/C JAY . . . Since this design is presented in basic plan form, a radio installation is not shown. Those who install proportional can easily approximate DeeBee setup in the pictures. For reeds, a standard servo group on removable mounting tray is recommended. Hardwood rails will be the only addition.

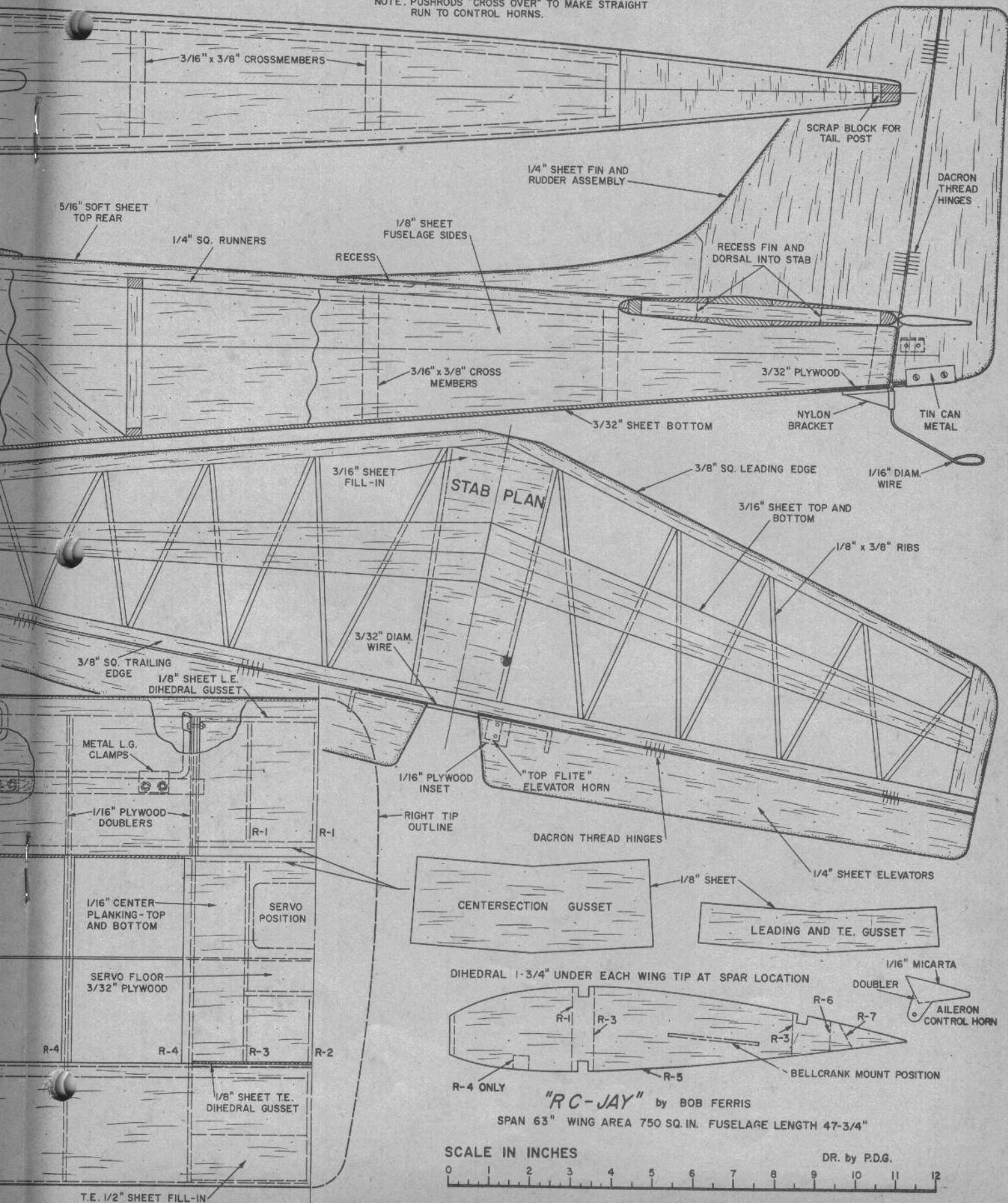NOTE: PUSHRODS "CROSS OVER" TO MAKE STRAIGHT RUN TO CONTROL HORNS.



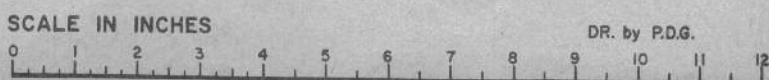"RC-JAY" by BOB FERRIS
 SPAN 63" WING AREA 750 SQ. IN. FUSELAGE LENGTH 47-3/4"







To the trade: This feature is open to all makes of equipment, domestic and foreign. Selection will be edited for reader interest and need.

SEEN THESE

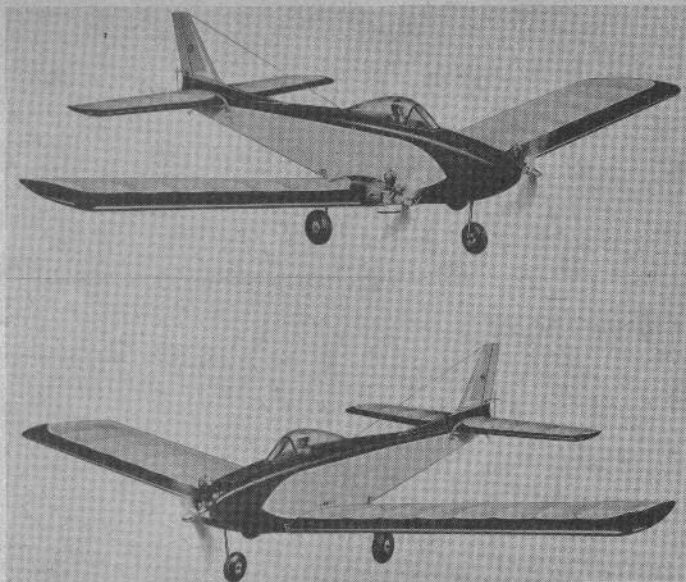
GL's coverage of new items, information and trade releases, now includes a coverage of useful products on the market.




1. Goldberg Models Skylark Jr.

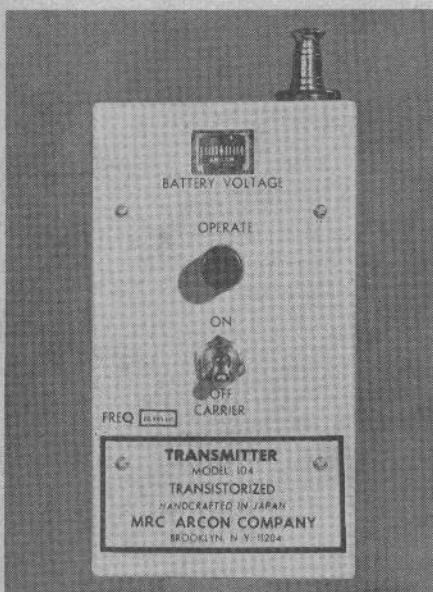

2. MRC Arcon Transmitter

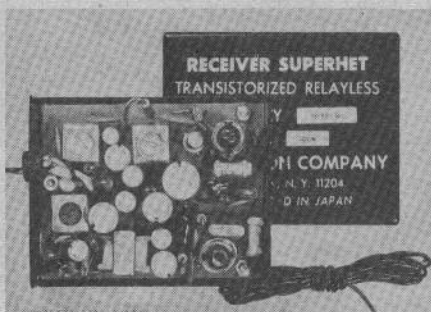


3. MRC Arcon Receiver

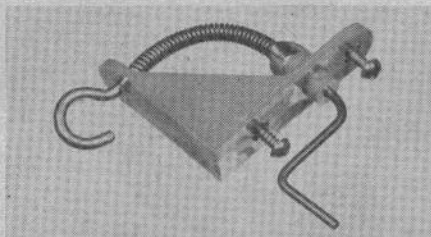


4. International's Side-Winder



5. Adams Proportional Actuator

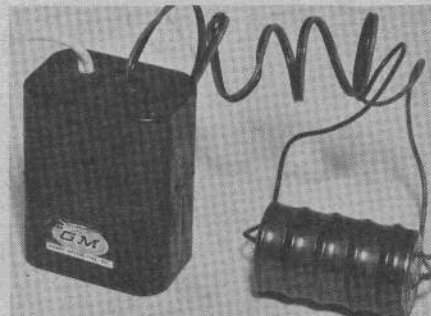

6. G.M. Hobby Charger

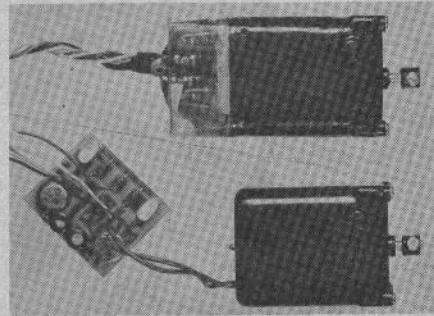

7. Relayless MC Servo

Skylark Jr. (Carl Goldberg Models, Inc., 9847 S. Claremont, Chicago 43, Ill.) for single channel, optional twin or single engine, .01 to .049, 37 in.; 2-3: MRC Arcon (MRC-Enya Co., 5300 21st Ave., B'klyn, N.Y. 11204) 18V x-mitter, matched superhet, relayless, 9V rcvr (\$79.95), built-in monitor; 4: Side-Winder escapement rubber winder (International Model Products, 33 Union Sq. W., New York 3, N.Y.), \$1.25, is 1 1/2 in. long dimension, weighs 1/6 oz.; 5: Adams proportional actuator (Ace dealers) for up to 1/2A, wgt. 29 grams, 2 center-tapped 30-ohm coils, 100 ma at 3V, \$6.95; 6: G.M. charger (G.M. Hobby Specialties, 105 Clifton Blvd., Clifton, N.J.) handles 20 to 40 ma, up to 9V, small in size—compare with servo nickel-cadmium battery pack—plugs into 110 AC household outlet (\$6.95); 7: Relayless version of Hillcrest Motor Control servo (Jerry Wellborn, P.O. Box 7258, Oklahoma City, Okla.) in two versions shown, one amplifier including servo, other encapsulated version with Acryjel. Encapsulated unit with Acryjel molding, \$14.95. Kit, including servo, \$12.00. Amplifier kit alone, \$8.00. Amplifier alone (assembled) \$10.00.

● Fuel Caddy from G.E.M. Models (48 W. Le Moyne, Lombard, Ill.). Chiefly concerned with manufacturing of fiber-glass boat kits, G.E.M. noted the need for an effective method for refueling boats and planes. The Fuel Caddy can be used for both transportation and dispensing of fuel—it holds a quart. The fuel syringe is eliminated. To fill the tank, the fuel line is removed from the solid fitting on the caddy, placed over tank inlet, then caddy is inverted and squeezed.

While Gary Preusse neglected to men-


tion price, GL can certify that the Fuel Caddy is quality merchandise—sample is excellent. In addition to the boat kits, G.E.M. handles Cameron and O&R engines, Octura, and G.E.M. fittings.

Gary also showed GL G.E.M.'s new heavy-duty green neoprene tubing for water hoses on boats or as fuel line for large glow engines. This tubing is 1/8" I.D. and 3/4" O.D., and is priced at \$.15 per foot.

G.E.M. also has a limited number of surplus 2/5 HP ball-bearing electric motors. They are 4 1/8" long, 2 3/8" dia., weigh 2 1/4


lbs. and draw 24 amps 24 volts at 10,000 rpm. These motors have powered 5 out of 8 winners of IMPBA records for electric speed boats. May also be used as model airplane engine starters; run well on 6 or 12 volts. Cost \$6.00, and a matching steel universal joint which fits a 3/16" shaft is \$2.95.

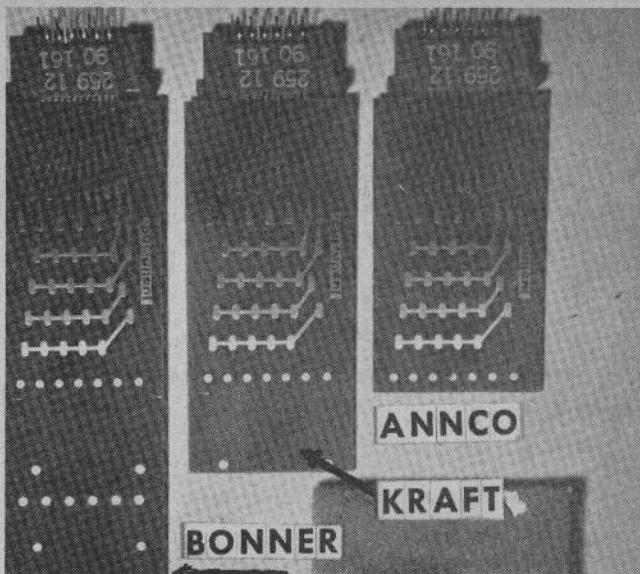● Omega Sales, Box 321, Racine, Wisc., advises they will have their popular reed switches available in SPDT configuration
(Continued on page 23)




8. Justin Micro-Tie Mk II

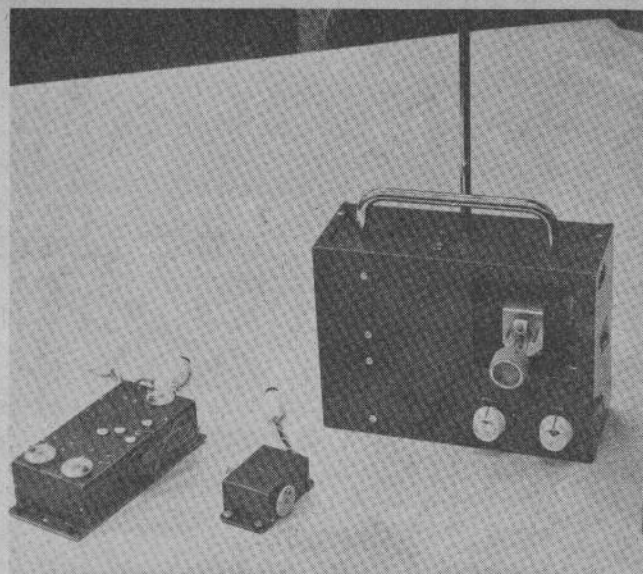8: Micro-Tie, Mark II (Justin Inc., 418 Agostino Rd., San Gabriel, Calif.) has greater versatility than company's old printed circuit board, thanks to redesign. Suits various servos—see article; 9: Bob Yates Multiplex 4-channel transistorized proportional (Bob associated with Reynolds Engineering, 2712 Greenway Ave., Winston-Salem, N.C.) sells direct to consumer at \$395.00 complete with 4 servos illustrated. Three servos can also be mounted in one case as shown. Feedback servos use Micro-Mo motor geared 60 to 1, bevel gear with total output ratio of 240 to 1. Weight 2 ozs. The elevator and rudder servos \$29.95, double-ended aileron servo \$32.95. See text; 10: MRC-Enya 45 R/C engine (MRC-Enya Co., Inc., 5300 21st Ave., B'klyn, N.Y. 11204) features separate idling and high performance ranges; double valve system eliminates compromise needle setting and stoppages on low-motor. Claimed 2000 to 13000 rpm, 7/10 h.p. Weight 10 oz. \$25.95 with throttle. (At dealer); 11: New 2V, 18 amp/hr acid cell battery (G.M. Specialties, 105 Clifton Ave., Clifton, N.J.) Use as booster for engine starting, or in multiples for boat drive. (4 x 1½ x 7—\$4.95.)




9. Yates Multiplex System

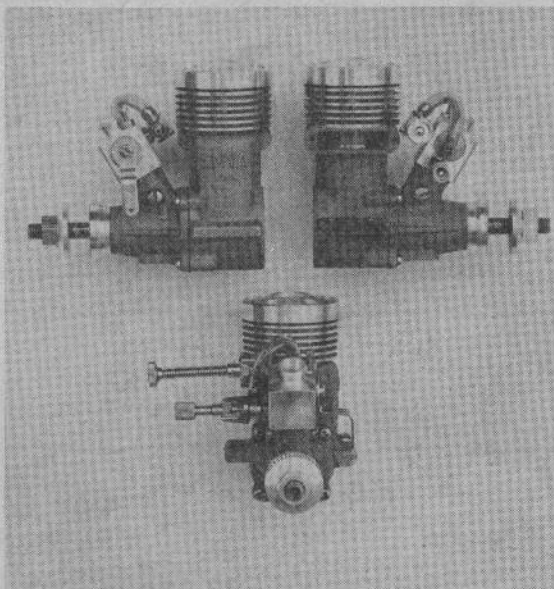


10. MRC-Enya 45 R/C




11. G.M. Acid Cell Battery

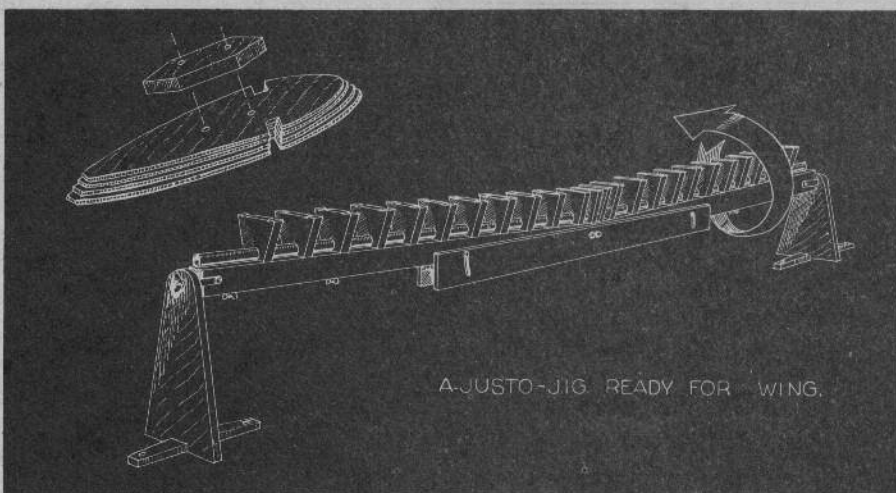

A-Justo-Jig (52 E. Washington St., Frankfort, Ind.) displayed the trundle-type fixture jig, shown in drawing and picture, left and below, at Toledo Weak Signals Conference. It insures accuracy, rotates 360 degrees to permit access to any portion of wing during assembly. Price will be under \$30 and the manufacturer will be guided by the interest you show in the device. It is described at length in the text. If such a jig is of interest to you, GL suggests you drop a line to A-Justo-Jig. The device was developed by James Kennedy, Jim Ellis, Bergen Hardesty.

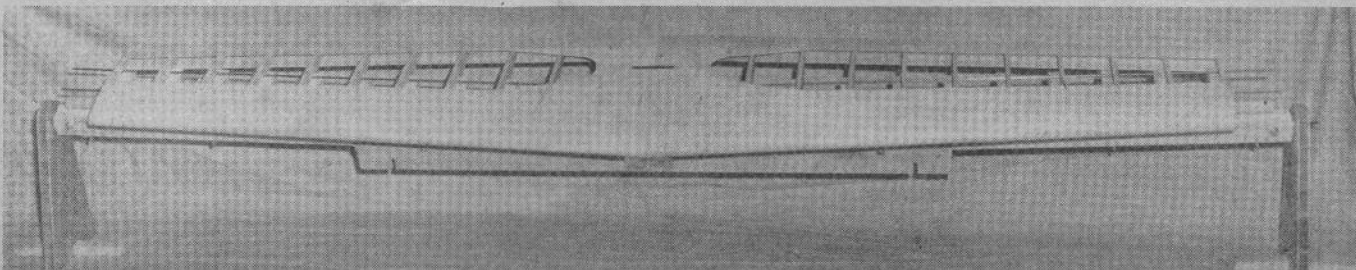


BITS AND PIECES...

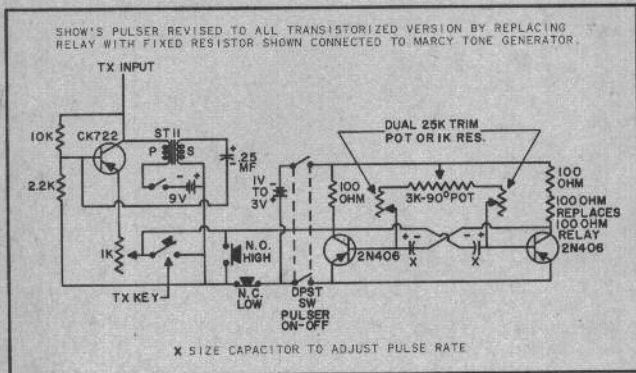

SHOWS PULSER—MARCYTONE GENERATOR

by Roland C. Rhein, Speedway, Ind.

■ Here is a diagram for a Shows pulser—with the relay removed—connected to a Marcytone generator. The pulser has been used all last summer, performs very well with any transistorized low-voltage tone generator. This scheme eliminates relay adjustments, and as noted, will work all the way down to 1 volt on the pulser. I hope someone else can find a use for this hookup that operates as reliably as I found it to.

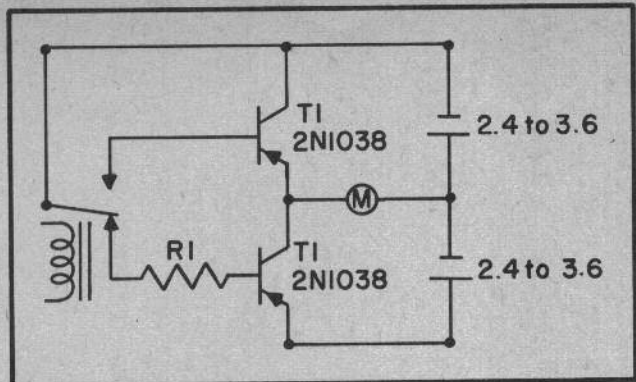

PROPORTIONAL CIRCUIT ELIMINATES ARCING

by Donald C. Fisher, Whitewater, Wisc.


■ This circuit answers the proportional fan's problems as far as relay contacts are concerned. It eliminates the necessity for cleaning, since it completely eliminates the biggest cause for the cleaning requirement—arcing.

R1 must be adjusted so that at 50-50 pulsing it will give neutral rudder. On 3.6 volts, this generally will be about 820 ohms. On 2.4 volts, 680 ohms is about right.

This circuit has several advantages over relayless circuits. The transistors are always driven to saturation, and do not tend to overheat, as in relayless circuits. Maximum power is always available for any given pulse rate, and high pulse rates do not cause relay points to carbon up.

I have flown this circuit for over a year and have found it extremely reliable. In fact, it has been so reliable that during the summer of 1963 I didn't have a single crash that was due to equipment failure.

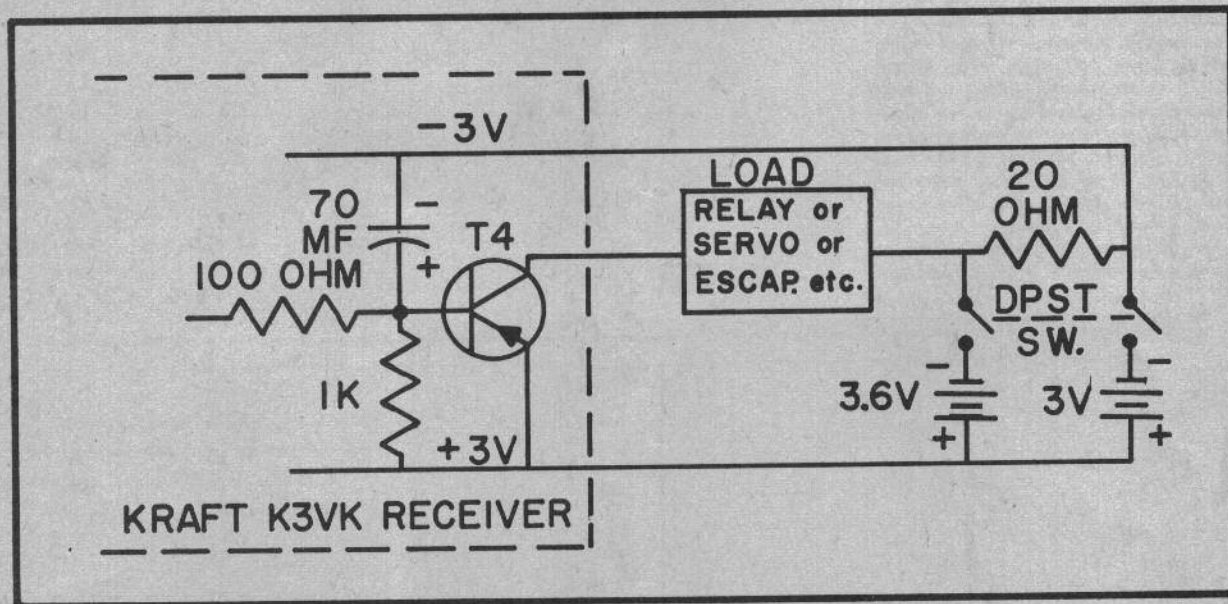I prefer the TI 2N1038, but I am sure that any 500 mil rating transistor would be found satisfactory.



K3VK MODIFICATION

by Allan K. Scidmore, Madison, Wisc.

■ Quite a few of us (MARCS) have one or more ships with the Kraft K3VK receiver and in general these have turned out to be quite reliable warm weather receivers. A few of us have yet to solve the below 50-degree operation problem, but that's beside the point. On several occasions we have observed interaction between the receiver and the escapement, relay, or servo that is being driven by the receiver signal (directly or indirectly). I have been using a separate supply to solve this oscillation problem now for two years and it appears to give satisfactory results to others who have tried it. The problem is quite similar to

"motorboating" in audio power amplifiers and the usual solution is adequate decoupling of the hi-gain low signal stages from the power stages. If the last transistor on the receiver (T4) is supplied from a separate or isolated supply, the problem has vanished. (The accompanying diagram should clarify these remarks.)


Note that the receiver drain is quite small if the last transistor is supplied from a separate supply. In my particular application the separate supply, V, was three Nicads for 3.6 volts and I used a 20-ohm resistor (shown dotted) to maintain the receiver batteries (2 AAA cells) in a charging rather than a discharging state. Although I had to charge the Nicads there was no need to replace these two small cells (about 0.3 oz. each) during the year.

CHANGING CONVERTER INPUT

by Frank J. Pisano, Staten Island, N.Y.

■ Just to let you know that 3.6V input transistorized power converter (GL Vol. IV, No. 3) can be changed to 6V input quite

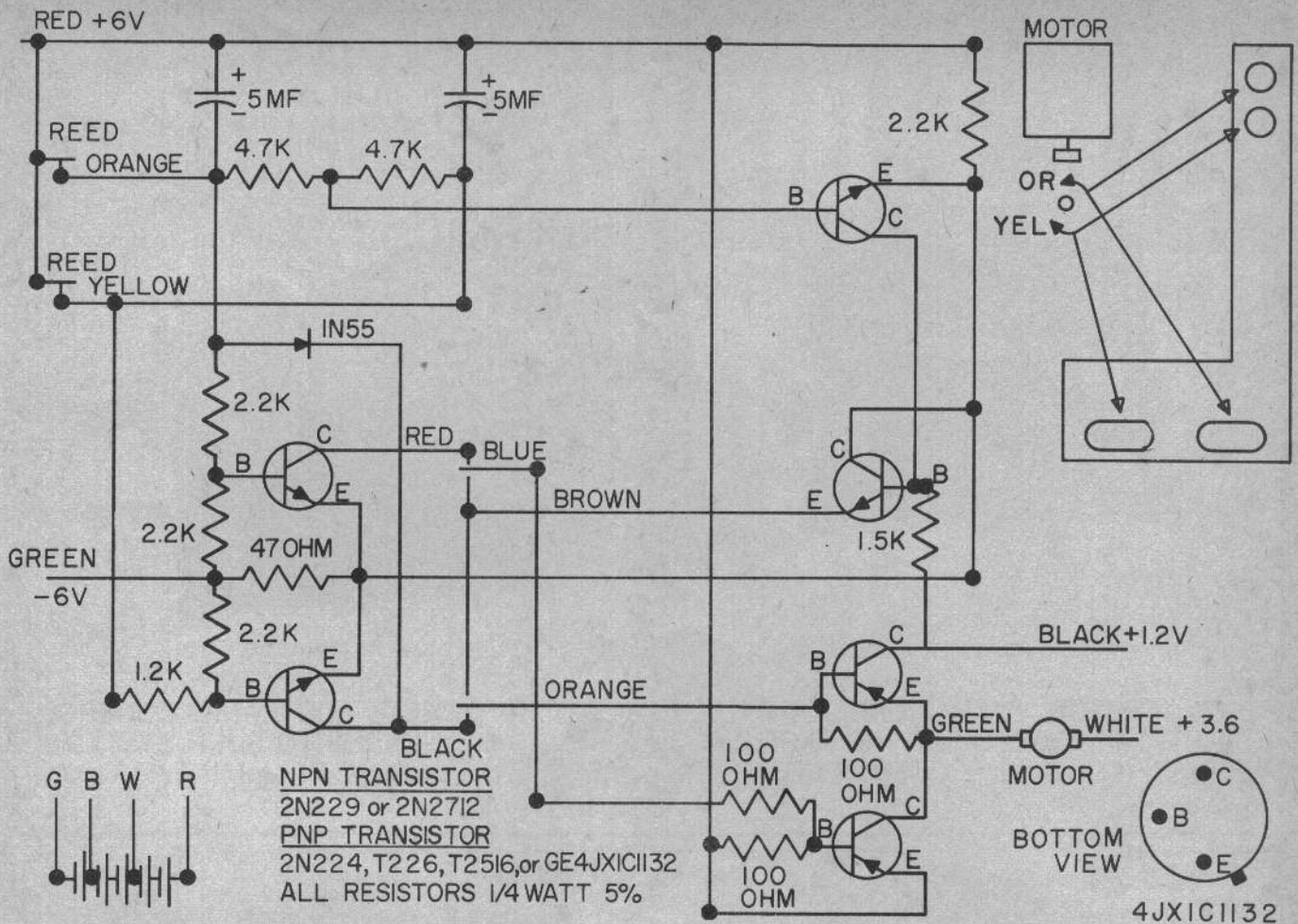easily by removing 250 turns from secondary of transformer. All components remain same output—same 135V at 20 to 25 ma. Some people still prefer 6V input as I do. I have series filament on my Orbit 10-channel so that I don't need dropping resistors on filaments.



TROUBLESHOOTING TRANSMITES

Mike Gossett and Bud Atkinson have developed some tips for troubleshooting Transmite servos with results attested to by other members of KC/RC.


If the servo will drive in one direction only, refer to upper right in drawing. Normally, the orange wire drives the servo in a counterclockwise direction, and the yellow wire clockwise. The arrows point to the transistors associated with the direction. The round symbols are the PNP drivers, oblong the NPN switches.

Replacing the opposite drive transistor will generally cure driving in one direction. If not, try replacing the switching transistor

as well. If servo works intermittently, Mike and Bud check for loose wiring and for solder joints subject to vibration troubles.

If the servo works correctly when the reed bank is bypassed, the capacitors are suspect. When a motor draws in excess of 300 ma it is replaced.

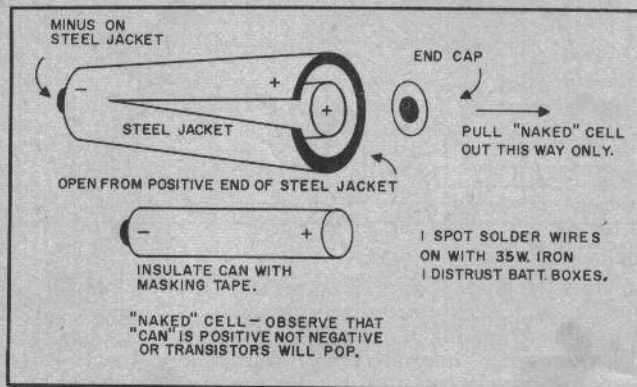
The new General Electric 4JXIC1132 transistor has been found to be one of the best for the drive circuit and will stand in excess of 300 ma without heating. It replaces the older Philco 2N223 and 2N224, and T2516 which are no longer manufactured. Basing on the 4JXIC1132 will be found different. A drawing of the 4JX is included.



WATCH THOSE E91 ENER-GIZERS

by Bob Gaede, Baltimore, Md.

One more R/C tip: The E91 Ener-Gizers (alkaline batteries) so highly touted for 1/4A and 1/2A have the same ills as all the other double-cased steel-jacketed cells—intermittent contact! After going nuts one Sunday with a buddy's Kraft 3 volt (it would work only with motor not running), I decided to experiment and take off the steel jackets. However, these EGI's are booby-trapped!! The polarity reverses with the "can" off and will blow out transistors if goofed! (See sketch.) Also, can must be removed as shown or loose end laps (causing all the trouble) will slip and short out half the "oomph" of the cell.

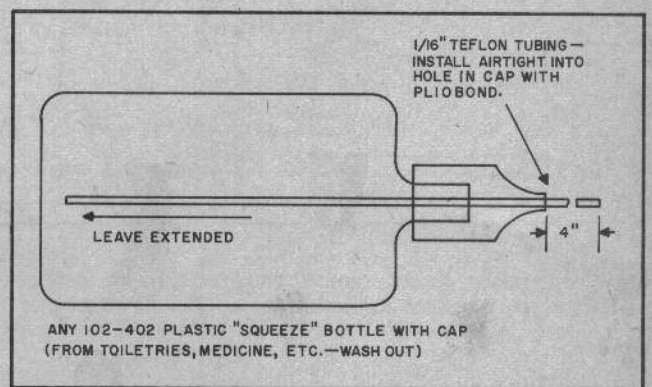


REMOVING EXCESS SOLDER

by Bob Gaede, Baltimore, Md.


Here is the solution for removing excess solder from P.C. boards, and relay, tube and socket terminals, etc., especially when switching components or repairing crash damage. This device does not leave excess solder in set to short out parts!

Procedure: 1) Heat joint to be disconnected; 2) Squeeze bottle, then apply tip of teflon to solder "blob." Release bottle and solder will be sucked up into teflon tube to solidify. (Teflon will not burn.); 3) Snip off 1/4" teflon, and you are ready for next fouled up joint!; 4) When teflon tube gets short, pull out of bottle and re-seal with Pliobond.

... Notes on Superhet Receivers ...

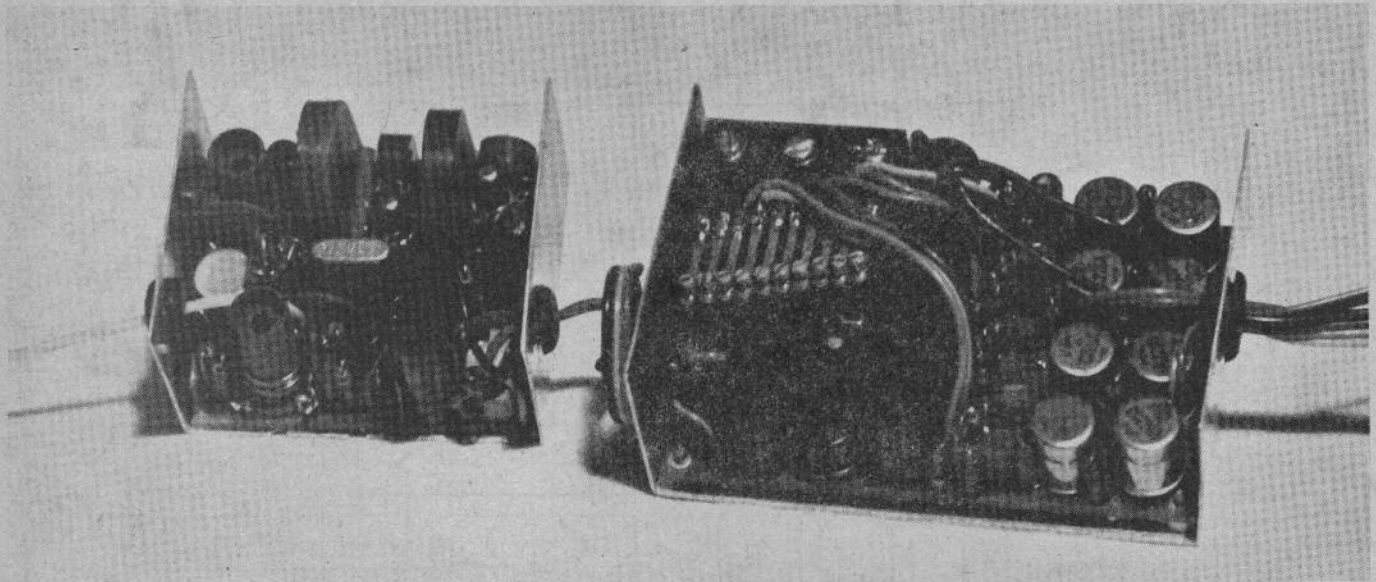

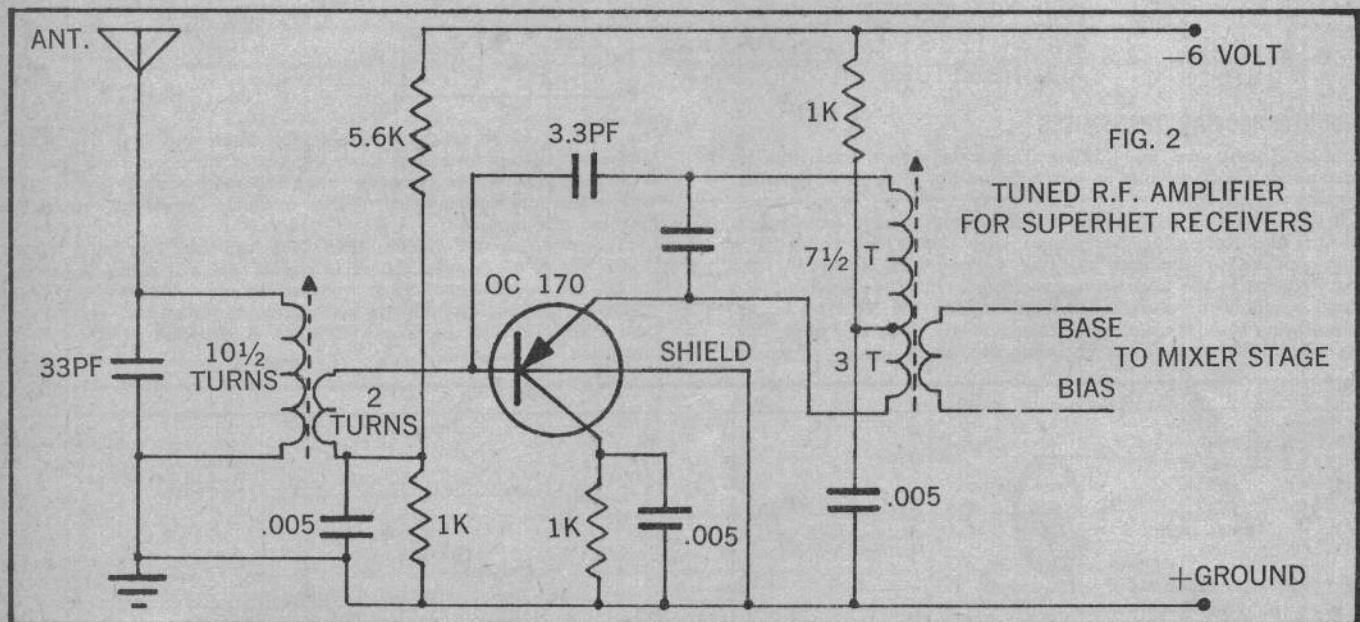by **DICK JANSSON** . . . A PIONEER IN THE FIELD OF SUPERHETS FOR RADIO CONTROL, THE AUTHOR IS NOTED FOR HIS APPLICATION OF RIGID STANDARDS TO SUCH SYSTEMS. THIS RECEIVER AND DECODER IS RESULT OF EXPERIMENTS IN PRACTICAL MINIMIZATION.



EXPERIMENTS WERE CONDUCTED recently to determine the practical minimization applicable to a superhet receiver system. Fig. 1 illustrates the flying equipment resulting from these trials. On the left is a receiver front end, assembled on a $1\frac{1}{2}$ by $1\frac{3}{4}$ inch printed-circuit board, weighing 45 gm. (about 1.6 oz.). On the right is a servo decoder unit consisting of an amplifier, reed bank, and four servo amplifiers, assembled on a $2\frac{5}{8}$ by $1\frac{3}{4}$ inch printed-circuit board and weighing 98 gm. (about 3.5 oz.).

A smaller servo decoder unit could be built but size and weight concessions were made, in the use of the Medco reed bank, to achieve ease in reed bank tuning and adjustment. The servo amplifiers are four transistor units for trimmable servos or self-neutralized servos (Bellmatic II).

Concessions were made also in the receiver size to include an R. F. amplifier to selectivity reject the I. F. amplifier image (between 26.1 Mc and 26.4 Mc for most 27 Mc

superhet receivers). Fig. 2 shows the R. F. amplifier, a conventional tuned-neutralized amplifier. The added parts cost is low, making the amplifier worthwhile in preventing I. F. image interference. It is estimated that a conventional transformer tuned I. F. amplifier could be constructed on the same size P. C. board as that illustrated with the transfilter I. F. amplifier.

Where can R/C equipment go from here? Some improvements may be gained from the future availability of smaller components. It may be difficult to use these as the P. C. board soldering techniques used on the illustrated units requires a delicate and skillful hand. More significant gains will be realized in the use of microelectronic circuits now being produced for advanced avionic equipment. These integrated circuits are not yet within the reach of the commercial R/C market, though, and they must remain a future vision. ■

Seen These?

(Continued from page 19)

Weight is 4.5 grams. Vibration can be withstood in excess of 35 g's. Over one hundred million switching actions at one-half ampere resistive load may be expected.

Ken Roberts of Omega states the SPDT was going in production. The 300-ohm version, known as the DT 300, has a maximum pull-in of 10 ma. (Probable price around \$6.00.) The DT-HR has a resistance of 3600 ohms, a pull-in of 3 ma, and will be priced around \$7.00. Further details from the manufacturer.

● James Kennedy, Jim Ellis and Bergen Hardesty of Frankfort, Ind., have come up with a new jig. Called A-Justo-Jig, it speeds the tedious task of building wings. The jig will accept any type of wing. A trundle type fixture allows 360-degree rotation for easy access to any part of the wing.

For greater accuracy, the A-Justo-Jig employs husky construction. Twenty-four adjustable rib locators are mounted on cadmium plated steel tubes to prevent warpage. The use of pine rib locators facilitates pinning ribs in place. The rib locators and the tubes are attached to sturdy dihedral rails. The dihedral rails are adjustable through a range of zero to 5 degrees. A large-size work bench is not a necessity. The A-Justo-Jig may even be mounted on a wall. It will accept wings of 6 ft., or slightly more, of any chord. Many stabilizers can also be constructed in a similar manner.

A-Justo-Jig was demonstrated at the Weaks Signals R/C Conference in Toledo, O. where many favorable comments were received. Although speed and accuracy are two of the desirable features of A-Justo-Jig, viewers were impressed with its versatility, and particularly that a wing could be constructed almost in its entirety before being removed from the jig.

The price will be under \$30.00, and production will be guided to a large degree by the interest you show in this device. Drop A-Justo-Jig a note at 52 E. Washington St., Frankfort, Ind., if you feel production of this item is warranted.

● Randy McGee of the Oklahoma City R/C Club visited GL and told of an interesting project that he and his fellow club members have taken on—a relayless unit from the popular Hillcrest motor control servo.

Photograph shows two versions. One is the amplifier, including the servo, and the other is the encapsulated version with Acryjel. The input is 0.7 MA. The output transistor will carry 3 amps, and it is reputed that two and three servos have been run simultaneously from one reed pair. Servo has a slip clutch, which makes it ideal for positionable action. The weight is 2 ounces, and it develops 4 pounds of torque.

The encapsulated unit with Acryjel molding is \$14.95. The kit, including servo, is \$12.00, the amplifier kit alone is \$8.00, and the amplifier alone assembled is \$10.00. Contact Jerry Wellborn at P.O. Box 7258, Oklahoma City, Okla.

● Dick Adams, an old timer to radio control, has been prevailed upon to reintroduce the Adams proportional actuator, initially introduced at the Nationals in 1953, and commercially available around that time. The new model is about half the size of the old one, and produces twice the torque.

This patented proportional actuator has many features not found on others of its

SENSIBLE R/C!

EVERY NEEDED FEATURE FOR TODAY'S FLYING CONDITIONS



The "Digitran" Transmitter
(8 Transistors)


Super-Heterodyne Receiver and Escapements
(9 Transistors)

TRANSMITTER 39.95 MARK VI ESCAPEMENT 11.95 MOTOR MINDER 5.95 RECEIVER 39.95

The BCT-18 "Digitran" is a true digital transmitter that forms the pulses, rapidly and accurately stepping the improved high resistance Mark VI Hyper Compound escapement. The BCR-18 is a crystal controlled super-heterodyne (weight 2 1/4 oz.) designed exclusively for model aircraft. These two units with escapements shown for a complete R/C system for right and left rudder, up

and down elevator and motor speed control. Motor control is by the "Quick Flip" system and with a special circuit, you get motor speed control every time. This system is applicable to any small to medium size model aircraft. Transmitter and receiver are powered by inexpensive 9V. batteries.

NO RELAYS - NO "ADD ONS" - NO GADGETS... JUST SENSIBLE CONTROL

 from the First Name in Radio Controls
Babcock Controls Inc. 20762 Laguna Canyon Rd. / Laguna Beach, Calif. / 494-0745

type. It is designed for 1/8A to 1/2A airplanes. Weight is 29 grams. Has two 30-ohm coils center tapped, and pulls a maximum of 100 ma at 3 volts. May be used with 6 volts. Designed for double-ended relayless or relay-type receivers. Delrin is used as the bearing material, and this is part of the secret for the fantastic performance. Delrin is excellent bearing material, and shows virtually no wear, and will never require lubrication.

This actuator represents a refinement of 11 years of testing. Price has been set at \$6.95. (Available through your Ace R/C dealer.)

● Justin Inc. has announced their new Micro-Tie, designated Mark II, more versatile by redesign of the printed-circuit board. The Mark I fit the back of a Bonner servo; the Mark II will fit a Bonner,

or by cutting off the board at appropriately marked spots, the new Kraft servo or the Ancco. In its smallest configuration (cut for the Ancco) it makes an ideal unit to mount to the fuselage side or glue to the servo tray.

The same high quality edge connector has been maintained and the new board is compatible with Micro-Tie systems already in use. Price remains \$7.95. The manufacturer has reported excellent reception of the Micro-Tie and we can attest to seeing many multi jobs with really sharp looking radio compartments which used it. Justin, Inc., 418 Agostino Rd., San Gabriel, Calif.

● Reynolds Engineering has developed a feedback servo measuring 1 x 1 3/4 x 2 1/8 in. Weight is two ounces. Uses the Micro-Mo 60/1 gear ratio and beveled gear with a total ratio output of 240 to one. Five

FLY AS HIGH AS YOU WANT

MRC-ARCON THE NEW DIMENSION IN R/C

Amazing range, unusual freedom from interference and rugged dependability mark the advance design MRC-ARCON R/C gear. Engineering Excellence from the combined skills of Japan's finest R/C manufacturer allied with the U.S. hobby industry's oldest and most dependable supplier of electronic equipment.

Designed by professional flyers to commercial standards and incorporating circuitry and features heretofore unavailable in any single unit. Completely transistorized, hand crafted, precision pretuned and supplied in matched sets. Simple installation with complete instructions and one year written guarantee supplied. Compare the finest in R/C at your dealer now. **SINGLE CHANNEL MATCHED SET TRANSMITTER AND SUPERHET RECEIVER... \$79.95**



TRANSMITTER Model 104

HIGHER OUTPUT—18 Volt battery supply eliminates range problems.
EASY TO HANDLE—comfortable one hand operation.
PRECISION CONTROL—microswitch for positive feathertouch actuation.
PENETRATING SIGNAL—tone modulation at 500 cycles per second.
BATTERY VOLTMETER—built in monitor warns you before it is too late.
CRYSTAL CONTROLLED—shock mounted crystal for frequency stability.
ECONOMICAL OPERATION—uses 2 inexpensive 9 volt transistor batteries.
LONG RANGE ANTENNA—12 section 50 inch retracts into transmitter.
COMPACT & LIGHTWEIGHT—Fits into Jacket pocket, weighs less than 1 pound.
RUGGED—Heavy gauge aluminum cabinet.


RECEIVER SUPERHET TRANSISTORIZED RELAYLESS

RECEIVER Model 1004 SUPERHETRODYNE

HIGHEST SELECTIVITY—three IF stages for adjacent channel rejection.
RELAYLESS—electronic switching, no vibration problems.
SENSITIVE—pulls in signals other receivers might miss.
RUGGED—sturdy aluminum cabinet, Epoxy-glass printed circuit board.
DEPENDABLE—9 volt transistor battery power—no design compromise.
PRETUNED—precisely matched to transmitter, crystal control stability.
COMPACT & LIGHTWEIGHT—miniaturized components selected for dependability.
COMPLETE—EASY INSTALLATION—connector prewired to receiver.

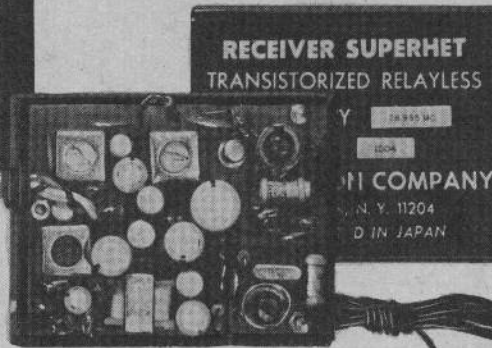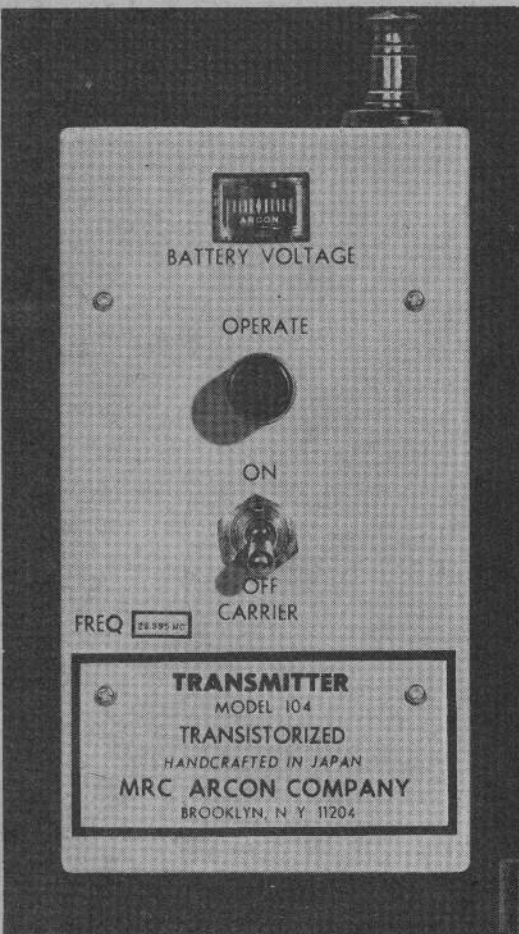

MRC-ARCON Multi Equipment

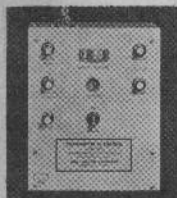

Matched Sets with exclusive features. Swivel mounted integral antennas to minimize null area effect. Jewelled battery voltmeters. Superhet Receivers. A host of other features.

6 Channel simultaneous matched set Receiver and Transmitter... \$139.95
10 Channel simultaneous matched set Receiver and Transmitter... \$179.95

MRC-ENYA COMPANY INC. • 5300 21st AVENUE • BROOKLYN 4, NEW YORK

WHEN YOU MOVE!

Postal regulations require that you pay extra postage on all magazines forwarded to you at a new address. Copies will not be forwarded free, and we cannot replace lost copies.

To insure delivery at your new address PLEASE NOTIFY US NOW OR SURELY 6 WEEKS IN ADVANCE OF YOUR MOVING. Write in old and new address below, if possible include the address label from your last issue. Thank you.

Please mail this form today to:

GRID LEAKS Subscription Dept. Box 301 Higginsville, Mo.-64037

Old Address

Name _____ *Please Print*

Address _____

City _____ State _____
zone

Be sure to give us your New Address

Name _____ *Please Print*

Address _____

City _____ State _____
zone

transistors are used in the amplifier. Has nylon bushings on the shaft, and a nylon disc for the hook-up arm. The aileron servo has a double-end disc so that hook up to linkage can be made from each side for strip ailerons. Output power is 4 lbs. Uses 2.4 or 3 volts on each side, and a 2.4 or 3 volt Refance voltage. (Can be used with or without the Refance voltage.)


The elevator and rudder servos are announced at \$29.95, and the aileron servo, double ended, is \$32.95. They were designed by Bob Yates, who is associated with Reynolds Engineering, at 2712 Greenway Ave., Winston-Salem, N.C.

Further information about this, as well as their new proportional 4-channel all-transistorized receiver and transmitter, may be had by writing directly to the manufacturer. The transmitter and receiver sell direct to consumer at \$395.00, complete with 4 servos as illustrated. The 3 servos may also be had mounted in one case, as shown in the photograph.

● In conjunction with their 33rd anniversary AHC (America's Hobby Center, 146 W. 22nd St., New York, N.Y. 10011) offers free their special 64-page Bargain Catalog which includes over 10,000 models and items—with it you get free gift coupons (with any order a gift is obtainable by attaching one of the coupons). Free copy of Bargain Bulletin # AB264 may be obtained by sending an unused five-cent stamp for postage and handling to AHC. The address included Dept. GL-AB—a common device to clue an advertiser on a magazine's effectiveness. May we suggest you say you saw it in GRID LEAKS—and do the same when answering any ad. Advertisers make possible more and better material.


● Top-Flite Models, Inc. (2635 S. Wabash, Chicago, Ill.) announces additional accessories available at your hobby shop, including: E37—2" nylon bellcrank, 25¢; E38—3" nylon bellcrank, 30¢; E39—4" elevator horn, 30¢; E40—Tauri landing gear, \$1.50; E42—pair of Taurus engine mounts, 50¢; E43—8" fuelproof canopy, \$1.00; E44—elevator horn with bearings (15-degree differential), 85¢; E45—pair formed leading edges, 33" long, \$1.50; E46—pair stripped ailerons, 75¢.

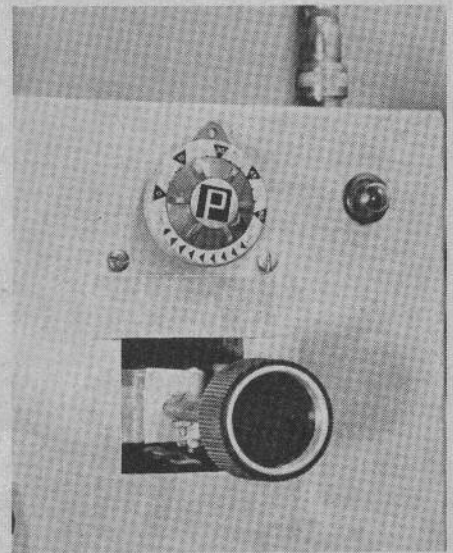● Looking for Dzus fasteners? Aircraft Plan Co. (P.O. Box 45, Babylon, N.Y.)



Engine run warning timer Bob Ferris' Dee Bee x-mitter (one prototype) came from Lafayette. Real purpose was parking meter warning—buzzes in pocket.

WORLD ENGINES

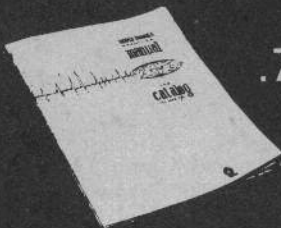

70

New Catalog

The new World Engines catalog and technical manual now runs one hundred thirty some pages. We think this to be the most complete catalog in model aviation. To justify the title "Technical Manual" the book includes. . . .

- ▶ Three view scale engine drawings.
- ▶ Circuit diagrams for Control-aire transmitter, amplifiers & receivers.
- ▶ Information on the new Orbit proportional equipment.
- ▶ Displacement, bore, stroke information of most of the World's model aircraft engines.




WORLD ENGINES INC.

8206 BLUE ASH RD. CINCINNATI 36, OHIO

Prize Winning OCTURA Hi-Impact Plastic R/C PROPS!

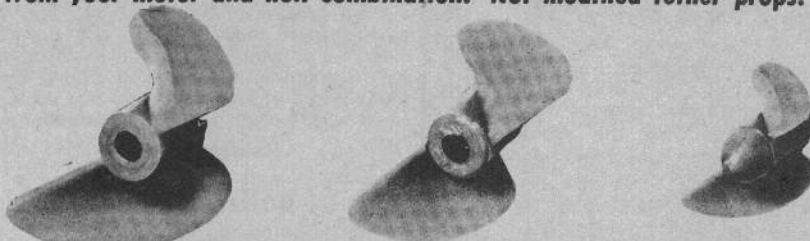Designed specifically for R/C model boats . . . get best performance from your motor and hull combination! Not modified tether props!



Octura props are the result of extensive tank testing and competition running. Are molded of high luster, high impact plastic. Range of diameters and pitches suitable for engines from .15 to 1.50 c.i. displacement. Completely finished and balanced—ready to install and run. Holder of more R/C model boat records, both here and abroad, than any other propeller. Look for the distinctive red color and shape. Propellers X35 thru X70 and 40P thru 62P are supplied with $\frac{3}{16}$ " bore and slotted to fit drive dog OC-6D.

The X30, 30P and 35P are tapped 8-32 and equipped with a molded tail nut. Available in two patterns, the power thrust designs for displacement and heavier type model boats plus speed thrust design, for hydro and light displacement hulls.

SPEED THRUST

X30	— $1\frac{3}{16}$ " D x $1\frac{2}{32}$ "	Pitch—15	Eng.—55¢
X35	— $1\frac{7}{16}$ " D x $1\frac{1}{16}$ "	Pitch—19	Eng.—65¢
X40	— $1\frac{1}{16}$ " D x $2\frac{7}{32}$ "	Pitch—29	Eng.—75¢
X45	— $1\frac{1}{4}$ " D x $2\frac{1}{2}$ "	Pitch—35-45	Eng.—85¢
X50	— $1\frac{3}{16}$ " D x $2\frac{25}{32}$ "	Pitch—56-60	Eng.—95¢
X70	— $2\frac{1}{4}$ " D x $3\frac{7}{8}$ "	Pitch—O & R, Twin 60	Eng.—\$1.75

POWER THRUST

30P	— $1\frac{3}{16}$ " D x $1\frac{1}{16}$ "	Pitch—15	Eng.—45¢
35P	— $1\frac{7}{16}$ " D x $1\frac{1}{16}$ "	Pitch—15-19	Eng.—55¢
40P	— $1\frac{1}{16}$ " D x $1\frac{7}{8}$ "	Pitch—15-29	Eng.—65¢
45P	— $1\frac{1}{4}$ " D x $1\frac{25}{32}$ "	Pitch—29-35	Eng.—75¢
50P	— $1\frac{3}{16}$ " D x $1\frac{25}{32}$ "	Pitch—35-45	Eng.—85¢
55P	— $2\frac{7}{32}$ " D x $2\frac{1}{4}$ "	Pitch—45-60	Eng.—90¢
62P	— $2\frac{1}{2}$ " D x $1\frac{25}{32}$ "	Pitch—60	Eng.—95¢

For RED-HOT sizzling performance ORDER one for your boat TODAY!

If your dealer can't supply you . . . send stamped, self-addressed envelope for literature and prices.

OCTURA MODELS BY MODEL BUILDERS . . . FOR MODEL BUILDERS!
8144 $\frac{1}{2}$ No. Milwaukee Avenue • Niles 48, Illinois

has two sizes, either size 75¢ the pair. The short version AJ4-55 is used in the Whistler R/C, long version in Stark Shark.

● Boat fans attention! Lumba-Lumba is the name of ship operated by Caltex Pacific Oil Co. to speed passengers and freight from Sumatra to Singapore, a graceful looking craft which resembles a cross between a small motorship and a big cabin cruiser. Sterling Models' (Belfield & Wister, Philadelphia 44, Pa.) 40-in. kit for gas or electric power makes a most distinctive R/C craft. A 38-piece metal fitting set sells for \$3.95, the boat kit, less fittings, \$16.95.

● Ted Strader's Scorpion, a functional looking design for any control from rudder only to multi, is a trike-geared shoulder wing for a .15. Span is 56 inches. GL previewed this one at the Bison's Conference—a nice job. (Special Edition Plans, Box 48, Massena, N.Y.—\$12.95.)

● Kraft Custom Battery Packs. Conveniently shaped in a sealed nylon case with a prewired plug ($2\frac{3}{8}$ x $1\frac{5}{16}$) these extra capacity 600-mah nickel-cadmium cells weigh $5\frac{1}{2}$ ounces. For 6V reed operation, \$24.95; with charger \$29.95. Proportional packs will be available to manufacturers' specifications.

Kraft Custom dual-simultaneous, six-channel transmitter with superhet receiver, \$119.95. Pre-cabled servo leads require only point-to-point wiring; 9V all-silicon transistor x-mitter. Tone stability from 0 to 140 degrees. Full $\frac{1}{2}$ watt input.

● Aero 35 engine price reduced. This novel horizontal piston engine formerly \$34.95 for standard and \$40.90 for R/C, now priced at \$28.95 and \$34.95 respectively.

R/C Jay

(Continued from page 15)

sides, center ply grain diagonal. But $\frac{1}{8}$ sheet with a $\frac{1}{16}$ doubler diagonal, as shown, is acceptable. If this suggests the ship is light, it is— $5\frac{1}{2}$ to 6 pounds gross. The use of $\frac{1}{2}$ in. thick top and nose blocking—with $\frac{1}{4}$ sq. corner strips for rounding—makes for quick assembly and some shaping for appearance. The Top Flite motor mounts incorporate right-thrust as they come from the manufacturer. An 8-oz. clunk tank supplies the Veco 45—or your favorite engine—and should have the feed $\frac{1}{2}$ inch below the needle. Hatch access to tank and battery pack is standard.

Tail surfaces are generally similar to Top Flite kit construction. Control surface areas and movements are correct. The over-and-under spars and sheeting of the wing are standard and require no description.

The steerable wire tail skid works very well on grass and seems to be acceptable on concrete, though a rubber tired wheel—the tread ground flat and with drag imposed—has been used for concrete. The two-wheel gear (Top Flite) does not seem to involve typical nose-over trouble on grass, even for beginners, probably due to the fact that there is not much of a couple between the thrust line and the wheel center, or between the thrust line and the center of aerodynamic drag of the machine—and the wheels are forward!

DuBro Kwik-Links are used for control linkages throughout, even on the aileron bellcranks. There has been evidence of pin wear in the Kwik-Link at the aileron horn, resulting in an excess softness in the setup—easily cured by installing another Kwik-Link. The wear is thought due

12 CHANNEL SUPER-HET

Flight Proven Reliability

Receiver operates on 6 volts. Temperature compensated zero°—140° F. New design high frequency reeds. High impact plastic case 1" x 2" x 3". Wt. $4\frac{1}{2}$ oz.

Ten Channel Super-het \$89.50
Twelve Channel Super-het 99.50

ALL TRANSISTOR TRANSMITTER

Operates on one nine volt battery. Features a meter for accurate tuning and battery checking. High quality components assure RF and tone stability. Size, 3"x $5\frac{7}{8}$ "x $8\frac{3}{4}$ ". Wt. $3\frac{1}{2}$ lbs. with battery.

10 Channel Transmitter \$118.50
12 Channel Transmitter 129.50
(less battery)

DM 60 Six Channel

6 Channel Super-regen. (relay) receiver \$57.50
6 Channel non-simul. transmitter 61.50

CONNECTORS

8 pin-polarized \$1.30 pair

SPDT RELAYS

50 ohm \$3.85 500 ohm \$4.00
100 ohm 3.95 1250 ohm 4.10
5000 ohm 4.25

REEDS

2, 4, 6, 8, 10 and 12 Channel

See Your Dealer Or Order Direct
Calif. Res. Add 4% Sales Tax

w. s. deans co. 8512 Gardendale
Downey, Calif.



R/C PROGRESS AT 1964 NATS

Radio control was born as a Nationals event the same year the Academy of Model Aeronautics was organized—1936. The Academy and R/C have progressed tremendously since then. The 1964 Nationals to be held July 20-26 at NAS Dallas will be another measure of this progress.

No contestants entered the 1936 R/C event, and in 1937 most of the equipment was plagued by bugs. Chet Lanzo was proclaimed the 1937 winner, although there was only a minimum demonstrated control of his aircraft, it met the only requirement of the event.

In contrast, at the 32nd Nationals held last year at Los Alamitos, Calif., 194 contestants flew in the five R/C events, accumulating 753 flights. Equipment failure was as rare as was controlled flight in 1936. The aircraft flown, and the skill with which they were flown, advanced the state of the art another degree toward the ultimate.

Technological progress is welcomed by the model builder and by the AMA, but it presents problems to both. R/Cers find it difficult to keep current with the latest equipment. The AMA must keep its Nationals procedures ahead of the ever improving and rapidly growing event. Larger numbers of contestants must be handled, and each given adequate opportunity to compete.

At Dallas, all Citizens Band flying will be done on the superhet frequencies, and four flight lines will operate simultaneously. This is expected to double the number of flights possible, two flight lines being the general rule in the past.

All superhet equipment will be checked for frequency accuracy and, if necessary, frequency changes will be made (aided by special facilities on the scene) to equalize flight line distribution of entrants. In response to an appeal by AMA for cooperation, R/C manufacturers are providing service booths for their equipment to expedite any need frequency for adjustments.

In attempting this new procedure, AMA Nationals officials fully realize the potential criticism that might accrue from every crash which remotely could be blamed on interference. They feel this approach should be tried, however, as the preferred method of increasing flights. Another approach would be to limit entries through a qualification system, but it is not desired to restrict entries except as a last resort. Yet a combination of both methods may be desirable for the Nationals coming up in Philadelphia and Chicago, which usually have a larger attendance.

In any case, AMA expects the 1964 Nats in Dallas to feature the world's greatest R/C sporting event this year, and Academy officials have been planning steadily and progressively to match the contest to the conditions.

to constant quivering, though slight, of the proportional gear. Hardly a problem, this may, or may not, deserve mentioning.

Having an experienced pulse man's way with Mighty Midgets, Bob has saved money in the construction of three servos, the principal innovation being the separation of the motor casing from the base, to permit a 90-degree displacement to lie flat, the parts epoxied together in the new position. The type of plugs and sockets (Amphenol) in the pictures (thick, round pins) have proved free of trouble on several of these ships which came to GL's attention.

Bulldog Tank

(Continued from page 13)

being able to fire the cannon."

The Bulldog tank comes with solid axles and only one drive motor. It was necessary to cut the axles so that the treads could be driven independently. (The axles were held in line by slipping a length of brass tubing over the severed axle halves.) Naturally, a second motor and gear train was necessary. The boys solved this problem by purchasing a second tank—four tanks in all! This may not have been the most economical approach possible, but it gave them additional ammunition for the cannon and a second rear deck for each tank to cover the power switches and the mounting hardware of the two drive motors. (The shells and cartridge cases are wood and metal respectively and fit into clip.)

If you will study the bottom view photo, the drive motors are seen at the rear. Just forward of them, mounted on the under side of the original battery compartment, are the connections to the four motor control relays and the wire-wound pot. Kern states that he used industrial-type relays available to him, while Phil employed normal modeling relays. The relay specs are not critical provided the relays can handle the electrical load at the voltage indicated.

The same applies to the wire-wound pot (4-watts) which is used to adjust the speed of the faster motor for straight ahead running when no turning signals are given. (It is hand adjusted.) The pot is in series with the motor.

Forward are two compartments which are separated by the plastic hammer and spring arrangement for the cannon. The receiver (six or more channel reeds needed) goes in the compartment on the port side (as seen with the tank in running position) and four surplus nickel-cad batteries fitted into the starboard compartment. Ahead of these, and mounted on the under side of the front apron are the battery holders for dry batteries to power the receiver. The installation on the underside of the tank is completed with the addition of the two headlights (self-focusing 3-volt lamps in series) just ahead of the receiver batteries, two slide switches mounted on the rear deck near the drive motors and a pin jack for the antenna, also located on the rear deck. All of the wheels on which the treads ride are held in place in their respective slots by the metal bottom cover which screws to the under side of the tank (not shown).

The cannon firing mechanism in the turret uses the original hammer and spring but is cocked electrically by an electric motor and gear train. The motor and all of the gears except the large metal one come from a Bonner Duramite servo. The motor runs until the microswitch senses that the hammer has been fully cocked. To fire the cannon, the receiver relay momentarily shorts the open contacts of the microswitch which starts the motor. The hammer is released, firing the cannon, and the

motor continues to run until the hammer is again cocked and the gun ready to fire again. When storing the tank for long periods of time, the cannon is fired and the battery power turned off before the cannon re-cocks itself. This leaves less tension on the cannon firing mechanism.

As can be seen from the diagram, the four nickel-cad batteries power all of the relays, the two drive motors and the cannon firing mechanism. (Also the headlights.) The contacts of all of the motor control relays are normally in the up position (K_1 , K_2 , K_3 and K_4). When energized, they move to the down position. K_1 and K_2 are locking relays that start the tank forward or backward. As shown in the diagram, down elevator would cause K_1 to close and remain locked closed. This starts both drive motors forward and turns on the headlights. If either left or right rudder were actuated, K_3 or K_4 close momentarily, causing one tread drive motor to reverse. The resulting turn is made in the length of the tank due to the tread reversal feature. If the low engine control is called for, the locking circuitry for K_1 and K_2 is released, causing the drive motors to stop and the headlights to go out. If high engine is called for momentarily, the microswitch in the gun turret is shorted and the gun fires and re-cocks itself.

The receiver power wiring is not shown since it will vary with the type of receiver used. The two switches mounted on rear deck of the tank are used to turn off the receiver power and to disconnect the nickel-cad batteries.

Grid Leaks at Play

(Continued from page 1)

have as many, or more, technical articles than in the old smaller format. We invite you to look this issue over closely, and since we believe you will find a greater technical coverage than ever before.


Plans will be presented on an occasional basis whenever there is a clearcut need for a certain type of plane—or boat.


We are very grateful to the many of you who have taken time to have sent us your comments. One comment even went so far as to say that we looked "too pretty" for him to submit any ideas or articles. This is to advise that we will accept pencil scratchings, provided they are legible, and we will do the art. What we are interested in primarily is your ideas which you would like to share with your fellow radio-control modelers.

● The last few issues of GRID LEAKS have been frustratingly late. This has been due to a series of circumstances which cannot be pinpointed in any one cause. However, when your printer moves a physical plant as large as American Press is, there are bound to be unforeseen delays.

We want to assure you that we are making every effort to correct this situation, and hope you will bear with us.

PAUL F. RUNGE, PUBLISHER

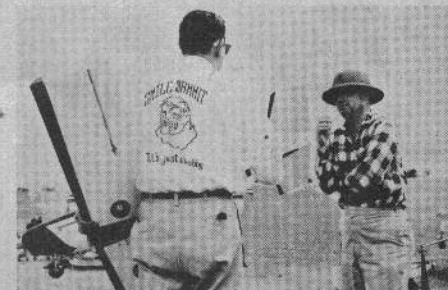

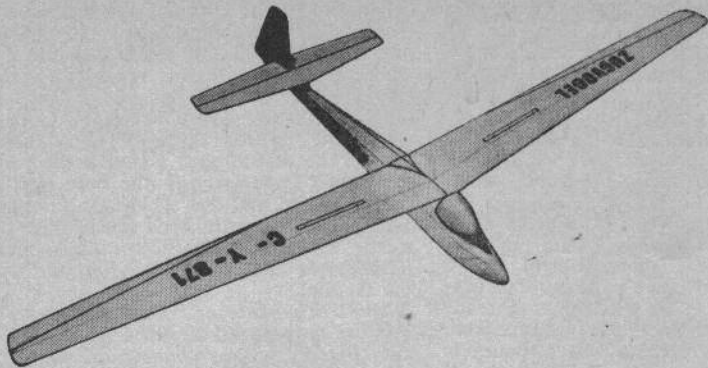

Building instructions in English. Completely descriptive stock list with numbered parts for easy reference. A typical European well engineered kit with plywood bulkheads (all cut out), pine longerons, with balsa sheeting to simulate all wood structure. Two large sheets with servo mounting directions, photos of construction, tissue, hardware & two kinds of glue included.

ZUGVOGEL R/C GLIDER KIT \$27.50

Send 10¢ in coin for 1964 Catalog

Direct - or from your dealer

Robbe True Scale kit - ZUGVOGEL - With ailerons and spoilers for 10 channel relayless equipment
Wing span - 94½" Wing area 825 sq. inches

WILLOUGHBY ENTERPRISES
14695 Candeda Place
Tustin, California. 92680

Perspective

(Continued from page 11)

we believe there is absolutely no margin for error. Only our most experienced production workers will be allowed to work on a system, and they will be instructed to take all the time necessary for perfection. There is a close correlation between the number of components in the system and the probability of failure. The only way the failure probability can be reduced is by intensive quality control standards. So far we have considered only production costs. As manufacturers, we must at least try to recoup the tens of thousands of dollars invested in the system's development. Certainly it should be obvious that a true proportional system must sell for several times the price of an equivalent reed system.

As manufacturers we have been guilty of overenthusiasm (because we are enthusiasts). For the past year production of our system has always seemed "just 60 days or less away." Then another 500 or so test flights would show up a weak point and back to engineering went the system. Each time it grew more complex as reliability needs indicated changes. Finally, the system seems to be completed, but our original cost estimates prove much too low. Perhaps we have aimed too high in our standards. We think not for very practical selfish reasons. If we cannot produce a trouble-free unit which the average user can expect to fly for long periods without maintenance, then we are better off to forget it.

Manufacturers do not make a profit or good will by repairs on defective systems. The proportional system can be excellent in respect to response, tracking, tight neutral, complete neutrals, complete freedom from drift, reliability, long service life, etc., if the enthusiast is willing to pay.

Why should proportional systems have to be so complex and difficult to produce? As stated before, if proportional systems don't work just about perfectly, one can do a better job of flying with reeds, so why bother. A look at the variety of systems currently under development and some of the problems involved should give an idea of the reason behind the proportional system's complexity.

First, and most difficult, is the RF link between the transmitter and receiver. This link must be analogous to a mechanical connection, yet our aircraft is rapidly moving through widely varying RF field strengths, is subject to out of phase (reflected signals) and interference on our crowded frequencies. Momentary loss of contact results in what we have come to call "glitches" or a short duration hop or twitch of the aircraft. A longer loss of the RF link results in the mating call of the proportional flyer (mating of the aircraft with earth, usually permanent) of "I ain't got it."

Our reed systems do not depend on such a tight RF link. Momentary loss of contact or RF phase reversals are completely unnoticed. Also, reeds are resistant to all but the most severe interference. Consequently, the proportional system requires

a more sophisticated and more expensive receiver than do reeds.

It is not the purpose of this article to go into detail regarding the various proportional systems. However, there are three distinct approaches under development or production. One uses variable tones transmitted in alternate sequence for the four channels of information. A second method is best described as CW transmission of either pulse-width variable carrier or spiked off carrier, both of which utilize digital logic techniques for decoding. The third system uses pulse width modulation of a subcarrier or subcarriers in combination with pulse rate changes or, as used in the latest Pullen system, digital logic decoding techniques.

System No. 1 is probably the oldest, and in our opinion, the least practical system. It is difficult to manufacture, tends towards interaction of control, and hard to stabilize. The error output to the servos is limited, and consequently, servo tracking and response is usually poor. The second systems are all variations of the original Digicon. They can feature excellent response, tracking and stability. However, we believe they are subject to interference and are uniquely subject to RF phase problems. The No. 3 systems can have the same features as No. 2 combined with the interference protection provided by the subcarrier. The subcarrier system also eliminates RF phase-shift problems. The major disadvantage to the subcarrier system is the somewhat noisier servo movement caused by the chopped subcarrier. This, however, is



BECOME AN R.C.M. & E. READER

SUBSCRIBE NOW!

1 Yr.	12 BIG ISSUES	\$ 5.00
2 Yrs.	24 BIG ISSUES	\$10.00

Ace Radio Control, Box 301, Higginsville, Mo.

Enclosed find \$5.00 for 1 yr. subscription

Enclosed find \$10 for 2 yrs. subscription

Name _____

Address _____

City _____ Zone _____

State _____

Send 50 Cents for Specimen Copy

NEW 1964 FOX MOTORS


FOX 59R/C



Best of the big motors! No "break-in." Exclusive Fox carburetion maintains proper low speed mixture at any attitude.

\$39⁹⁵

FOX 07

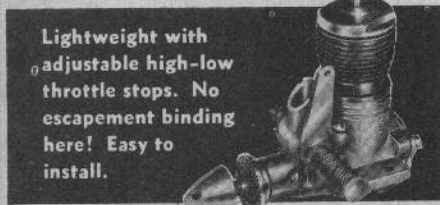

Lightweight with adjustable high-low throttle stops. No escapement binding here! Easy to install.

\$10⁹⁵

FOX
MANUFACTURING COMPANY
FORT SMITH, ARKANSAS

Have More Fun with RADIO CONTROL . . . get R/C primer

by Howard G. McEntee



68 PAGES ON:
Frequency and licensing info
Control Components
Transmitters
Installation
Model Boats
Field Tests
Maintenance
Troubleshooting

\$2.00

This new book on the fundamentals of radio control tells how R/C functions, how to mount them, how to service and maintain them. Many diagrams and sketches on the USE of R/C, NOT on building 'em!

CLIP & MAIL

Kalmbach Publishing Co.
Dept. 717-GL, Milwaukee, Wis. 53233

Enclosed find \$2.00. Please send postpaid your new book, R/C Primer.

Name _____

Address _____

City, Zone, State _____

not noticeable at the control, and we believe that the subcarrier is necessary for reliability.

The variety of methods for proportional control under development indicates the embryonic stage of design. They are all complicated and the systems which show promise are much more complicated than the others. Perhaps there may soon be a radical break-through with a simple reliable control system which all of us can afford. It is also possible that we may be entirely too old to enjoy the hobby when this occurs.

In the meantime, I believe those coming into the hobby or now in it and ready to advance to multi-channel control would be well advised to move with caution. It is much more fun to fly reliably with reeds than to suffer with an exotic but unreliable control system. For those where money is no object, we at Kraft Radio Control will offer a custom proportional control system. The price will be \$800.00 to \$900.00. Is it worth the price for merely enjoying the hobby, which should be our main concern? It most certainly is not. However, if you must have proportional control, we believe it is worth every cent.

(Publisher's comment: Every once in awhile a manufacturer will let his hair down and speak straight from the shoulder. This, in our opinion, is what Phil Kraft has done in this article. His reasoning, we feel, is logical and to the point.)

Phil's interpretation of "true proportional control" may not agree with other manufacturers' opinions, or our own. We do believe that the validity of Phil's statement of policy merit the use of the columns of GRID LEAKS, and we are presenting his article with no cuts.

Comments are invited from individuals, manufacturers, and other interested parties, on this "perspective" on proportional.)

Gemini Switcher

(Continued from page 10)

capacitors, as they must be reinstalled whenever the Transmite is used with a reed system.

3. Locate where the red and brown wires are soldered to the printed circuit switching plate in the lid of the Transmite. Solder one end of an 1/8-in. length of blue insulated hookup wire to the same pad as the red wire on the P/C switching board. Solder one end of an 8-in. length of brown insulated hookup wire to the same pad as the brown wire on the P/C switching board. Lead both new wires out of the servo through the grommet along with the rest of the cable.

4. Inspect the rudder Transmite amplifier board and determine if two or three 100-ohm (brown, black, brown) resistors are used in the area shown in figure D. Transmite amplifiers built since mid 1962

have three 100-ohm resistors and this amplifier requires no further modification. If only two resistors were used the third resistor must be added. Unsolder the original blue wire (not the one just added) from the P/C switching board. Now solder one end of a 100-ohm resistor to the pad where the blue wire was removed. Solder the blue wire to the other end of the 100-ohm resistor as shown in Fig. E. Goo or epoxy the resistor to the P/C switching board. The resistor just added is the resistor shown in series with the base lead of transistor Q6 on the schematic diagram. The 100-ohm resistor need not be removed if the servo is used in a multi system. Reassemble the Transmite for use with the Gemini.

Gemini Schematic and Circuit Operation: For the purpose of simplifying the schematic, Fig. F, several connections were not shown. They can be clearly seen by mentally noting that RR1 ties to RR2, LR1 ties to LR2, and RN1 ties to RN2. RR2 is the yellow signal wire and LR2 is the orange signal wire from the rudder servo. ENG1 and ENG2 tie to the yellow and orange signal wires from the engine servo.

The positive end of a six cell series connected battery pack is designated 0 volts. Connections to 0, -2.4, -4.8, and -7.2 volts are shown—1.2 volts per cell.

Transistors in digital circuitry may be thought of as switches. "On" transistors will allow current to flow from the emitter to collector whenever the base-emitter junction is forward biased. For PNP transistors this means the base must be more negative than the emitter, for NPN transistors the base must be more positive than the emitter. "Off" transistors will not allow current flow because their base-emitter junctions are for forward biased. This could mean either that the base and emitter are at the same voltage or that the base emitter junction is reverse biased.

The Gemini circuitry consists of:

1. The rudder servo amplifier Q1-Q6. The circuitry shown is basically that of the Bonner neutralizing Transmite amplifier and is included in the schematic to show its function to the Gemini operation. The engine servo amplifier is identical so it is not repeated on the schematic in the interest of simplicity.

In neutral, signal wires RR2 and LR2 are nonconducting. Q1 and Q4 are biased off by their base resistors which are tied to -7.2 volts. Q2 also sees -7.2 volts on its base and is biased off, which allows Q3 to remain on since its base is tied through a resistor to -4.8 volts and the emitter voltage of Q3 is about -6 volts. If the diamond-shaped neutralizing wiper on Q3 collector contacts either printed-circuit switching pad (located in the lid of the Transmite servo) either Q5 or Q6 will be turned on and the servo motor B1 will drive the P/C pad wipers in the proper direction until the neutralizing wiper runs off the P/C at neutral and opens the base Q5 or

SPECIFICATION FOR THE GEMINI SWITCHER

Ambient Operating Temperature Range: 0 to 130 degrees F.

Weight: Rudder-Motor Version (RM-1) 3 oz.

RM-1 System (Switcher, rudder and engine servos, 3-volt receiver and Nicad batteries) 16 oz.

Size: RM-1 1-13/16 X 2-11/16 X 1

Construction: Glass-cloth epoxy-resin-laminated printed-circuit board. Separate color-coded cables contain complete wiring to batteries, a 3-volt receiver, the rudder and the engine servo. Industrial quality American-made components are used throughout.

Battery Requirements: Six 450- or 500-mah minimum capacity nickel cadmium batteries connected in series and tapped at 0, -2.4, -4.8 and -7.2 volts.

Voltage Range: 7 to 9 volts measured across the six cells.

Current Drain: Approximately 25 ma Idle RM-1
35 ma Signal RM-1

NOW, 24 HOUR ASSEMBLY!

COMPLETE CONTROLS!
Rudder, Elevator,
Ailerons and Engine.
Wing Span: 57"
Wing Area: 620 sq. in.
Wght.: 5 lbs.

COMPLETE KIT
only \$14.95

TAKE A GOOD
LOOK AT

JENNY

THE NEW LIVEWIRE!

Versatile!

Use the "JENNY"
for . . .

TRAINING!
ACROBATICS!
CONTESTS!
COMBAT!

and considerable FUN!

SEND FOR COMPLETE DETAILS!

New Type Kit!

Assemble the "Jenny"
. . . Like a plastic model
from completely fin-
ished parts, even the
plywood fuselage! Kit
has many unusual fea-
tures plus all the bits
and pieces required.

SINGLE TO MULTI CHANNEL RADIOS!

.19 to .45
Engines

2 or 3 wheel
landing gear!

deBOLT MODEL ENG. CO.

3833 HARLEM RD.
BUFFALO 15, N. Y., U. S. A.

Q6 circuit. The neutralizing wiper and the limit switch wipers from the bases of Q5 and Q6 run in the same direction at the same time and is shown by the dotted line which indicates the wipers are mechanically tied together.

Having shown that with no signal input to RR2 or LR2 that the servo will self neutralize, let's take a look at what happens when a signal is applied. Suppose that RR2 is tied to -2.4 volts. Two things happen. One, Q2 is turned on, which turns Q3 off. No current can now flow through the neutralizing wiper to either Q5 or Q6 even if the neutralizing wiper is on a P/C pad. Two, Q1 is turned on and supplies current through the limit switch wiper to the base of Q5. Motor B1 drives and moves down the P/C pads until the Q5 base limit switch wiper runs off the end of the Q1 collector P/C pad. Base current to Q5 is broken and the motor stops with the rudder at full right.

During the same time the neutralizing wiper has moved onto the Q4 collector P/C pad and the Q6 base limit switch wiper has moved farther down the same pad. The servo will stay in full right until the signal wire RR2 is opened. When RR2 is opened, the initial conditions for neutralizing are set up and Q3 supplies base current to Q6 to drive the servo back to neutral from right. If, instead, LR2 had been tied to -2.4 volts, Q3 would be turned off as before and Q4 would supply base current to Q6 and the servo would drive to left rudder and remain there as long as the signal is held. Neutralizing is the same as for right rudder except Q5 will conduct the motor current. If the signal is released before the rudder servo gets to full right or left, the neutralizing circuitry simply takes over and drives the servo back to neutral. The circuit operation just described applies specifically to the Gemini operation. As a matter of interest, the servo amplifiers operate identically in a resonant reed relayless bang-bang multi hookup except the yellow and orange signal wires are tied to 0 volts through the vibrating reed, and filter capacitors are tied between RR2 and LR2 and 0 volts to filter the DC pulses coming from the vibrating reeds.

2. The Schmidt trigger Q7 and Q8. The Schmidt trigger is a voltage level detector. It determines whether the rudder servo will run toward right or left when the receiver relay is pulled in. If the input voltage at the junction of the 4.7K and 10K resistor is more positive than minus one volt, Q7 is off and Q8 is on. When the input voltage is more negative than minus one volt, Q7 is on and Q8 is off. The collector volt-

age of the on transistor will be approximately -.5 volts and of the off transistor will be approximately -4.8 volts.

3. The rudder servo "AND" Gates Q9 and Q10. "AND" Gates have two inputs which must be of the correct polarity for the transistor to conduct. The emitters of Q9 and Q10 are tied together and are at -7.2 volts when the receiver relay is open, one input comes from the receiver relay. The receiver relay ties across the 15-UFD filter capacitor and supplies -2.4 volts to the Q9 and Q10 emitters when the relay is closed. (Transmitter key is depressed.) The filter capacitor filters out relay contact bounce which may be as many as a dozen bounces lasting for 2 or 3 milliseconds. All relays and switches exhibit this bouncing when they are closed. Pulsed relay proportional fans take note.

The second input is supplied by the Schmidt trigger. If the rudder servo is resting at neutral when the receiver relay is closed, the input to the Schmidt trigger is 0 volts, since Q4 is turned off by the -7.2 volt bias as described earlier and the Q4 collector pad is tied to 0 volts through the Q6 base limit switch wiper and Q6 base resistors. Schmidt trigger Q7's collector is at approximately -4.8 volt. "AND" Gate Q9 base is tied to Q7 collector through the 2.2K resistor and, since Q9 emitter is now tied to -2.4 volts through the closed receiver relay, Q9 will now conduct to signal wire RR2 and the rudder servo will be driven toward right. Q8 collector is at approximately -.5 volts and "AND" Gate Q10 cannot conduct because Q10 base is tied to Q8 collector through the 2.2K resistor and Q10 base (-.5 volts) is more positive than its emitter (-2.4 volts). The rudder servo will remain right as long as the receiver relay is pulled in. When the receiver relay is released, Q9 can no longer conduct and the Transmite neutralizing circuitry turns on Q6 to drive the servo left toward neutral. The neutralizing current flowing through the resistor between Q6 limit switch wiper and Q6 base causes a voltage drop across the resistor. The voltage on the Q4 collector printed circuit pad becomes more negative than -1 volt (usually -4 to -7.2 volts) and Schmidt trigger Q7, Q8 switches and applies -.5 volts to Q9 base resistor and -4.8 volts to the Q10 base resistor. If the receiver relay is left open, neither Q9 nor Q10 can conduct and the neutralizing circuitry continues to drive the rudder servo back to neutral.

If, however, the receiver relay is once again closed while the neutralizing circuitry is driving the rudder servo back to neutral from right, Q9 and Q10 will now have -2.4 volts applied to their emitters. Only Q10

can conduct and this ties LR2 to -2.4 volts which turns on Q4, which in turn supplies current to Q6 to drive the rudder servo left. Neutralizing circuitry Q3 was turned off as Q4 came on. Since Q4 is now conducting, the Schmidt trigger input continues to stay more negative than -1 volt. When the Q6 limit switch wiper runs off the Q4 collector P/C pad, the 10K resistor from 0 volts to the Q4 collector acts as the Q4 collector load and the input to the Schmidt trigger is maintained at more negative than -1 volt as long as the receiver relay is held in at left rudder. Now, when the receiver relay is released, Q10 ceases to conduct and the Transmite neutralizing circuitry turns on Q5 and drives the rudder servo right toward neutral. As the relay

ADAMS PROPORTIONAL ACTUATOR



THIS PATENTED PROPORTIONAL ACTUATOR has many features not found on others of its type. Designed for $\frac{1}{8}$ A to $\frac{1}{2}$ A airplanes. Weighs 29 grams, has 30 ohm coils on each side of the double coil, pulling 100 MA at 3 volts. May be used up to 6 volts. Designed for double ended relayless or relay type receivers. Features a Delrin bearing which never requires any lubrication, and makes the actuator free swinging, and is part of the secret of its fantastic performance. Adams Manufacturing Co. was one of the first to introduce a proportional actuator. This is a refinement of eleven years of testing.

Only \$6.95. Available through your Ace R/C dealer. Janesville, Wisconsin

Adams Manufacturing Co.
Janesville, Wisconsin

Citizen-Ship

- **SELECTIVE SUPERHET** Flying for ALL Classes of R/C
- **COMPLETE SYSTEMS PACKAGES**

IN '64

RSH SINGLE CHANNEL RELAYLESS SELECTIVE SUPERHET RECEIVER

The SMALLEST Superheterodyne Receiver on the market. 1/4A or 1/2A plane accommodates complete installation. Battery requirement 2 pencils. Selectivity permits flying 6 planes at same time. Especially designed for use with CITIZEN-SHIP SPX or TTX Transmitter.



\$34.95

Available in all 6 legal FCC Frequencies.

Suggested list price

6 CHANNEL ALL TRANSISTORIZED SELECTIVE SUPERHET SYSTEM:

\$189.95

Suggested List Price

The all purpose system—multi for the beginner OR the contest flyer. (For rudder, intermediate or pylon racing.)

Complete System—**SAVE \$17.80**

over items purchased separately
SL-6 ALL TRANSISTORIZED High Power Transmitter. If purchased separately, suggested list price**\$74.95**
RL-6 ALL TRANSISTORIZED SUPERHET Relayless Receiver. If purchased separately, suggested list price.....**\$54.95**
3 TNA SERVOS purchased separately — Suggested list priceea. **\$25.95**



SL-6

COMBINATION PACKAGE

SL-6 Transmitter and RL-6 Receiver

\$119.95

Suggested List Price

SAVE \$9.95

over items purchased separately

Available in all legal FCC Frequencies



RL-6

NEW BARGAIN PACKAGE Complete Single Channel System. SAVE \$2.95

OVER ITEMS PURCHASED SEPARATELY

TTX Transmitter (no license required) packaged with completely wired R/C Pak w/SE-2 Escapement—Suggested List Price.....**\$61.95**
 w/PSN-2 Escapement—

Suggested List Price.....**\$59.95**

CITIZEN-SHIP "Awards" Program continued in '64

Send for Catalog for complete description of all Citizen-Ship equipment and details of "Awards" Program.

Citizen-Ship

RADIO CORPORATION

810 E. 64th St.

Indianapolis, Indiana

was released, Q4 collector voltage became 0 volts and the Schmidt trigger resets to drive the rudder toward right the next time the receiver relay is pulled in.

4. Engine storage trigger Q11. Q11 puts out a positive going pulse each time the receiver relay is closed while the rudder servo is running from left to neutral. Only during this phase of operation is RN1 more negative than RR1 which is the condition needed for making Q11 conduct. These pulses are used to trigger the engine speed storage circuitry.

5. Engine speed storage circuitry, bistable multivibrators Q12, Q13, Q14, and Q15. The two bistable multivibrators are similar in operation to the Schmidt trigger in that one transistor is on while the other is off. The difference is that the Schmidt trigger output depends on the voltage level at the input while the bistable multivibrator changes state each time a pulse is received. In others words, say that Q12 is on and Q13 is off. They will remain that way indefinitely until their input circuitry receives a positive going pulse from Q11. Then Q12 will be off and Q13 will be on. The two will reverse outputs each time a pulse is received. The bistable multivibrator is the basic counting circuit in all digital computers. The bistable multivibrator composed of Q14 and Q15 is triggered by a positive going signal from the collector of Q13. The important thing to see here is that while multivibrator Q12, Q13 changes state once for each pulse that comes from Q11, multivibrator Q14, Q15 changes once for every other pulse from Q11 since it is triggered only when Q13 collector goes positive, which is every other time multivibrator Q12, Q13 changes. A positive going pulse is one which goes from a given voltage level to a more positive voltage level.

6. "AND" Gates Q16 and Q17. Q16

and Q17 complete the logic circuitry which supplies -2.4 volt signals to the engine servo signal wires, ENG1 and ENG2. A look at the voltage at the bases and emitters of Q16 and Q17 will quickly show their operation. There are four voltage combinations available from the two multivibrators. These four combinations correspond to the engine speed sequence high, medium, low, medium.

For the multivibrators assume the collector voltage of the on transistor is -2.4 volts and of the off transistor is -7.2 volts. These voltages are applied to the Q16 and Q17 "AND" Gates and are as follows in Fig. G.

Q16		Q17		Result
BASE	EMITTER	BASE	EMITTER	
-7.2	-7.2	-7.2	-2.4	High ENG.
-2.4	-7.2	-2.4	-2.4	Med ENG.
-7.2	-2.4	-7.2	-7.2	Low ENG.
-2.4	-2.4	-2.4	-7.2	Med ENG.


In high engine only Q17 is on because its base is more negative than its emitter while Q16 has its base and emitter both at -7.2 volts and thus is turned off. In medium engine neither Q16 or Q17 can conduct since their base emitter junctions are not forward biased. In low engine Q16 is on and Q17 is off.

As each pulse is put through Q11 the engine speeds will be repeated in sequence. When either Q16 or Q17 is on the engine servo will run to one extreme or the other. When both Q16 and Q17 are off the neutralizing circuitry in the Transmite returns the engine to medium speed.

The engine storage multivibrators, then, will count and store the number of engine speed change pulses received and will change the engine speed accordingly and hold it there until the next engine speed change pulses are received.

OMEGA SALES & ENGINEERING

NEW

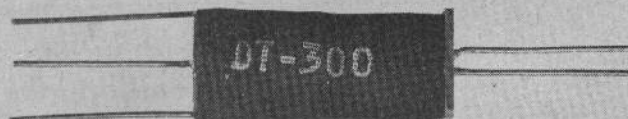

OMEGA'S MINIATURE "SPDT" MAGNETIC REED RELAYS

MODEL	PULL-IN SENSITIVITY	RESISTANCE	PRICE EA.
300-DT	6 to 10 Ma max @ 1.8 to 2.8 V	300 ohm	\$5.95 p.p.
HR-DT	2 to 3 Ma max @ 7 to 9 V	3600 ohm	\$6.95 p.p.

OMEGA MINIATURE "SPST" MAGNETIC REED RELAYS

MODEL	PULL-IN SENSITIVITY	RESISTANCE	PRICE EA.
AR-300	8 to 15 Ma @ 2.5 to 4.5 V	300 ohms	\$3.50 p.p.
AR-500	4.5 to 10 Ma @ 2.3 to 5.0 V	500 ohms	\$3.75 p.p.
HR-1	1.5 to 2.7 Ma @ 5.5 to 9.5 V	3600 ohms	\$4.00 p.p.

NOTE: For a Specific Pull-In of any of the above, add 25¢ to the price of each unit.

SIZE: 3/8" x 3/8" x 7/8"

Send Check or Money Order — No C.O.D.'s.

- Model 300 DT — \$5.95 p.p. Model HR DT — \$6.95 p.p. Model AR 300 — \$3.50 p.p.
 Model AR 500 — \$3.75 p.p. Model HR 1 — \$4.00 p.p.

NAME _____
 STREET _____
 CITY _____ STATE _____ ZIP _____

OMEGA SALES & ENGINEERING • BOX 321, RACINE WISCONSIN 53401

The Monitor

(Continued from page 2)

down finally he made some "100 vertical banks." After it hit the ground he realized in his excitement that he had not let up on the button. While the Cub stood up, the tube receiver, not very well tied down, was smashed and the escapement was a "pretzel."

Reminding us of a remark we'd made in *Flying Models* that "there is no need to teach model building to any reader capable of tackling R/C, etc.," Tony commented, "... but it seems all the writers find no need for explaining anything in detail. One is supposed to know all these things somehow, or one has no business fooling with radio. How does one learn when there is no person around to explain the workings of this highly intricate thing?"

"I saw an ad for a new type of pulse set-up. I wrote the manufacturer to please send me some details. Apparently, they just make them. They don't explain them. So I will not buy same. I bought a lot of things that I probably will never use, just to learn the how's and why's."

"There's a young lad here who would like to get into R/C, but the price tags of some of the equipment loom very large since his income is so small. I think this is the biggest problem that is keeping the younger set out of this wonderful sport, even more than a lack of a helping hand from oldtimers."

We since had several long, long letters from Tony. He went through a disastrous big powered glider and, after it settled off a cliff with a tiny engine howling like mad, and cracking it up several times, asks why the manufacturer didn't say it was for experts. He started off with a McCoy 19 on a Freedom 15—a perfectly good model by the way—cut down to a Fox 15 and



The biggest smile in this pic belongs to Harry Sampey, caught talking shop at Toledo Conference by GL photog.

finally a Fox 10 turning a 9 x 4 before he could fly it, and this sort of thing is almost standard procedure with a beginner anyway. He seems to have hit the jackpot with a Skylark with a Fox 15 and a 9 x 4 prop. (Perhaps he has only finally mastered control technique.)

"Now I am interested in a battery complement that is lighter and also rechargeable. But I can't decipher the ads and this is maddening. For example," Tony points out, "a nicad 500 mah, or a 250 mah—what is it? How many volts does it put out? What do I need for running an escapement and a 3-volt receiver? I like to have a separate battery for the receiver and the escapement (you learn by osmosis!). Why can't the manufacturers explain these things? They would sell more if the average guy was able to understand the mumbo-jumbo. Don't they realized that beginners could use nicads? Most beginners use


WORLD WIDE RADIO CONTROL

9810 WYOMING, DET. MICH. 48204 dept 6L5

Clip and paste to card for your free copy of "Quick Blips" or shoot us a dime for the latest World Wide catalog, don't forget your name and address.

- Please send me Quick Blips
 Here's my dime for a catalog

PAINLESS PROPORTIONAL

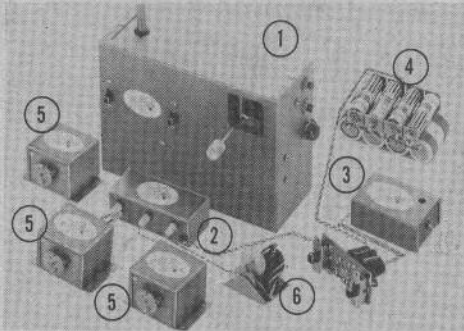

1. All transistor tone transmitter with left hand throttle advance and retard.
2. Decoder will provide two separate and simultaneous commands, one selective command.
3. Super Het receiver, single tuning slug, rejects adjacent channels.
4. Battery pack. 4. 1200 mah nicad pack included.
5. Proportional servo, 49 to 1 gear ratio, low current drain of 150 ma during operation.
6. Trimmable throttle servo, med. to fast throttle operation. Completely wired ready to plug in. Field charger not illustrated.



You can't beat it! \$12.95 gets you a battery pack of solder tabbed 500 mah nicad sintered plate cells. Welded together and sleeved with vinyl. Wt. 4.7 oz. 1 3/8 dia. X 1 7/8. NEED BUTTON CELLS? 225 mah .85 ea. 450 mah 1.47 ea. 500 mah 2.39 ea. All cells have solder tabs

Easy on the pocket book. Easy to install. The Multiplex Master Proportional Radio Control system puts you in the air right now! Enjoy the versatility of "multi" flying with this fine deluxe completely built-up system. You get transmitter, decoder, receiver, 3 proportional servos, trimmable motor servo, battery pack, field charger and service kit. Just plug it together and GO! Superhet and fully fail safe of course. Yes, with the Multiplex Master you can operate nose wheel, brakes and more. All this for only \$224.95.

TAG THIS!
TWO WORLD CHAMPIONS!
 Ed Kazmirski's magnificent "Orion" from Top Flite

EITHER KIT 1750
 Tom Brett's sleek "perigee" by DeBolt

dry cells because they don't know what else to buy. (Tony uses nicad in a general sense—it is a Gould-National tradename.)

"Someday, I might like to go to proportional with the single-channel gear I now have. But first I have got to know more about what's a good unit, and what isn't. And, more to the point, how does it work? A guy does not have to be an electronics expert to fly R/C but from all that I get out of the ads, it would sure help like..."

Back in the days when everything was single-channel and there was only one make of escapement and everybody used standard dry batteries, it was comparably easy to write useful instructional articles. Today there are so many variations to radio that the story cannot be told properly even in a book. Nor is it very easy, or perhaps even feasible, to prepare a completely

honest article about even such a simple thing as single channel.

Two summers ago when we designed the Miss America kit, we ran the gauntlet of almost every make of relayless receiver, receiver and escapement combination, dry batteries, alkaline batteries, and nickel cads. No beginner looked worse! Do you tell a beginner he must use nickel-cads when the voltage—and it is more when freshly charged—may exceed the safe voltage of a receiver, or that a receiver may not even oscillate (what's that?) at such a voltage. That on a hot day a transistor may leak, due to this voltage, to hold the escapement in, or to lock it in when in the air (interference, you say!). What about dry cells with false bottoms? Ditto on energizers. What about escapement spring tension—sometimes set so low that

NEW! AIR-SPAN FAST^{ER} LINK
 FINE ADJUSTMENT—POSITIVE

Watch for **AIR-SPAN'S** new **TRIM BAR ASSEMBLY**

FULL CONTROL YOKE ASSEMBLY 29c

SPRING STEEL YOKE
 Easy on and off on the field

SPLIT SLEEVE
 for Solid Solder Joint

F&N PRODUCTS
 1024 Dodge Ave.
 Evanston, Ill.

3/4" thread on 4" rod
 1/2" of fine adjustment

SUPERHET QUADRUPLIX

You asked for it - Now you can have it!

IT'S TRANSISTORIZED

Solid state servo amplifiers are employed, and through advanced design technique and the use of high quality components, they are immune to extremes in temperature and humidity.

IT'S PREWIRED

Elevator and rudder servos, Dee Bee modified Bellamatics, are mounted on a sturdy 2 1/4" by 5" fiberglass base, along with the servo amplifiers, the on-off switch, and sockets for plugging in the aileron and engine speed servos.

IT'S SMALLER


The model "21" receiver measures only 2 1/4" by 1 3/4" by 3 3/4". The "21" transmitter, with circuitry nearly identical to that used in the Mk II and including a front panel charging jack, is two inches shorter than the Mk II.

IT'S TESTED

In spite of continued requests from flyers who knew he had a superhet Quadruplex receiver over a year ago, Don Brown wouldn't release the "21" until it had gone through many hours of test-flying and bench-checking. The problems of combining superhet with multi-simultaneous tone separation have been overcome. Don has been the guinea pig. You are expected only to have the pleasure of using dependable equipment!

IT'S \$479. COMPLETE

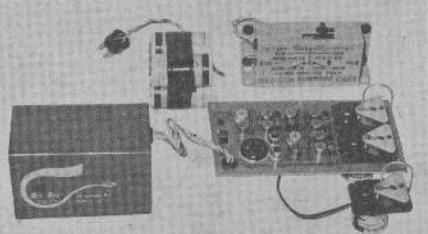Includes transmitter, receiver, amplifiers, four servos, and all required sealed nicad batteries.



the QUADRUPLIX "21"

That means only 21 ounces of airborne equipment, including the four 1.25 amp/hour nicad rcvr/servo battery pack.

Still the most for the money in multi-proportional equipment, the superregen QUADRUPLIX Mk II, on CB or 6 meters, will continue to be available for the remarkably low price of **\$389.95**

CHARGER . . . Not included with the "21" or Mk II systems, a transmitter and receiver battery charger is available as added reliability insurance—only \$15.95



FOR YOU:

Each month the staff of R/C Modeler wraps up another issue designed to bring you the finest material and latest information in the radio control field.


Successful designers and flyers explain the latest trends in RC, providing YOU, The RC'er, with up-to-the-minute data on every phase of our sport.

Whether at home or abroad, your RCM editors are constantly searching for new and better material. Foreign news, compiled by Cliff Rausin, is brought to you while it is still news; W. R. Weaver discusses RC techniques in the Far East; Bill Murray scans the Canadian scene; and whether in Germany or Belgium, South Africa or New Zealand, RC activities from every far-off point of the globe are as near as your mailbox.


The result is the most complete magazine ever published covering interests vital to the radio control modeler. It is YOUR magazine — written by RC'ers for RC'ers. If you have not already done so, use the coupon to subscribe today.

even an .049 will cycle the thing until the rubber runs down. The details are legion. Do they really need to be?

What will help? Well, for one thing, we "experts" seem to have forgotten that simple models are just as much fun as the multi missiles, that flying them properly is a special art, that reliability, in any system and for any modeler, is of paramount importance, that we can't take simple things for granted, that people need help, that we all need to explain better and go easy on this insider's jargon stuff . . . ad infinitum.

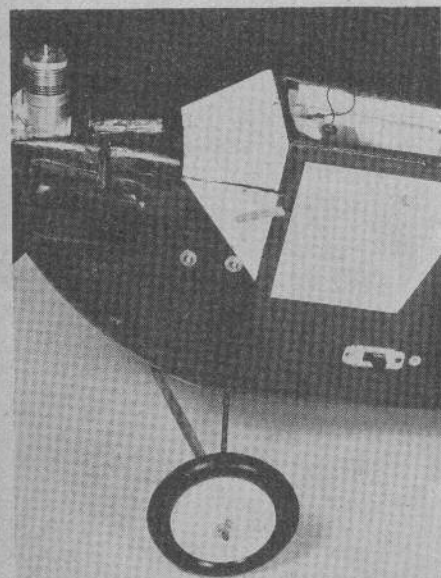

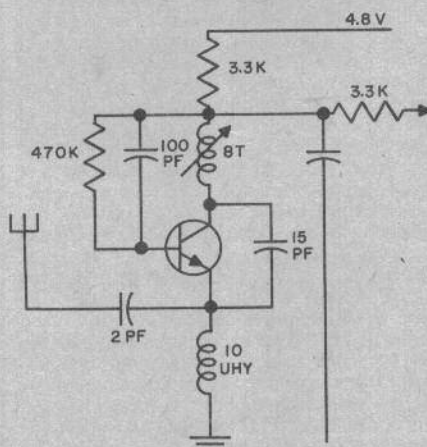Williams Bros. wheels lend old-time air to period crates. Great for WW-1. Here, ye ed dolled up an Airknocker.



This schematic shows changes to the Phelps' receiver for 50-54 mc usage.

We suppose the Bulldog tank, to say nothing of the boat pictures, in this issue, and the Nautilus sub in the last, may not interest every airplane man. Having built 90-plus R/C planes and at long last losing count, your editor can take or leave things that are aquatic or run on the ground, but to ignore anything as substantial as R/C boating today seems akin to editorial segregation. We have faith, however, that the constructive info and ideas, especially in operational systems, displayed in the relatively few such items published in GL, will not be lost on the most avid plane enthusiast, who we suspect, has moments when he'd like to forget the repairs or the latest interference rumors.

Extra pages allow us to broaden policy without decreasing the things for which GL always has been noted.

Gentlemen:
Enter my subscription to R/C MODELER
 for 1 year for \$ 5.50
 for 2 years for \$10.00

Name _____

Address _____

City _____ State _____

Clip and Mail This Coupon with Payment to:

R/C MODELER

P.O. Box 487, Sierra Madre, Calif.

Kraft Custom Radio Control

TAKES PLEASURE IN ANNOUNCING AN EXCLUSIVE

FRANCHISE DISTRIBUTION PLAN!

In order to pass on to the consumer the lowest possible user cost for quality R/C, Kraft Custom Radio Control announces that effective March, 1964, all Kraft Custom equipment will be distributed exclusively by through Franchised Dealers. New prices also will go into effect.

This is a first in the R/C industry. It will provide the finest in distribution for the consumer through his Franchised Dealer. Further details on the Franchise plan may be had by writing Ace R/C, Inc., Box 301, Higginsville, Missouri 64037.

KRAFT CUSTOM PRICE LIST 3-64

Model No.	Item	User net
KTx1 and KR-1	Matched Single Channel Transistorized Transmitter and Single SH Receiver (NOTE: Both are new items)	\$ 64.95
KT10 - KR10	Matched 10 channel Receiver and Transmitter	\$189.90
KT12 - KR12	Matched 12 channel Receiver and Transmitter	\$209.90
KT-10	10 channel Transmitter	\$119.95
KT-12	12 channel Transmitter	\$129.95
KR-10	10 channel Receiver	\$ 79.95
KR-12	12 channel Receiver	\$ 89.95
KRSC-1	Single channel Convertible Receiver	\$ 49.95

Available in the following frequencies at the same prices:

CB: 26.995, 27.045, 27.095, 27.145, 27.195 mc.

Hams: 52.950, 53.025, 53.100, 53.175, 53.250 mc.

Kraft Custom Radio Control

SOUTH EL MONTE, CALIFORNIA

AWARD WINNING "SAMPEY 404" PROPORTIONAL EQUIPMENT
HOLDER OF NATIONAL CHAMPIONSHIP AND WORLD'S ALTITUDE RECORD

buy NOW!

IMMEDIATE DELIVERY

On TIME!

THROUGH  TIME PAYMENT PLAN

**at
LOWER
PRICES**

MODEL 404-B1 BASIC SYSTEM

\$399

1 ea. Transmitter — 1
 ea. Receiver Super-Het.
 4 ea. S-75 Servos.
 The Model 404-B
 transmitter and re-
 ceiver operate on 4.8
 volts. Use your pres-
 ent batteries to oper-
 ate the system.

\$79.00 Down — \$20.97 Per Month



Model 404-B2 COMPLETE SYSTEM

\$498
 \$98.00 Down
 \$26.22 Per Mo.

1 ea. Transmitter — 4 ea.
 Servos — 1 ea. Receiver—1
 ea. Dual Charger — 1 ea.
 Airborne Power Pak—1 ea.
 Transmitter Pac — 1 ea.
 Power Junction.

**Model 404-B3 Complete System
(with extras)**

\$525
 \$105.00 Down
 \$27.53 Per Mo.

Same as Model 404-B2 Plus
 1 ea. Preprogram Motor
 Control (Aux. Channel)—1
 ea. Pitch Reversing Control
 (Inverted Flying).

*After nearly two years of manufactur-
 ing proportional systems, the famous
 Model 404 is being advanced to a Model
 404-B which is now in full production.
 Identical to the model 404 in all aspects
 but with a few added features, such as
 the elimination of the airborne power
 converter and subsequent change in volt-
 age to 4.8 volts to permit five hours
 flight time on one charge. Other fea-
 tures include changes in the servo to al-
 low for an extremely long life under all
 conditions. These design advancements
 along with increased production have al-
 lowed us to lower our prices and still
 produce with the highest quality.*

TO SPEED YOUR ORDER — PLEASE CUT OUT AND MAIL

SAMPEY & COMPANY, INC.
 1607 FORSYTHE ROAD
 ORLANDO, FLORIDA

- ADDITIONAL INFORMATION
- PRE-PAID CASH ORDER
- TIME PAYMENT ORDER

NAME _____ MODEL 404-B1
 ADDRESS _____ MODEL 404-B2
 CITY _____ ZONE _____ STATE _____ MODEL 404-B3

AMOUNT ENCLOSED WITH ORDER \$ _____ BALANCE \$ _____

Please make cash payment by check or money order—20% deposit required on all C.O.D. orders—all time payment orders will be shipped by REA or truck.

Sampey & Company

1607 Forsythe Road

Orlando, Florida